

LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY(A) (Approved by A.I.C.T.E & Permanently Affiliated to JNTUGV, Vizianagaram) Accredited by NBA & NAAC with 'A' Grade Jonnada (Village), Denkada (Mandal), Vizianagaram Dist. – 535 005. Phone No. 08922-241111, 241112 E-Mail.: lendi\_2008@yahoo.com Website: www.lendi.org

# **Department of Electrical and Electronics Engineering**

# LAB MANUAL

Name of the laboratory: Electrical Engineering Virtual Lab

**Regulation: R20** 

Subject Code: C329

**Branch: Electrical and Electronics Engineering** 

Year & Semester: III B. Tech- II Semester

# INSTITUTE VISION, MISSION DEPARTMENT VISION, MISSION PEO & PO/PSO

LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY

Page ii

### LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY(A)



(Approved by A.I.C.T.E & Permanently Affiliated to JNTUGV, Vizianagaram) Accredited by NBA & NAAC with 'A' Grade Jonnada (Village), Denkada (Mandal), Vizianagaram Dist. - 535 005.

Phone No. 08922-241111, 241112

E-Mail.: lendi 2008@yahoo.com

Website: www.lendi.org

# **INSTITUTE**

# VISION

Produce globally competent and quality technocrats with human values for the holistic needs of industry and society.

# **MISSION**

- > Creating an outstanding infrastructure and platform for enhancement of skills, knowledge and behaviour of students towards employment and higher studies.
- > Providing a healthy environment for research, development and entrepreneurship, to meet the expectations of industry and society.
- > Transforming the graduates to contribute to the socio-economic development and welfare of the society through value based education.

LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY(A)



(Approved by A.I.C.T.E & Permanently Affiliated to JNTUGV, Vizianagaram) Accredited by NBA & NAAC with 'A' Grade

Jonnada (Village), Denkada (Mandal), Vizianagaram Dist. – 535 005.

Phone No. 08922-241111, 241112

Website: www.lendi.org

# **Department of Electrical and Electronics Engineering**

E-Mail.: lendi 2008@yahoo.com

# VISION

To be a hub for imparting knowledge, skills, and behaviour for exemplary contributions in the field of Electrical and Electronics Engineering.

# MISSION

- To impart Technical Education through the state-of-the-art infrastructure facilities, laboratories and instruction.
- To inculcate industry-oriented learning through industrial visits, internships, projects at Industries, MOUs, to make students' technically skills oriented.
- Creating conducive environment for higher education, employment and entrepreneurship through quality education, professional skills and research.
- To promote societal commitment among students by inculcating moral and ethical values.

# **PROGRAM EDUCATIONAL OBJECTIVES (PEOs)**

**PEO1:** Graduates shall have strong foundation in core and allied Electrical and Electronics Engineering, in sciences and mathematics, to become globally competent in designing, modelling and critical problem solving.

**PEO2:** Graduates shall involve in research activities in the field of electrical and electronics engineering through lifelong learning and provide solutions to engineering problems for sustainable development of society.

**PEO3:** Graduates shall have good communication skills and socio-ethical values for getting employment or higher studies by excelling in competitive examinations and be able to work in supportive and leadership roles.

# **PROGRAM SPECIFIC OUTCOMES (PSOs)**

**PSO1:** Capable of design, develop, test, verify and implement electrical and electronics engineering systems and products.

**PSO2**: Succeed in national and international competitive examinations for successful higher studies and employment.

# PROGRAM OUTCOMES (POs)

DO1	Engineering Knowledge: Apply the knowledge of mathematics, science,
POI	engineering fundamentals, and an engineering specialization to the solution of
	complex engineering problems.
PO2	Problem Analysis: Identify, formulate, review research literature, and analyze
102	complex engineering problems reaching substantiated conclusions using first
	principles of mathematics, natural sciences, and engineering sciences.
	Design/development of Solutions: Design solutions for complex engineering
PO3	problems and design system components or processes that meet the specified
	needs with appropriate consideration for the public health and safety, and the
	cultural, societal, and environmental considerations
	Conduct Investigations of Complex Problems: Use research-based knowledge
PO4	and research methods including design of experiments, analysis and
	interpretation of data, and synthesis of the information to provide valid
	conclusions.
PO5	Modern Tool Usage: Create, select, and apply appropriate techniques, resources,
100	and modern engineering and IT tools including prediction and modelling to
	complex engineering activities with an understanding of the limitations.
PO6	The Engineer and Society: Apply reasoning informed by the contextual
	knowledge to assess societal, health, safety, legal and cultural issues and the
	consequent responsibilities relevant to the professional engineering practice.
PO7	Environment and Sustainability. Understand the impact of the professional
	the knowledge of and need for sustainable development
DOQ	<b>Explose:</b> Apply ethical principles and commit to professional ethics and
PUð	responsibilities and norms of the engineering practice
<b>D</b> O0	<b>Individual and Team Work</b> : Function effectively as an individual and as a
109	member or leader in diverse teams and in multidisciplinary settings
	<b>Communication</b> : Communicate effectively on complex engineering activities
PO10	with the engineering community and with society at large, such as being able to
1010	comprehend and write effective reports and design documentation, make
	effective presentations, and give and receive clear instructions.
	<b>Project Management and Finance</b> : Demonstrate knowledge and understanding
PO11	of the engineering and management principles and apply these to one's own
	work, as a member and leader in a team, to manage projects and in
	multidisciplinary environments.
<b>DO1</b>	Life-Long Learning: Recognize the need for, and have the preparation and
P012	ability to engage in independent and life-long learning in the broadest context of
	technological change.



LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY(A) (Approved by A.I.C.T.E & Permanently Affiliated to JNTUGV, Vizianagaram) Accredited by NBA & NAAC with 'A' Grade Jonnada (Village), Denkada (Mandal), Vizianagaram Dist. – 535 005. Phone No. 08922-241111, 241112 E-Mail.: lendi 2008@yahoo.com Website: www.lendi.org

# COURSE OUTCOMES (COs)

- **CO1:** Analyze Basic Network Theorems.
- CO2: Analyze the performance and characteristics of DC Machine & Transformer
- **CO3:** Determine the Equivalent circuit parameters of Induction Motor
- CO4: Apply Speed control techniques of Induction Motor
- **CO5:** Apply the Knowledge of Synchronization to ensure safe integration of synchronous machines and optimize the performance by adjusting excitation to achieve the desired power factor

LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY(A)



(Approved by A.I.C.T.E & Permanently Affiliated to JNTUGV, Vizianagaram) Accredited by NBA & NAAC with 'A' Grade

Jonnada (Village), Denkada (Mandal), Vizianagaram Dist. – 535 005.

Phone No. 08922-241111, 241112

Website: www.lendi.org

#### E-Mail.: lendi\_2008@yahoo.com

**COURSE INFORMATION SHEET** 

# AY-2023-24

PROGRAM: Electrical and Electronics Engineering	DEGREE: <b>B.TECH</b>
COURSE: Electrical Engineering Virtual Lab	SEMESTER: III-II CREDITS: 2
COURSE CODE: C329 REGULATION:R20	COURSE TYPE: CORE
COURSE AREA/DOMAIN: Electrical Circuits & Electrical Machines	CONTACT HOURS: <b>3 Hours/Week.</b>
CORRESPONDING LAB COURSE CODE (IF ANY):-	LAB COURSE NAME (IF ANY):

### SYLLABUS:

UNIT	DETAILS	HOURS
Ι	Verification of Superposition Theorem.	3
II	Verification of Thevenin's Theorem.	3
III	Verification and Norton's Theorem.	3
IV	Magnetization characteristics of DC Shunt Generator. Determination of Critical FieldResistance and Critical Speed.	3
V	Load test on DC Shunt Generator.	3
VI	Speed control of DC Shunt motor by Field and Armature Control.	3
VII	Equivalent circuit of Three Phase Induction Motor.	3
VIII	Speed control of Slip ring Induction Motor.	3
IX	OC & SC Test on Single Phase Transformer.	3
Х	V and Inverted V curves of a Three Phase Synchronous Motor.	3
	Additional Experiments	
XI	Verification Of Maximum Power Transfer Theorem	3
XII	Synchronization of Alternator With Infinite busbar	3
	TOTAL HOURS	36

# **TEXT/REFERENCE BOOKS:**

T/R	BOOK TITLE/AUTHORS/PUBLICATION
Т	A. Chakrabarti, Circuit Theory (Analysis and Synthesis). Fifth Edition : 2006, Dhanpat Rai and Co.
R	Parker Smith, Problems in Electrical Engineering. Ninth Edition :2003, M/s Constable and Company, London.
R	D.P. Kothari, I.J. Nagrath, Electrical Machines, Tata McGraw-Hill, 2004
R	N. Mohan, Electric Machines and Drives: A First Course, Wiley, 2012.

## **COURSE PRE-REQUISITES:**

C.CODE	COURSE NAME	DESCRIPTION	SEM
C115	Electrical Circuits	Electrical circuit theorems	II-I
C203 & C212	Electrical Machines-I & Electrical Machines-II	Speedcontrolmethods,CharacteristicsofGeneratorandInductionmotor,O.C & S.C testsofTransformers.	II-I & II- II

# **COURSE OBJECTIVES:**

1	To verify the Network Theorems.
2	To Control the Speed of the DC Motors & Induction Motor.
3	To Evaluate the Performance of DC Machines & Transformer.
4	To Obtain Equivalent circuit parameters of Induction Motor
5	To Assess the V & Inverted V Curves of Three Phase Synchronous Motor.

# **COURSE OUTCOMES:**

CO.NO	DESCRIPTION	PO(112) MAPPING	PSO(1,2) MAPPING
C329.1	Analyze Basic Network Theorems.	PO1,PO2,PO3,PO5,PO8,PO9,	PSO1.PSO2
		PO10,PO11,PO12.	1.001,1.002
C329.2	Analyze the performance and characteristics of DC Machines $\&$	PO1,PO2,PO3,PO5,PO8,PO9,	
	Transformer.	PO10,PO11,PO12.	PS01,PS02
C329.3	Determine the Equivalent circuit	PO1,PO2,PO3,PO5,PO8,PO9,	
	parameters of induction wotor.	PO10,PO11,PO12.	PSO1,PSO2
C329.4	Apply Speed control techniques of Induction Motor	PO1,PO2,PO3,PO5,PO8,PO9,	
	Induction Motor.	PO10,PO11,PO12.	PSO1,PSO2
C329.5	Apply the Knowledge of Synchronization to ensure safe	PO1,PO2,PO3,PO5,PO8,PO9,	PSO1,PSO2
	integration of synchronous		

machines and optimize the performance by adjusting excitation to achieve the desired power factor PO10,PO11,PO12.

COURSE OVERALL PO/PSO MAPPING: PO1,PO2,PO3,PO5,PO8,PO9,PO10,PO11,PO12, PSO1,PSO2

# COURSE OUTCOMES VS POs MAPPING (DETAILED; HIGH: 3; MEDIUM: 2; LOW: 1):

CO.NO	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12	PSO1	PSO2
C329.1	3	2	3	-	3	-	-	2	3	2	1	2	3	2
C329.2	3	2	3	-	3	-	-	2	3	2	1	2	3	2
C329.3	3	2	3	-	3	-	-	2	3	2	1	2	3	2
C329.4	3	2	3	-	3	-	-	2	3	1	1	2	3	2
C329.5	3	2	3	-	3	-	-	2	3	2	1	2	2	2
C329*	3	2	3	-	3	_	-	2	3	2	1	2	3	2

\* For Entire Course, PO & PSO Mapping

### **POs & PSO REFERENCE:**

PO1	Engineering Knowledge	PO7	Environment & Sustainability	PSO1	Capable of design, develop, test, verify and implement Electrical and Electronics Engineering systems and products.
PO2	Problem Analysis	PO8	Ethics	PSO2	Succeed in national and international competitive examinations for successful higher studies and employment.
PO3	Design & Development	PO9	Individual & Team Work		
PO4	Investigations	PO10	Communication Skills		
PO5	Modern Tools	PO11	Project Mgt. & Finance		
PO6	Engineer & Society	PO12	Life Long Learning		

# **COs VS POs MAPPING JUSTIFICATION:**

SNO	PO/PSO MAPPED	LEVEL OF MAPPING	JUSTIFICATION
			Understanding the Network theorems strongly required to
	PO1	3	enhance engineering knowledge by enabling efficient circuit
			design.
C320 1			Incorporating theorems into problem analysis involves
C329.1	PO2	2	identifying circuit elements and reducing them to their
			equivalent forms moderately.
			Analyzing basic network theorems is crucial in design and
	PO3	3	development because they simplify complex circuits,

			anabling afficient design validation and optimization of
			electrical systems highly
			Implementation of Network theorems with modern tools is
	PO5	3	highly required for precise simulations and visualizations of
	105	5	circuit behaviour
			The use of network theorems supports moderate learning for
	POG	2	practical application
	100		Analyzing basic network theorems is highly required for both
	POQ	3	individuals and teams work together better. It gives everyone
	109	5	a clear way to solve problems and communicate designs
			A palyzing basic naturals theorems slightly strengthens
	<b>DO10</b>	2	Analyzing basic network theorems slightly strengthens
	POIO	Z	communication skins by enabling engineers to clearly
			Slightly importe lifelong learning as it introduces engineering
	DO11	1	Sugnity impacts melong learning as it introduces engineering
	PUII	1	Analysis of naturaly theorems are superstated with 1.6
	DO10		Analysis of network theorems are somewhat required for
	PO12	2	Life long learning.
		2	Implementation of network theorems equips engineers with
	PSOI	3	essential skills to design, develop, test, verify in electrical
			and electronics systems.
	DCOO	2	Moderate importance for problem-solving and optimization
	PSO2	2	in electrical systems.
	PO1	3	analyzing the performance and characteristics of DC
			Machine & Transformer is strongly required to engineering
			knowledge
	PO2		Understanding key parameters like efficiency, torque, and
		2	voltage regulation, engineers can identify issues, optimize
			performance, and ensure reliability moderately in electrical
			systems.
	200	2	Evaluating the performance and characteristics of DC
C329.2	PO3	3	machines and transformers is Substantially required for
			design and development in engineering.
		_	Analyzing the performance and characteristics of DC
	PO5	3	machines and transformers using modern tools is
			Substantially required for accurate simulations and data
			visualization.
			Moderate requirement for practical application of
	PO6	2	performance analysis.
			Evaluating the performance and characteristics of DC
	PO9	3	machines and transformers are Substantially required to both

	1	1	
			individual and team work by encouraging collaboration in
			testing.
			Analyzing performance and characteristics of DC machines
	PO10	2	and transformers moderately strengthens communication
			skills by enabling engineers to clearly explain complex
			circuit concepts.
			Minimal impact on lifelong learning, though technical
	PO11	1	understanding contributes to broader skills.
			Analysis of performance and characteristics of DC machines
	PO12	2	and transformers are somewhat required for Life long
			learning.
			Implementation of performance and characteristics of DC
	PSO1	3	machines and transformers equips engineers with essential
			skills to design, develop, test, verify in electrical and
			electronics systems.
			Moderate role in addressing real-world problems in electrical
	PSO2	2	and electronics systems.
			Obtaining the equivalent circuit parameters of an induction
	PO1	3	motor is Substantially required for applying engineering
	101	5	knowledge effectively. It allows engineers to analyze motor
			nerformance design control systems and optimize
			efficiency
			Understanding the equivalent circuit parameters is
	PO2	2	moderately required for angineers can accurately diagnose
	102	2	noderatery required for engineers can accuratery diagnose
			solutions for orbansing officiancy and reliability in motor
			solutions for emancing efficiency and renability in motor
	DOG	2	Acquiring the equivalent circuit parameters of an induction
C329.3	PO3	3	motor is Substantially required for design and development.
		_	Using modern tools to obtain the equivalent circuit
	PO5	3	parameters of an induction motor enhances accuracy and
			efficiency.
			Moderate requirement for applying the knowledge in
	PO6	2	practical scenarios for real-world solutions.
			Function effectively as an individual and as member in a
	PO9	3	team for obtaining the equivalent circuit parameters of an
			induction motor.
			Equivalent circuit parameters of an induction motor improves
	PO10	2	communication skills slightly by necessitating clear
			explanations of technical details and results.
L	1	1	

·			
			Minimal contribution to lifelong learning but supports
	PO11	1	continued development in engineering practice.
			Equivalent circuit parameters of an induction motor are
	PO12	2	somewhat required for lifelong learning.
			Obtaining circuit parameters of an induction motor is
	PSO1	3	essential for engineers to design, develop, test, verify, and
			implement electrical and electronics systems effectively
			Moderate requirement for ensuring operational efficiency in
	PSO2	2	electrical systems.
			The Engineering knowledge is Substantially required for
	PO1	3	analysing the speed control techniques of motors.
	PO2	2	analysing the speed control of motors is moderately Problem
			analysis is required
			Speed control techniques for different motors are
	PO3	3	Substantially required for develop and design.
	PO5	3	speed control techniques enhances accuracy and efficiency
			Using modern tools is Substantially required
	PO6	2	Moderate requirement for practical knowledge application in
			motor control.
C220.4			Analysing the speed control techniques of motors Function
C329.4	PO9	3	effectively as an individual and as member in a team.
	PO10	1	Analyzing the speed control of motors is slightly strengthens
			communication skills by enabling engineers to clearly
			explain complex circuit concepts.
	PO11	1	understanding supports professional growth is slightly impact
			on lifelong learning, but the
	PO12	2	Analyzing of speed control methods of motor are somewhat
			required for lifelong learning.
	PSO1	3	Speed control of Motor is Substantially for engineers to
			design, develop, test, verify, and implement in electrical and
			electronics systems effectively
	PSO2	2	Supports optimization and efficiency in motor systems for
			electrical systems.
			Creating the V and inverted V curves of a three-phase
	PO1	3	synchronous motor is supported by engineering knowledge,
C220 5			as it requires analyzing how the motor performs under
C329.3			different loads and excitation levels.
			Develop the V & Inverted V Curves of Three Phase
	PO2	2	Synchronous Motor Problem analysis is moderately required
·			

EEV LAB

		Development of V & Inverted V Curves of Three Phase
PO3	3	Synchronous Motor are highly required for develop and
		design.
		Using modern tools is Highly required to develop the V &
PO5	3	Inverted V Curves of Three Phase Synchronous Motor
		enhances accuracy and efficiency.
		Moderate requirement for practical understanding and
PO6	2	application in engineering.
		Function effectively as an individual and as member in a
PO9	3	team in the development of V & Inverted V Curves of Three
		Phase Synchronous Motor.
		Analyzing the V & Inverted V Curves of Three Phase
PO10	2	Synchronous Motor slightly strengthens communication
		skills by enabling engineers to clearly explain complex
		circuit concepts.
		Slightly contributes to lifelong learning by extending
PO11	1	knowledge of motor characteristics.
		Analysis of V & Inverted V Curves of Three Phase
PO12	2	Synchronous Motor are somewhat required for lifelong
		learning.
		V & Inverted V Curves of Three Phase Synchronous Motor
PSO1	2	is moderately required for engineers to design, develop, test,
		verify, and implement in electrical and electronics systems
		effectively
		Supports real-world engineering problem-solving related to
PSO2	2	synchronous motor performance.

# WEB SOURCE REFERENCES:

1	https://www.vlab.co.in/broad-area-electrical-engineering
2	https://ems-iitr.vlabs.ac.in/

# DELIVERY/INSTRUCTIONAL METHODOLOGIES:

☑CHALK & TALK	□CT TOOLS	□WEB REFERENCES	□STUDENT SEMINARS
□NDUSTRIAL	□INTERNSHIPS	☑ EXPERIMENTAL	□MODEL-BASED
VISITS		LEARNING	LEARNING
□GUEST	☑ COLLABORATIVE	⊐MINI/MAJOR	□CASE STUDIES/REAL
LECTURES	LEARNING	PROJECTS	LIFE EXAMPLES

# ASSESSMENT METHODOLOGIES-DIRECT

□ ASSIGNMENTS	□ STUD. SEMINARS	☑ TESTS/MODEL	☑ END SEM EXAM
		EXAMS	
⊠STUD. LAB	🗹 STUD. VIVA	□ MINI/MAJOR	
PRACTICES		PROJECTS	CERTIFICATIONS
□ ADD-ON	□ OTHERS		
COURSES			

# ASSESSMENT METHODOLOGIES-INDIRECT

ASSESSMENT OF COURSE OUTCOMES	□ STUDENT FEEDBACK ON FACULTY				
(BY FEEDBACK, ONCE)	(TWICE)				
□ ASSESSMENT OF MINI/MAJOR	□ OTHERS				
PROJECTS BY EXT. EXPERTS					

Prepared by

Approved by PAC Member

Signature of HOD, EEE

Course Code	Course Title	Hrs./Week L: T: P	Credits
R20EEE-PC3205	Electrical Engineering Virtual Lab	0:0:3	1.5

#### **Course objectives:**

- To verify the Network Theorems.
- To Control the Speed of the DC Motors & Induction Motor.
- To Evaluate the Performance of DC Machines & Transformer.
- To Obtain Equivalent circuit parameters of Induction Motor
- To Assess the V & Inverted V Curves of Three Phase Synchronous Motor.

Course outcomes: At the end of this course, the students will be able to

- 1. Analyze Basic Network Theorems. (L4)
- 2. Analyze the performance and characteristics of DC Machines & Transformer. (L4)
- 3. Determine the Equivalent circuit parameters of Induction Motor. (L4)
- 4. Apply Speed control techniques of Induction Motor. (L3)
- 5. Apply the Knowledge of Synchronization to ensure safe integration of synchronous machines and optimize the performance by adjusting excitation to achieve the desired power factor (L3)

### All the Following Experiments are to be conducted:

- 1. Verification of Superposition Theorem.
- 2. Verification of Thevenin's Theorem.
- 3. Verification and Norton's Theorem.
- 4. Magnetization characteristics of DC Shunt Generator. Determination of Critical Field. Resistance and Critical Speed.
- 5. Load test on DC Shunt Generator.
- 6. Speed control of DC Shunt motor by Field and Armature Control.
- 7. Equivalent circuit of Three Phase Induction Motor.
- 8. Speed control of Slip ring Induction Motor.
- 9. OC & SC Test on Single Phase Transformer.
- 10. V and Inverted V curves of a Three Phase Synchronous Motor.

# **LIST OF EXPERIMENTS (Performed in the Laboratory)**

- 1. Verification of Superposition Theorem
- 2. Verification of Thevenin's Theorem.
- 3. Verification and Norton's Theorem.
- Magnetization characteristics of DC Shunt Generator. Determination of Critical Field Resistance and Critical Speed.
- 5. Load test on DC Shunt Generator.
- 6. Speed control of DC Shunt motor by Field and Armature Control.
- 7. Equivalent circuit of Three Phase Induction Motor.
- 8. Speed control of Slip ring Induction Motor.
- 9. OC & SC Test on Single Phase Transformer.
- 10. V and Inverted V curves of a Three Phase Synchronous Motor.

# **ADDITIONAL EXPERIMENTS**

- 11. Verification of Maximum Power Transfer Theorem
- 12. Synchronization of Alternator With Infinite busbar

# **INDEX**

S.NO	Title of the Experiment	CO	РО	Page No
1	Verification of Superposition		PO1,PO2,PO3,PO5,PO8,PO9,	
1	Theorem.	CO1	PO10,PO11,PO12.PSO1,PSO2	1-4
	Varification of Theyanin's Theorem	CO1	PO1 PO2 PO3 PO5 PO8 PO9	
2	vermeation of Thevenin's Theorem.	001	PO10.PO11.PO12.PSO1.PSO2	
				5-9
2	Verification and Norton's Theorem.		PO1,PO2,PO3,PO5,PO8,PO9,	
3		CO1	PO10,PO11,PO12.PSO1,PSO2	10-13
	Magnetization characteristics of DC		PO1.PO2.PO3.PO5.PO8.PO9.	
	Shunt Generator Determination of	CO2	PO10,PO11,PO12.PSO1,PSO2	1/ 10
4	Critical Field Pasistance and Critical	02		14-18
	Speed			
	Lood test on DC Shunt Consisten			
5	Load test on DC Shunt Generator.		PO10.PO11.PO12.PSO1.PSO2	
		CO2		19-23
_	Speed control of DC Shunt motor		PO1,PO2,PO3,PO5,PO8,PO9,	
6	by Field and Armature Control.	CO2	PO10,PO11,PO12.PSO1,PSO2	24-31
			DO1 DO2 DO2 DO5 DO8 DO0	-
7	Equivalent circuit of Three Phase		PO1, PO2, PO3, PO3, PO8, PO9, PO10 PO11 PO12 PSO1 PSO2	
	Induction Motor.	CO3	1010,1011,1012.1001,1002	32-40
0	Speed control of Slip ring Induction		PO1,PO2,PO3,PO5,PO8,PO9,	
8	Motor.	CO4	PO10,PO11,PO12.PSO1,PSO2	41-44
			DO1 DO2 DO2 DO5 DO9 DO9	
9	OC & SC Test on Single Phase		PO1,PO2,PO3,PO5,PO8,PO9, PO10 PO11 PO12 PSO1 PSO2	
	Transformer.	CO2	r010,r011,r012.r501,r502	45-50
	V and Inverted V curves of a Three		PO1,PO2,PO3,PO5,PO8,PO9,	
10	Phase Synchronous Motor.	CO5	PO10,PO11,PO12.PSO1,PSO2	51-55
		0.05		51-55
	ADDITION	AL EX	PERIMENTS	
11	Verification Of Maximum Power		PO10 PO11 PO12 PSO1 PSO2	
	Transfer Theorem	CO1	r010,r011,r012.r501,r502	56-60
	Synchronization of Alternator With		PO1,PO2,PO3,PO5,PO8,PO9,	
12	Infinite busbar	CO5	PO10,PO11,PO12.PSO1,PSO2	61-66
				01 00

# 1. VERIFICATION OF SUPERPOSITION THEOREM

# <u>AIM:-</u>

To Verify Superposition Theorem.

# THEORY:-

If a number of voltage or current source are acting simultaneously in a linear network, the Resultant current in any branch is the algebraic sum of the currents that would be produced in it, when each source acts alone replacing all other independent sources by their internal resistances.



Fig.1 : Circuit for analysis of Superposition theorem



# Fig.2 : Circuit with only V<sub>2</sub> short circuited

In given figure 1 apply superposition theorem , let us first take the sources  $V_1$  alone at first replacing  $V_2$  by short circuit as shown in figure 2.Here,

$$I_{1'} = \frac{V_1}{\frac{R_2 * R_3}{R_2 + R_3} + R_1}$$
$$I_{2'} = I_{1'} * \frac{R_3}{R_2 + R_3}$$
$$I_{3'} = I_{1'} - I_{2'}$$





Next, removing  $V_1$  by short circuit, let the circuit be energized by  $V_2$  only as shown in figure 3. Then,

$$I_{2''} = \frac{V_2}{\frac{R_2 * R_3}{R_2 + R_3} + R_2}$$
$$I_{1''} = I_{2''} * \frac{R_3}{R_1 + R_3}$$
$$I_{3''} = I_{2''} - I_{1''}$$

As per superposition theorem,

$$I_{3} = I_{3'} + I_{3''}$$
$$I_{2} = I_{2'} - I_{2''}$$
$$I_{1} = I_{1'} - I_{1''}$$

# **CIRCUIT DIAGRAM:-**



Fig.1 : Circuit diagram of experimental set-up for verification of Superposition theorem

### PROCEDURE:-

- 1. Connect the circuit as shown in the diagram, keeping the switches open and resistance at their maximum positions.
- 2. Set S<sub>1</sub> to position "aa" and S<sub>2</sub> to position "cc" respectively which means both the sources are energized. Note down the current I<sub>1</sub>, I<sub>2</sub> and I<sub>3</sub> from ammeter A<sub>1</sub>, A<sub>2</sub> and A<sub>3</sub>.
- Set S<sub>1</sub> to positions "aa" and S<sub>2</sub> to position "dd" respectively which means the, only 220V source is energized and the terminals of S<sub>2</sub> are shorted. Note down current I<sub>1</sub>', I<sub>2</sub>' and I<sub>3</sub>'from the ammeter A<sub>1</sub>, A<sub>2</sub> and A<sub>3</sub>.
- Set S<sub>1</sub> to position "bb" and S<sub>2</sub> to position to "cc" respectively. Which means the, only 110V source is energized and the terminals of S<sub>1</sub> are shorted. Note down current I<sub>1</sub>", I<sub>2</sub>" and I<sub>3</sub>" from the ammeter A1, A2 and A3.
- 5. Compare I<sub>1</sub>, I<sub>2</sub> and I<sub>3</sub> with I<sub>1</sub>+I<sub>1</sub>", I<sub>2</sub>+I<sub>2</sub>" and I<sub>3</sub>+I<sub>3</sub>" taking care of signs properly of verify the theorem.

6. Repeat the step (2) to (6) for five different values of resistance for each three rheostats.

Social no. of	In pr	resence of both V <sub>1</sub> an	id V <sub>2</sub>		n presence of V <sub>1</sub> onl	у	In presence of V <sub>2</sub> only			
Observation	Brach current I <sub>1</sub> (in amps)	Brach current I <sub>2</sub> (in amps)	Brach current I <sub>3</sub> (in amps)	Brach current I <sub>1</sub> (in amps)	Brach current I <sub>2</sub> (in amps)	Brach current I <sub>3</sub> (in amps)	Brach current I <sub>1</sub> (in amps)	Brach current I <sub>2</sub> (in amps)	Brach current I <sub>3</sub> (in amps)	
1st	0.42308	-0.084615	0.33846	0.59231	-0.33846	0.25385	-0.16923	0.25385	0.084615	
2nd	0.57037	-0.12222	0.44815	0.81481	-0.48889	0.32593	-0.24444	0.36667	0.12222	
3rd	0.47143	-0.15714	0.31429	0.78571	-0.62857	0.15714	-0.31429	0.47143	0.15714	
4th	0.82500	-0.13750	0.68750	1.1000	-0.55000	0.55000	-0.27500	0.41250	0.13750	
5th	1.1000	0.0000	1.1000	1.3200	-0.44000	0.88000	-0.22000	0.44000	0.22000	

### **OBSERVATION TABLE:-**

**<u>RESULT</u>:-** Hence Verified the Superposition Theorem and Note down the observation values Virtually

**<u>OUTCOME</u>**: By doing this Experiment CO1 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 2. VERIFICATION OF THEVENIN'S THEOREM

# <u>AIM :-</u>

To Verify Thevenin's Theorem.

# THEORY:-

Its provides a mathematical technique for replacing a given network, as viewed from two terminals, by a single voltage source with a series resistance. It makes the solution of complicated networks quite quick and easy. The application of this extremly useful theorem will be explained with the help of following simple example.



Fig.1 : Circuit with source E and Load  $R_L$ 

Suppose, it is required to find current flowing through load resistance R<sub>L</sub>, as shown in figure 1.

This expression proceed as under:

1) Remove R<sub>L</sub> from the circuit terminals A and B and redraw the circuit as shown in figure

2. Obviously, the terminal have become open circuited.



#### Fig.2 : Circuit with R<sub>L</sub> removed

2) Calculate the open circuit Voltages  $V_{O.C.}$  which appears across terminals A and B when they are open .ie. when  $R_L$  is removed.

As seen,  $V_{.O.C.}$  = drop across  $R_2$  = IR<sub>2</sub> where I is the circuit current when A and B is open.

$$I = \frac{E}{r + R_1 + R_2}$$
$$V_{o.c.} = I * R_1$$
$$V_{o.c.} = \frac{E * R_2}{r + R_1 + R_2}$$

It is also called Thevenin voltage( $V_{th}$ ).

3) Now, imagine the battery to be removed from the circuit, leaving its internal resistance r behind and redraw the circuit as shown in figure 3.



Fig.3 : Circuit with R<sub>L</sub> and E removed

When viewed inwards from the terminals A and B, the circuit consists of two parallel paths: one containing  $R_2$  and another containing ( $R_1$ +r). The equivalent resistance of the network as viewed from these terminals is given as,

$$R_{th} = \frac{(R_1 + r) * R_2}{R_1 + r + R_2}$$

The resistance "R<sub>th</sub>" is also called Thevenin equivalent resistance.

Consequently , as viewed from terminals A and B, the whole network (excluding  $R_1$ ) can be reduced to single source (called thevenin's source) whose e.m.f equal to  $V_{O.C.}$  and whose internal reistance equal to  $R_{th}$  as shown in figure 4.

4)  $R_L$  is now connected back across terminals A and B from where it was temporally removed earlier. Current flowing through  $R_L$  is given by,

$$I_1 = \frac{V_{th}}{R_{th} + R_L}$$



Fig.4 : Thevenin's equivalent circuit

**PROCEDURE:**-



#### [Fig 1: Circuit diagram for Experimental set-up for verification of Thevenin's theorem]

1) Keep all the resistance close to their maximum respective values.

2) Close the switch  $S_1$  to "aa" and  $S_2$  to "cc" positions. Observe the load current ( $I_L$ ) and voltage ( $V_L$ ) readings. The load resistance

$$R_L = \frac{V_L}{I_L}$$

3) Remove the load by opening the switch  $S_2$  and read the open circuit voltage (or Thevenin equivalent voltage)  $V_{th}$ .

4) Next, compute the resistance (R<sub>TH</sub>) of the network as seen from the load terminals,

a) Replace the 220 V source by a short by closing  $S_1$  to "bb".

b) Apply 110 V at the output terminals by closing  $S_2$  to "dd". Read the voltmeter (V) and ammeter (I) and get

$$R_{th} = \frac{V}{I}$$

5) Now compute the load current. Applying Thevenin theorem

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

6) Compare the above computed load current with its observed value in step (2) and verify the theorem.

#### **OBSERVATION TABLE:-**

Serial no. of Observation	Load Current(I <sub>L</sub> ) from case 1	Load Voltage(VL)	Load Resistance (RL)=VL/IL	Thevenin Voltage(V <sub>th</sub> ) from case 2(a)	2nd Voltage source(v) for case 2(b)	Ammeter Reading(I) from case 2(b)	Thevenin Resistance R <sub>th</sub> =V/I	Load current $(I_L)=V_{th}/(R_{th}+R_L)$
1st	0.12941	38.823	300	73.333	220	0.82500	266.67	0.12941
2nd	0.12941	25.88199995	200	73.333	220	0.60000	366.67	0.12941
3rd	0.078571	15.7142	200	88.000	110	0.30556	359.99	0.15715
4th	0.31429	62.85800000	200	110.00	110	0.73333	150.00	0.31429
5th	0.15714	31.428	200	55.000	220	1.4667	150.00	0.15714

EEV LAB

LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY

Page 8

**<u>RESULT</u>:-** Hence Verified The Thevenin's Theorem And Note down The Observation Values Virtually

**OUTCOME:-** By doing this Experiment CO1 and PO1,PO2,PO3,PO5,PO8,PO9, PO10,PO11,PO12.PSO1,PSO2 are Attained

# 3. VERIFICATION OF NORTON'S THEOREM

#### <u>AIM :-</u>

To Verify Norton Theorem.

#### **THEORY:-**

A linear active network consisting of independent and(or) dependent voltage and current sources and linear bilateral network elements can be replaced by an equivalent circuit consisting of current sources in parallel with the resistance, the current source being the short circuited current across the load terminal and resistance being the internal resistance of the source network looking through the open circuited load terminals. In order to find the current through  $R_L$ , the load resistance of the figure 1 by Norton's theorem, let,replace  $R_L$  by short circuit as shown in figure 2.



[Fig 1: Circuit with source V<sub>S</sub> and Load R<sub>L</sub>]



### [Fig 2: Circuit with R<sub>L</sub> shorted]

Obviously, in Fig 2;

$$I = \frac{V_s}{R_1 + \frac{R_2 * R_3}{R_2 + R_3}}$$

$$I_{s/c} = I \frac{R_3}{R_3 + R_2}$$

Next, the short circuit is removed and the independent source is deactivated as shown in figure 3.



[Fig 3: Circuit with source V<sub>s</sub> deactivated and Load R<sub>L</sub> open]

From Fig 3;

$$R_{int} = R_2 + \frac{R_1 * R_3}{R_1 + R_3}$$

As per Norton's theorem, the equivalent circuit as shown in figure 4, would contain a current source in parallel to the internal resistance, the current source being the short circuited current across the shorted terminals of the load resistor.





Obviously, from Fig 4;

$$I_L = I_{s/c} \frac{R_{int}}{R_{int} + R_L}$$





# [Fig 1: Circuit diagram for Experimental set up]

- 1. Keep all the resistance close to their maximum respective values.
- 2. Close the switchs<sub>1</sub>to "aa" ands<sub>2</sub>to "cc" positions .Observes the load current I<sub>L</sub>and voltage  $V_L$ readings. The load resistance  $R_L = V_L / I_L$
- 3. Short the load terminals and find the short circuited current  $I_{sc}$ .
- 4. Next, compute the resistance R<sub>int</sub> of the network as seen from the load terminals,
  - Replace the 220 V source by a short by closing s<sub>1</sub> to "bb".
  - Apply V=110 V at the output terminals by closing  $s_2$  to "dd". Read the current from ammeter (I) and get  $R_{int} = V/I$
- 5. Now compute the load current  $I_L$  applying Norton theorem.

$$I_L = I_{sc} \frac{R_{int}}{(R_{int} + R_L)}$$

6. Compare the above computed load current with its observed value in step (2) and verify the theorem.

Serial no. of Observation	Load Current(I <sub>L</sub> ) from case 1	Load Voltage(V <sub>L</sub> )	Load Resistance (R <sub>L</sub> )=V <sub>L</sub> /I <sub>L</sub>	Norton current(I <sub>sc</sub> ) from case 2(a)	2nd Voltage source(v) from case 2(b)	Ammeter Reading(I) from case 2(b)	Norton Resistance R <sub>n</sub> =V/I	Load current $(I_L)=I_{sc}*R_n/(R_n*R_L)$
1st	0.28387	85.161	300	0.67692	110	0.50769	216.67	0.28387
2nd	0.25882	77.646	300	0.67692	110	0.59231	185.71	0.25882
3rd	0.15714	47.142	300	0.44000	220	1.3200	166.67	0.15714
4th	0.20000	40.000	200	0.44000	220	1.3200	166.67	0.20000
5th	0.22000	22.000	100	0.36667	220	1.4667	150.00	0.22000

#### **OBSERVATION TABLE:-**

**<u>RESULT</u>:-** Hence Verified The Norton's Theorem And Note down The Observation Values Virtually

**<u>OUTCOME</u>:-** By doing this Experiment CO1 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained.

# 4. <u>MAGNETIZATION CHARACTERISTICS OF DC SHUNT</u> <u>GENERATOR. DETERMINATION OF CRITICAL FIELD</u> <u>RESISTANCE AND CRITICAL SPEED</u>

<u>**AIM:-**</u>To study the magnetisation characteristics of DC Shunt Generator. Draw the graph between the armature voltage and field current.

#### **THEORY:-**

A DC generator, whose schematic equivalent circuit is shown in figure 1, is an electrical machine that converts the mechanical energy of a prime mover (e.g. DC motor, AC induction motor or a turbine) into direct electrical energy. The generator shown in figure 1 is self-exciting. It uses the voltage Ea generated by the machine to establish the field current  $I_f$ , which in turn gives rise to the magnetic-field flux  $\Phi$ . When the armature winding rotates in this magnetic field to cut the flux, the voltage Ea is induced in the armature. This voltage is commonly referred to as the armature electromotive force or EMF. The induced EMF is proportional to the rate of cutting the flux and is given by emf formula.

$$E=\frac{P\emptyset NZ}{60A}$$

where,

 $\Phi =$  flux in webers

N = armature speed in rpm

Z = total number of armature conductors

P = number of poles

A = number of parallel paths



### **Equivalent circuit of DC Shunt Generator**

The magnetic field necessary for generator action may be provided by

(a) permanent magnets,

(b) (b) electromagnets receiving their exciting current from an external source, and

(C) electromagnets being excited from the current obtained from the generator itself.

The use of permanent magnets is confined to very small generators. The electromagnetic excitations listed in (b) and (c) above give rise to generators having somewhat different types of characteristics.

In the case of a compound generator, the series and shunt fields may be connected so as to aid each other, i.e., the fluxes set up by each will add up.

An increase in the total flux will generate a greater EMF. Such a connection is known as cumulative. If, however, the shunt and series windings are so connected that the flux set up by one opposes the other, then the induced EMF will be smaller. This type of connection is called differential.

### **<u>Critical Field Resistance:</u>**

It is that value of the field resistance at which the D.C. Shunt Generator will fail to excite. It is that speed for which the given shunt field resistance becomes the critical field resistance. Critical field resistance is obtained by plotting the OCC as in fig.2 and determining the slope of the tangent to the linear position of the curve from the origin. While drawing the tangent, the initial position of the O.C.C is neglected.

Due to residual magnetism in the poles, a small amount of EMF is generated even when  $I_f = 0$ . Hence, the curve starts a little way up. The slight curvature at the lower end is due to magnetic inertia. It has seen that the first part of the curve is practically straight. Hence the flux and consequently generated EMF is directly proportional to the exciting current. However at the higher flux densities where it is small iron path reluctance becomes appreciable and straight. Field windings are connected parallel to the armature, so it is called DC Shunt Generator. Due to residual magnetism some initial emf and hence some current will be generated. This current while passing into the field coils will strengthen the magnetism of poles. This will increase pole flux which will further increase the generated emf. Increased emf and flux proceeds till equilibrium reached at some point in the graph between  $I_f$  and  $E_g^*$ 



Fig. 2 Magnetisation characteristics of DC Shunt Generator

# **CIRCUIT DIAGRAM:-**

From	R	В	В	В	F	A	Н	C	D	E	G
То	L	Н	A2	F2	I	Aı	F1	A3	A4	F3	F4

**STEP 1:** Make connections as per the instructions given below:



#### PROCEDURE:-

# NOTE: If wire is wrongly connected, Click on node number to detach the wire.

**STEP 2:** Click on Check button for checking the connections.

**STEP 3:** Click on MCB to turn on the supply.

**STEP 4:** Now, move the slider on the rheostat to take observations from Voltmeter and Ammeter.

**STEP 5:** Click on Add to Table button to add values to the observation table.

**STEP 6:** Repeat steps 4 to 5 to add more values in the table.

**STEP 7:** Click on Graph button to make a respective graph regarding the values in the table.

**STEP 8:** Click on Print button to print the webpage.

**STEP 9:** Click on Reset button to reset the webpage.

### **OBSERVATION TABLE:**

S.No.	Voltage (V)	Current (A)
1	0	0
2	115	0.16
3	120	0.18
4	126	0.20
5	129	0.21
6	133	0.23
7	138	0.28
8	142	0.30

# GRAPH:-



**RESULT:** Hence studied the Magnitization Characteristics of DC Shunt Generator & Draw

the graph between the Armature voltage and Field current Virtually

**<u>OUTCOME</u>:-** By doing this Experiment CO2 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 5. LOAD TEST ON DC SHUNT GENERATOR

AIM:- To study the load characteristics of DC Shunt Generator. Draw the internal characteristics and external characteristics under different loading condition.

# THEORY:-

In a shunt generator, the field winding is connected in parallel with the armature winding so that terminal voltage of the generator is applied across it. The shunt field winding has many turns of fine wire having high resistance. Therefore, only a part of armature current flows through shunt field winding and the rest flows through the load. Figure shows the connections of a shunt wound generator. The armature current I<sub>a</sub> splits up into two parts- a small fraction I<sub>sh</sub> flowing through shunt field winding while the major part I<sub>L</sub> goes to the external load.



Shunt Wound Generator

Fig. 1 Equivalent circuit of DC shunt generator for load characteristics

### **Internal characteristic**

The internal characteristic curve represents the relation between the generated voltage Eg and the load current IL. When the generator is loaded then the generated voltage is decreased due to
armature reaction. So, generated voltage will be lower than the emf generated at no load. Here in the figure below AD curve is showing the no load voltage curve and AB is the internal characteristic curve.

#### **External or Load characteristic**

AC curve is showing the external characteristic of the shunt wound DC generators. It is showing the variation of terminal voltage with the load current. Ohmic drop due to armature resistance gives lesser terminal voltage the generated voltage. That is why the curve lies below the internal characteristic curve.

## $\mathbf{V} = (\mathbf{E}_g - \mathbf{I}_a \ \mathbf{R}_a) = \mathbf{E}_g - (\mathbf{I}_L + \mathbf{I}_{sh})\mathbf{R}_a$

The terminal voltage can always be maintained constant by adjusting the load terminal. External characteristics of shunt dc generator When the load resistance of a shunt-wound DC generator is decreased, then load current of the generator increased as shown in above figure. But the load current can be increased to a certain limit with (up to point C) the decrease of load resistance. Beyond this point, it shows a reversal in the characteristic. Any decrease of load resistance results in current reduction and consequently, the external characteristic curve turns back as shown in the dotted line, and ultimately the terminal voltage becomes zero. Though there is some voltage due to residual magnetism. We know, Terminal voltage Now, when IL increased, then terminal voltage decreased. After a certain limit, due to heavy load current and increased ohmic drop, the terminal voltage is reduced drastically. This drastic reduction of terminal voltage across the load results the drop in the load current although at that time load is high or load resistance is low. That is why the load resistance of the machine must be maintained properly. The point in which the machine gives maximum current output is called breakdown point (point C in the figure).



Fig. 2 Load characteristics of DC shunt generator

Note - It may be seen from the external characteristic that change in terminal voltage from noload to full load is small. The terminal voltage can always be maintained constant by adjusting the field rheostat R automatically.

# **CIRCUIT DIAGRAM:-**

From	R	R	В	В	A2	L	F	А	L2	A4	Z4	I	J	Н	Н
То	С	Е	G	A2	Z2	D	Z1	Aı	A4	Z4	K	J	L1	A3	Z3



LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY

## PROCEDURE:-

**STEP 1:** Make Connections as per the instructions

STEP 2: Click on "Check" Button for checking the connections.

**STEP 3:** If connections is correct, MCB will be turned ON.

**STEP 4:** Select the No. of Bulbs from the Lamp load.

STEP 5: Click on "Add" Button to add the values to the Observation Table.

**STEP 6:** Add different values to the Table by increasing the lamp load.

**STEP 7:** Click on **''Graph''** Button to Create Graph.

**STEP 8:** Click on **"Print"** Button to print the webpage.

**STEP 9:** Click on **"Reset"** Button to reset the webpage.

#### **OBSERVATION TABLE:-**

S.No.	Current (A)	Voltage (V)
1	3.6	205
2	5.5	200
3	7	195
4	8.1	189
5	10.2	184
6	11	179

# Graph:-



**<u>RESULT</u>**:- Hence Studied the Load characteristics of DC shunt generator & Draw the internal &

External characteristics under different load conditions virtually.

**<u>OUTCOME:</u>** By doing this Experiment CO2 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 6. <u>SPEED CONTROL OF DC SHUNT MOTOR BY FIELD AND</u> <u>ARMATURE CONTROL</u>

# (A).Speed Control of DC motor by Armature Resistance Control

<u>AIM:-</u> To study the speed control of D.C. Shunt motor by armature control method. Draw the graph between armature voltage and motor speed by varying the armature voltage. THEORY:-

We know that the speed of DC motor is given by:

 $N = \frac{V-I_aR_a}{k\Phi}$ 

The above equation shows that the speed depends upon the supply voltage V, the armature circuit resistance Ra, and the field flux  $\Phi$ , which is produced by the field current. In practice, the variation of these three factors is used for speed control. Thus, there are three general methods of speed control of D.C. Motors.

- 1. Resistance variation in the armature circuit. This method is called armature resistance control or Rheostat control.
- 2. Variation of field flux  $\Phi$ . This method is called field flux control.
- 3. Variation of the applied voltage. This method is also called armature voltage control.



Equivalent circuit for armature control of DC motor

#### Speed control by varying armature\_resistance:

In this method a variable series resistor  $R_{ext}$  is put in the armature circuit. In this case the field is directly connected across the supply and therefore the flux  $\phi$  is not affected by variation of  $R_{ext}$ . in this case the current and hence the flux are affected by the variation of the armature circuit resistance. The voltage drop in  $R_{ext}$  reduces the voltage applied to the armature and therefore the speed is reducing.

The slope of the n vs.  $I_a$  or n vs. Te characteristic can be modified by deliberately connecting external resistance rext in the armature circuit. One can get a family of speed vs. armature curves for various values of  $r_{ext}$ . From these characteristics it can be explained how speed control is achieved. Let us assume that the load torque  $T_L$  is constant and field current is also kept constant.

Therefore, since steady state operation demands  $T_e = T_L$ ,  $T_e = k_{\phi}$  too will remain constant; which means  $I_a$  will not change. Suppose  $r_{ext} = 0$ , then at rated load torque, operating point will be at C and motor speed will be n. If additional resistance  $r_{ext1}$  is introduced in the armature circuit, new steady state operating speed will be n1 corresponding to the operating point D. In this way one can get a speed of n2 corresponding to the operating point E, when  $r_{ext2}$  is introduced in the armature circuit. This same load torque is supplied at various speed. Variation of the speed is smooth and speed will decrease smoothly if rext is increased. Obviously, this method is suitable for controlling speed below the base speed and for supplying constant rated load torque which ensures rated armature current always. Although, this method provides smooth wide range speed control (from base speed down to zero speed), has a serious draw back since energy loss takes place in the external resistance rext reducing the efficiency of the motor.



**Armature Current la** 

#### Armature current speed characteristics of DC motors

## PROCEDURE:-

STEP 1: Make connections as per the instructions given below:

From	R	В	В	В	F	А	G	I	С	A1	К
То	L	D	A2	F2	Е	J	Η	F1	A1	к	С



NOTE: If wire is wrongly connected, Click on node number to detach the wire.

STEP 2: Click on Check button for checking the connections.

**STEP 3:** Click on MCB to turn on the supply.

**STEP 4:** Now, move the second slider to get corresponding values of Voltmeter and Speedometer.

**STEP 5:** Click on Add to Table button to add values to the observation table.

**STEP 6:** Repeat steps 4 to 5 to add more values in table.

**STEP 7:** Click on Graph button to make a respective graph regarding the values in table.

**STEP 8:** Click on Print button to print the webpage.

EEV LAB LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY

**STEP 9:** Click on Reset button to reset the webpage.

S.No.	Voltage (V)	Speed (RPM)
1	220	1360
2	200	1190
3	180	1080
4	160	950
5	140	825
6	120	690

# **OBSERVATION TABLE:-**

## **GRAPH:-**





and Draws the graph between Voltage and motor speed by varying the Armature voltage

**<u>OUTCOME</u>:-** By doing this Experiment CO2 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 6(B). Speed Control of DC motor by field resistance control

**<u>AIM</u>**: To study the speed control of DC Motor by field resistance Control. Draw the graph between the armature current and motor speed by varying the field resistance. **<u>THEORY:</u>** We know that the speed of shunt motor is given by:

$$N = (V_a - I_a R_a)/k\Phi$$

Where,  $V_a$  is the voltage applied across the armature and  $\phi$  is the flux per pole and is proportional to the field current I<sub>f</sub>. As explained earlier, armature current I<sub>a</sub> is decided by the mechanical load present on the shaft. Therefore, by varying  $V_a$  and If we can vary n. For fixed supply voltage and the motor connected as shunt we can vary  $V_a$  by controlling an external resistance connected in series with the armature. I<sub>f</sub> of course can be varied by controlling external field resistance R<sub>f</sub> connected with the field circuit.

Thus for shunt motor we have essentially two methods for controlling speed, namely by:

- 1. Varying armature resistance.
- 2. Varying field resistance.



Speed control by varying field current:

In this method field circuit resistance is varied to control the speed of a d.c shunt motor. Let us rewrite the basic equation to understand the method.

$$N = (V_a - I_a R_a)/k\Phi$$

If we vary  $I_f$ , flux  $\varphi$  will change, hence speed will vary. To change  $I_f$  an external resistance is connected in series with the field windings. The resistance is called the shunt field regulator the field coil produces rated flux when no external resistance is connected and rated voltage is applied across field coil. It should be understood that we can only decrease flux from its rated value by adding external resistance. Thus the speed of the motor will rise as we decrease the field current and speed control above the base speed will be achieved. Speed versus armature current characteristic is shown below.



Fig. 2 Torque speed characteristics of DC motors

## **Procedure:**

STEP 1: Make connections as per the instructions given below:



**STEP 2:** Then Check the connections by clicking on "Check" Button.

**STEP 3:** If it shows alert **"Incorrect Corrections"** then click on node number to detach the wire or press reset button and make connection again.

**STEP 4:** If it shows alert "Correct Connections" then Turn On the MCB.

**STEP 5:** Then set the Voltmeter first with the help of the second slider.

STEP 6: Now, move the first slider to get corresponding values of Ammeter and Speedometer.

**STEP 7:** Press the "Add to table" button to insert the values in the table.

STEP 8: After inserting values on table click on "Plot graph" to get your required graph.

**STEP 9:** Click on **"Print"** button to print the webpage.

**STEP 10:** Click on "**Reset**" button to reset the webpage.

## **OBSERVATION TABLE:-**

S.No.	Current (A)	Speed (RPM)
1	0.1	2500
2	0.2	2340
3	0.3	2100
4	0.4	1930
5	0.5	1700
6	0.6	1575

## GRAPH:-



LENDI INSTITUTE OF ENGINEERING AND TECHNOLOGY

**<u>RESULT</u>:-** Hence the speed control of DC Motor by Field control method Verified. And draws field resistance and Armature current virtually.

**<u>OUTCOME:</u>** By doing this Experiment CO2 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 7. <u>EQUIVALENT CIRCUIT OF THREE PHASE INDUCTION</u> <u>MOTOR.</u>

# 7(A).No load test on three phase induction motor

Aim: To Study No Load Test on Three Phase Induction Motor

## Theory:

A large percentage of the electrical power generated in the world is consumed by induction motors, as these are the main drive motors used in the industries. Practicing engineers should be conversant with the performance characteristics. Equivalent circuit parameters of the machine should be known for predicting the performance. While motor designer calculates the parameters using design details, measured values are preferable for prediction.

The steady-state performance of a poly-phase induction motor can be obtained using per phase equivalent circuit.

The symbols are,

- V1 = input voltage per Phase
- R1,X1 = resistance and leakage reactance of the stator per phase
- R2,X2 = resistance and leakage reactance of the rotor per phase
- Xm= magnetizing reactance
- Rc= core loss resistance
- I1, I2 = stator and rotor currents (referred to stator) per phase.

The developed torque is given as,  $T=3(I2)2R2/(s\omega s)$  N-m

Where,

- $\omega s = synchronous speed in radians/sec$
- $\omega r = rotor speed in radians/sec$
- s = slip.

The parameters could be determined by 'no-load' and 'blocked-rotor' tests, the former determines Rc and Xm while the latter yields R1, R2, X1, X2. Following equations could be used

- X1 = R1 + jX1
- X2 = R2/S + jX2
- $S = \omega s \omega r / \omega$

- The Torque T = 3(I2)2R2/s
- Input power = 3V1II pf
- Output power =  $(1-S) \omega s$



Per phase equivalent circuit of a poly phase induction motor

Start the motor by applying the normal frequency reduced voltage to the stator and gradually increases the voltage to its rated value under no load condition. In case of slip-ring motor short circuit the slip rings before starting. Note down the readings of voltmeter, ammeter, wattmeters and tachometer at different voltages.

# PROCEDURE:-

- 1. NO load is connected to Induction motor so as to carry out NO load test on induction motor.
- 2. Close the TPST (Triple Pole Single Throw) switch connecting three phase mains supply to induction motor.
- 3. Start the motor by applying reduced voltage to the stator.
- 4. Gradually increases the voltage to its rated value.
- 5. Now increase the voltage by clicking the arrows on three phase variac



6. As we go on increasing the supply voltage we can observe the change in speed of motor in digital tachometer.



- 7. Observe the readings of voltmeter, ammeter, wattmeters and tachometer at various stator input voltages.
- 8. Store the data by clicking "Start Storing Data" at various i/p voltages
- 9. Go on repeating this procedure till sufficient readings are stored.
- 10. Now display the data by clicking "Show data". It will display data as shown.
- 11. Now select one of the graph from available graphs and use "Generate graph" to plot the graph .For Ex.



12. While switching off, gradually decrease the voltage applied to motor and make it zero.

13. Open the TPST switch.



# **OBSERVATION TABLE:-**

V <sub>S</sub> (Volt)	I <sub>L</sub> (Amp)	W-1 (Watt)	W-2 (Watt)	Speed (r.p.m)	Total copper loss	Rotor angle	i/p Power
414.00	3.40	-24.27	904.79	1494.00	125.30	79.8	431.74
450.00	3.72	-580.77	1076.03	1495.00	376.36	80.3	488.53
480.00	4.00	-31.54	1234.15	1495.00	173.22	80.3	560.32
490.00	4.05	-688.49	1275.61	1495.00	446.20	80.3	579.14
500.00	4.13	-716.42	1327.36	1495.00	464.35	80.3	602.63

# GRAPH:-



**<u>RESULT:-</u>** Hence The test verifies that the motor is functioning correctly under no load conditions Virtually

**<u>OUTCOME:-</u>** By doing this Experiment CO3 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 7(B).Blocked Rotor test on three phase induction motor

AIM:- Study blocked rotor test on induction motor

# THEORY:-

A large percentage of the electrical power generated in the world is consumed by induction motors, as these are the main drive motors used in the industries. Practicing engineers should be conversant with the performance characteristics. Equivalent circuit parameters of the machine should be known for predicting the performance. While motor designer calculates the parameters using design details, measured values are preferable for prediction.

The steady-state performance of a poly-phase induction motor can be obtained using per phase equivalent circuit. The symbols are,

- V1 = input voltage per Phase
- R1,X1 = resistance and leakage reactance of the stator per phase
- R2,X2 = resistance and leakage reactance of the rotor per phase
- Xm = magnetizing reactance
- Rc = core loss resistance
- I1, I2 = stator and rotor currents (referred to stator) per phase.

The developed torque is given as,

 $T = 3(I2)2R2/(s\omega s) N-m$ 

Where,

- $\omega s = synchronous speed in radians/sec$
- $\omega r = rotor speed in radians/sec$
- s = slip.

The parameters could be determined by 'no-load' and 'blocked-rotor' tests, the former determines Rc and Xm while the latter yields R1, R2, X1, X2.

Following equations could be used

- X1 = R1 + jX1
- X2 = R2/S + jX2
- $S = \omega s \omega r / \omega$
- The Torque T = 3(I2)2R2/s
- Input power = 3V1IIpf

• Output power = $(1-S) \omega s$ 



Per phase equivalent circuit of a poly phase induction motor

In blocked rotor test, rotor is not allowed to rotate so the speed of the rotor is zero r.p.m, slip corresponding to zero speed is unity. Now, increase the stator voltage till motor current reaches to its rated value. Note down the readings of voltmeter, ammeter, wattmeters and tachometer at different stator voltages.

## **CIRCUIT DIAGRAM:-**



#### PROCEDURE:-

- 1. Rotor of induction motor is blocked in order to perform block rotor test.
- 2. Close the TPST (Triple Pole Single Throw) switch connecting three phase mains supply to induction motor.
- 3. Vary input current from zero to rated value (415V).
- 4. Observe the readings of voltmeter, ammeter, watt meters and tachometer at different i/p voltages.
- 5. Now increase the voltage by clicking the arrows on three phase variac



- 6. Store this data by clicking "Start Storing Data"
- 7. Go on repeating this procedure till sufficient readings are stored.
- 8. Now display the data by clicking "Show data". It will display data as shown
- 9. Now select one of the graph from available graphs and use "Generate graph" to plot the graph. For Ex.

## **OBSERVATION TABLE:-**

Current	Total Copper Loss	Rotor Angle	Supply Voltage
0.47	39.06	29.31	15
1.02	180.94	29.31	35
1.50	388.12	29.31	50
1.65	466.81	29.31	55
1.77	542.97	29.31	60
1.97	673.42	29.31	65

# GRAPH:-



**<u>RESULT:-</u>** Hence The test verifies that the motor is functioning correctly under Blocked rotor load conditions Virtually

**<u>OUTCOME:-</u>** By doing this Experiment CO3 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

EEV LAB

# **8. SPEED CONTROL OF SLIPRING INDUCTION MOTOR**

**<u>AIM</u>:-** To perform the speed control test on slip ring induction motor by rotor resistance control method. Plot the motor speed characteristics at different values of applied resistance in slip ring of induction motor.

# THEORY:-

A wound rotor induction motor or slip ring induction motor has a stator like the squirrel cage induction motor, but a rotor with insulated windings brought out via slip rings and brushes. However, no power is applied to the slip rings. Their sole purpose is to allow resistance to be placed in series with the rotor windings while starting.



# **SLIP RING CHARACTERISTCS**

A slip ring motor or a phase wound motor is an induction motor which can be started with full line voltage, applied across its stator terminals. The rotor winding terminals of a wound rotor motor are connected to three slip-rings mounted on but insulated from the shaft. The leads, from the three brushes pressing on these slip-rings are taken to external resistances. At the time of start, the value of starting current is adjusted by adding up external resistance to its rotor circuit. As the rotor speeds up, the external resistance is decreased in steps so that motor torque tends to remain maximum during the accelerating period. Finally, under normal operation, the external resistance is fully cut off and the slip-rings are short-circuited so that motor now develop full load torque at low value of slip-rings. The point to be noted is the "slip necessary to generate maximum torque is directly proportional to the rotor resistance." So it is evident that the slip increases with increase in external resistance.

With the above statements, let us discuss the different methods of speed control of slip ring induction motors:

- 1. Rotor Rheostat Control
- 2. Cascade Control

## SPEED CONTROL BY ROTOR RHEOSTAT CONTROL

The external rheostat which is used for the starting purpose of these slip ring motors can be used for its speed control too. But the point to look into is the starting rheostat must be rated for "continuous" operation. With the same rheostat added to the rotor circuit, it is possible to regulate the speed of slip ring motors. The resistance is engaged maximum during starting and slowly cut-off to increase the speed of the motor. When running at full speed, if the need arises to reduce the speed, the resistance is slowly added up and thus speed reduces. To understand the speed control, let us look into the torque-slip relation given below.

## Torque T = S/R

Where,

S is the slip of the motor,

R is the Rotor resistance.

It is evident from the above relation that as the rotor resistance increases, the torque decreases. But for a given load demand, the motor and thus the rotor has to supply the same torque without any decrease. So in order to maintain the torque constant, as the rotor resistance increases the slip also increases. This increase in slip is nothing but decrease in motor speed.

## **DISADVANTAGES:**

But there are some disadvantages in this method of speed control. As the rotor resistance is increased, the "I<sup>2</sup>R" losses also increases which in turn decreases the operating efficiency of the

motor. It can be interpreted as the loss is directly proportional to reduction in speed. Since the losses are more, this method of speed reduction is used only for short period only.



# **CIRCUIT DIAGRAM:-**

# PROCEDURE:-

**STEP 1**: Make connections as per the instructions. If the wire is wrongly connected, Click on node number to detach the wire. detach the wire.

STEP 2: Click on "Check" button for checking the connections.

- If connection is correct, an alert appears. Click ok. Now, go to step 4.
- If connection is wrong, an alert appears. Click ok. Now, go to step 3.

**STEP 3:** Check the connection and either detach the incorrect wire connection or Click on Reset button and start from step 1.

**STEP 4:** Switch on the MCB

**STEP 5:** Click on the autotransformer knob.

**STEP 6:** Slide the knob of the Rheostat to change the resistance.

**STEP 7:** Click on "Add to table" button to insert the readings in the table.

**STEP 8:** Follow the procedure from step 6 to step 7, till you have the 6 readings in the table.

**STEP 9:** After taking minimum 6 readings, Click on the "**Graph**" button.

**STEP 10:** Click on **"Print"** button to print the full connections with graph and table.

## **OBSERVATION TABLE:-**

S.No.	Current (A)	Power (W)	Speed (RPM)		
1	2.6	40	1474		
2	4.8	680	1388		
3	5.5	820	1363		
4	6.4	1040	1334		
5	7.5	1160	1278		
6	8	1200	1250		

# GRAPH:-





resistance control method virtually

**<u>OUTCOME:</u>** By doing this Experiment CO4 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 9. OC & SC TEST ON SINGLE PHASE TRANSFORMER

AIM:- Open Circuit and Short Circuit Test On ingle Phase Transformer.

# THEORY:-

The open circuit and short circuit tests are performed for determining the parameter of the transformer like their efficiency, voltage regulation, circuit constant etc. These tests are performed without the actual loading and because of this reason very less power is required for the test. The open circuit and the short circuit test gives a very accurate result as compared to the full load test.

# **OPEN CIRCUIT TEST**

The purpose of the open-circuit test is to determine the no-load current and losses of the transformer because of which their no-load parameter is determined. This test is performed on the primary winding of the transformer. The wattmeter, ammeter, and the voltage are connected to their primary winding. The nominal rated voltage is supplied to their primary winding with the help of the ac source.

The secondary winding of the transformer is kept open and the voltmeter is connected to their terminal. This voltmeter measures the secondary induced voltage. As the secondary of the transformer is open, no-load current flows through the primary winding. The value of no-load current is very small as compared to the full rated current. The copper loss occurs only on the primary winding of the transformer because the secondary winding is open. The reading of the wattmeter only represents the core and iron losses. The core loss of the transformer is same for all types of loads.





# **CALCULATION OF OPEN CIRCUIT TEST:-**

Let,

$$\label{eq:W0} \begin{split} W_0 &- \text{wattmeter reading} \\ V_1 &- \text{voltmeter reading} \\ I_0 &- \text{ammeter reading} \\ \end{split}$$
 Then the iron loss of the transformer  $P_i = W_0$  and

The no-load power factor is

 $\cos\Phi = W_0/(V_1I_0)$ 

Working component Iw is

Putting the value of  $W_0$  from the equation (1) in equation (2) you will get the value of working component as

 $I_w = I_0 cos \Phi$ 

Magnetizing component is

 $I_m = (I_0^2 - I_w^2)^{1/2}$ 

No load parameters are given below:

Equivalent exciting resistance is

 $R_0 = V_1 / I_1$ 

Equivalent exciting reactance is

 $X_0 = V_1 / I_m$ 

## **SHORT CIRCUIT TEST:**

The short circuit test is performed for determining the below mention parameter of the transformer.

1. It determines the copper loss occurs on the full load. The copper loss is used for finding the efficiency of the transformer.

2. The equivalent resistance, impedance, and leakage reactance are known by the short circuit test.

The short circuit test is performed on the secondary or high voltage winding of the transformer. The measuring instrument like wattmeter, voltmeter, and ammeter are connected to the high voltage winding of the transformer. Their primary winding is short circuited by the help of thick strip or ammeter which is connected to their terminal. The low voltage source is connected across the secondary winding because of which the full load current flows from both the secondary and the primary winding of the transformer. The full load current is measured by the ammeter connected across their secondary winding.

The low voltage source is applied across the secondary winding which is approximately 5 to 10% of the normal rated voltage. The flux is set up in the core of the transformer. The magnitude of the flux is small as compared to the normal flux. The iron loss of the transformer depends on the flux. It is less occur in the short circuit test because of the low value of flux. The reading of the wattmeter only determines the copper loss occur on their windings. The voltmeter measures the voltage applied to their high voltage winding. The secondary current induces in the transformer because of the applied voltage.



Fig. 2 Equivalent circuit diagram for short circuit test on transformer

# **CALCULATION OF SHORT CIRCUIT TEST:-**

Let,

$$\label{eq:Wc-Wattmeter reading} \begin{split} W_c &- Wattmeter reading \\ V_{sc} &- Voltmeter reading \\ I_{sc} &- Ammeter reading \end{split}$$

Then the full load copper loss of the transformer is given by

$$P_c = [I_{fl} \! / \! I_{sc}]^2.W_c$$

$$I_{sc}^2 \cdot R_s = W_c$$

Equivalent resistance referred to secondary side is

$$R_{s}=W_{c}.{I_{sc}}^{2}$$

Equivalent impedance referred to the secondary side is given by

$$Z_s = V_{sc}/I_{sc}$$

The Equivalent reactance referred to the secondary side is given by

$$X_s = [Z_s^2 - R_s^2]^{1/2}$$

# CIRCUIT DIAGRAM:-





## PROCEDURE:-

STEP 1: Make the proper connection by clicking the node as instructed below. If the wire

is wrongly connected, Click on the node number to detach the wire.

STEP 2: Click on "Check Connection" button for checking the connections.

- If connection is correct, an alert appears. Click ok. Now, go to step 4.
- If connection is wrong, an alert appears. Click ok. Now, go to step 3.

**STEP 3:** Check the connection and either detach the incorrect wire connection or Click on **"Reset"** button and start from step 1.

STEP 4: Switch on the MCB.

**STEP 5:** Click on the Autotransformer knob.

**STEP 6:** Click on "Add to Table" button to add the readings to the observation table.

STEP 7: Click on "Short Circuit Test" button to perform the SC Test.

**STEP 8:** Make the proper connection by clicking the node as instructed below. If the wire is wrongly connected, Click on the node number to detach the wire.

From	А	В	D	Е	Е	D	Н	С	L	V	S1
То	D	Е	F	G	I	P2	М	L	P1	P2	S2



STEP 9: Repeat steps 2 to 6.

**STEP 10:** Click on "**Submit**" button to get an equivalent circuit diagram of transformer.

**STEP 11:** Click on "**Print**" button to print the webpage.

# OC TEST:

# OBSERVATION TABLES.No.Poc(Watt)Ioc(A)Voc(V)1500.9230

# **SC TEST:**

OBSERVATION TABLE									
S.No.	S.No. Psc(Watt) Isc(A) Vsc(V)								
1	37.5	4.5	11						

**<u>RESULT</u>**: Hence Determined the Transformer Equivalent Circuit from open circuit and Short circuit

**<u>OUTCOME</u>**: By doing this Experiment CO2 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained

# 10. V AND INVERTED V CURVES OF THREE PHASE SYNCHRONOUS MOTOR

AIM:- V Curves and Inverted V curves of Three Phase Synchronous Motor.

## THEORY:-

Electromagnetic devices draw a magnetizing current from the a.c source, in order to establish the working flux. This magnetizing current lags the applied voltage by almost 900.

A synchronous motor is a double-excited machine, its armature winding is energised from an a.c source and its field winding from d.c source. When synchronous motor is working at constant applied voltage, the resultant air gap flux demanded by applied voltage remains constant. This resultant air gap flux is established by both a.c in armature winding and d.c in the field winding. If the field current is sufficient enough to set up the air-gap flux, as demanded by constant applied voltage then magnetizing current or lagging reactive VA requied from the a.c source is zero and therefore motor operates at unity power factor. This field current, which causes unity power factor operation of the synchronous motor, is called normal excitation or normal field current. If the current less than the normal excitation, i.e the motor is under excited, then the deficiency in flux must be made up by the armature winding m.m.f. In order to do the needful, the armature winding draws a magnetizing current or lagging reactive VA from the a.c source and as a result of it, the motor operates at a lagging power factor. In case the field current is made more than its normal excitation, i.e the motor is over-excited, operates at leading power factor. Fig(1) shows the variation of armature current and power factor with field current at no load, half load and full load conditions.

# **CIRCUIT DIAGRAM:-**



Circuit Diagram: V Curves and Inverted V Curves of three Phase Synchronous Motor

## PROCEDURE:-

- 1. The machine under consideration salient pole synchronous motor. The short circuited aluminium damper bars are put in the rotor to make it self-starting. When 3 phase supply is applied to the stator of motor, motor will act like induction machine and it will attain speed slightly less than synchronous speed. This is achieved by switching on the 3 phase supply with TPST (triple pole single throw) for synchronous motor.
- 2. With the help of 3 phase auto-transformer the voltage to be applied to the stator of synchronous motor is varied smoothly. When motor attends speed near to synchronous speed (generally at rated voltage), turn field supply on of motor with help of DPST (double pole single throw) switch and apply rated voltage in steps. Here onwards the speed of synchronous machine will be constant as synchronous speed.



3.Output of motor will drive DC generator which in turn will drive electrical load (resistive load bank).



4.Now depending on excitation for synchronous machine (which can be varied by altering rheostat arrangement in expt.) given to the synchronous motor, the power factor of motor will operate on the (over-excitation) leading, (critical) unity or (under-excited) lagging power factor.



To keep air gap flux constant in synchronous motor reactive power is needed. It is met by AC supply of synchronous motor depending on its field excitation. Plot the variations of stator current drawn by the synchronous motor with its field current.

- 5. Its graph follows shape of V, hence the name V curves. This characteristic of synchronous machine. Variation of power factor with field current of motor in exactly reverse fashion, which is called as inverted V curves. The point of least armature current drawn from stator of Synchronous motor will correspond to unity power factor and both graphs will have same field current reading.
- 6. Store this data by clicking "Start Storing Data"
- 7. Go on repeating this procedure till all load are connected and data is stored.
- 8. Now display the data by clicking "Show data". For Ex.

## **OBSERVATION TABLE:-**

Vfa	Ifa	Vs	Inl	ve	-m	speed	Power Factor
2	0.01	300	3.52	429	1.26	1500	0.09
14	0.08	300	2.65	429	1.26	1500	0.20
24	0.13	300	1.80	429	1.26	1500	0.33
32	0.18	300	1.27	429	1.26	1500	0.53
38	0.21	300	0.96	429	1.26	1500	0.72
44	0.24	300	0.79	429	1.26	1500	0.93
50	0.28	300	0.75	429	1.26	1500	1.00
58	0.32	300	0.89	429	1.26	1500	0.87
64	0.36	300	1.10	429	1.26	1500	0.77
70	0.39	300	1.25	429	1.26	1500	0.65
104	0.58	215	3,22	420	1.23	1467	0.42
124	0.69	215	3.71	420	1.23	1467	0.37

- Vfa=field voltage of alternator
- Ifa=field current of alternator
- Vt=terminal voltage
- Vs=supply voltage
- Ial=alternator current
- 10. These V curves can be performed on various loads and no load conditions on the synchronous motors.

11.While switching motor off, in stepwise manner reduce the stator supply to zero, and switch off TPST (triple pole single throw) switch. Then in steps cut down field supply for synchronous motor.



11. Now select one of the graph from available graphs and use "Generate graph" to plot the graph.

**<u>RESULT</u>:-** Hence Verified the V curves and Inverted V curves of 3 Phase synchronous

Motor Virtually.

**<u>OUTCOME:</u>** By doing this Experiment CO5 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained
# 11.VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM

AIM:- Verification of Maximum Power Transfer Theorem

### THEORY:

Maximum power is transferred from a source of given voltage and an internal impedance to the load impedance  $Z_L$  in the following circuit shown in figure 1, under three conditions



[Fig 1: Circuit diagram with source and load impedance(i.e. Z<sub>S</sub> and Z<sub>L</sub>)]

### 1. When only X<sub>L</sub> is adjustable:

Under this condition the power consumed by the load  $(I^{2*}R_L)$  is maximum, when I is maximum, since  $R_L$  is constant.

$$egin{aligned} I &= rac{V_s}{R_s + jX_s + R_L + jX_L} \cdots (1) \ |I|_{max} &= rac{V_s}{R_s + R_L} \cdots \cdots (2) \ && ext{when} \ X_L &= -X_s \end{aligned}$$

This means that if the load reactance( $X_L$ ) is made equal magnitude and opposite in sign to the internal reactance( $X_s$ ), the power transferred is maximum.

# When only RL is adjustable:

From equation (1) in section (1), one may write

$$P = |I^2| * R_L = rac{V_s^2 * R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \dots (3)$$

Differentiating the equation (3) w.r.t RL and equating to zero, one obtains.

$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2 \dots \dots \dots (4)}$$

#### 3. When both $R_L$ and $X_L$ are adjustable:

Under this condition both equation (2) and (4) are valid simultaneously and one obtains.

RL=Rs

**PROCEDURE:**-



#### 1. When only XL is adjustable:-

- 1. Take a suitable set of values of  $V_s$ ,  $X_S$ ,  $X_L$  as shown in the figure. You can choose  $X_S$  to be inductive ( $L_s$ ) and capacitive ( $C_s$ ).  $X_L$  can choose as inductive( $L_L$ ) and capacitive ( $C_L$ ) to the load.
- 2. Next choose a suitable load resistance (R<sub>L</sub>).
- 3. For the maximum power theorem, the condition would be  $R_L=R_S$ ,  $X_S(i.e. X_1)=-X_{L.}(i.e. X_2)$

Where,



Take an example, put  $L_s=1$  mH,  $C_s=10.1$  µF.

Now for different value of  $C_s$ , note down  $V_1$  and  $V_4$ .

Load power (P<sub>L</sub>) = 
$$I^{2*}R_L = I*I*R_L = (V_1/100)*V_4$$
  
=  $K*V_1*V_4$   
where K=1/100 = 1/R<sub>s</sub>

Enter the value of the voltage for different values of  $C_s$  and obtain the set corresponding to the maximum value of  $(V_1*V_4)$ . Verify that for this set  $V_2=V_6$ .

#### 2. When only RL is adjustable:

Repeat the procedure of part (1), with C<sub>s</sub> fixed and R<sub>L</sub> varied. At the point of maximum power check

$$R_L = \sqrt{(R_s^2 + (X_1 + X_2)^2)}$$

# 3. When both RL and XL are adjustable:

Repeat the procedure of part (2), varying  $C_s$  and obtain the maximum power condition.

Check under this condition,

 $\nabla_{\text{RL}} = \nabla_{\text{RS}}$  i.e.  $\nabla_1 = \nabla_4$ ;  $\nabla_{\text{LS}} = \nabla_{\text{CL}}$  i.e.  $\nabla_2 = \nabla_6$ ;

#### **CIRCUIT DIAGRAM:-**



#### **OBSERVATION TABLE:-**

Load Resistance (RI)	Power(p)
10	700
20	900
30	900
40	850
50	800
60	750
70	700
80	650

# GRAPH:-





**OUTCOME:** By doing this Experiment CO1 and PO1,PO2,PO3,PO5,PO8,PO9, PO10,PO11,PO12.PSO1,PSO2 are Attained

# **12. SYNCHRONIZATION OF ALTERNATOR WITH INFINITE BUS BAR**

#### Aim:

To study the Synchronization of the alternator with infinite bus bar.

#### **EQUIPMENTS REQUIRED:**

- 1. DC Motor Alternator Set
- 2. Voltmeter-1
- 3. Rheostats-2
- 4. Tachometer-1

### **THEORY:**

Before synchronization, following conditions must be satisfied:

#### (1) EQUALITY OF VOLTAGE

The terminal voltage of both the systems i.e. the incoming alternator and the bus bar voltage or other alternator must be same.

# (2) PHASE SEQUENCE

The phase sequence of both the systems must be same.

# (3) EQUALITY OF FREQUENCY

The frequency of both the systems must be same. The condition (1) can be checked with the help of voltmeter and the condition (2) and (3) by any synchronizing method. There are two synchronizing methods

- a. Using incandescent lamp
- b. Using synchroscope. Now we discuss in detail about these methods.

#### (a) Using Incandescent lamp:

Let machine G2 be synchronized with machine G1 which is already connected with the bus bar, using three lamps (L1, L2 and L3) method. These lamps are known as synchronizing lamps connected as shown in Fig.1

If the speed of machine 2 is not brought upto that of machine 1 then its frequency will also be different, hence there will be a phase difference between their voltages as shown in Fig.2. Due to difference in frequencies the resultant voltage will under go changes similar to the frequency changes of beats produced when two sound sources of nearly equal frequencies are sounded together.



Fig. 1 Synchronization using three lamp method

The resultant voltage is sometimes maximum and sometimes minimum. Hence, the lamps will flicker, sometimes dark and sometimes bright. Synchronization is done at the middle of the dark period. This method of synchronizing is known as dark lamp method.



Fig. 2 Waveforms when two systems operating at different frequencies

Lamp L1 is connected between A1 and A2, L2 between B1 and C2 and L3 between C1 and B2. These three lamps slowly brighten and darken in cyclic successor in a direction depending upon whether incoming machine 2 is fast or slow. The synchronizing switch will be closed at the moment when lamp L1 will be completely dark. This transposition of two lamps suggested by Siemens and Aalske helps to indicate

Whether the incoming machine 2 is running too slow or too fast. If lamps were connected symmetrically, they would dark out or glow up simultaneously (if phase rotation is same.).

#### This method has following drawbacks:

The lamps become dark at about one third of the rated voltage. Hence, faulty synchronizing may be done in dark period.

- 1. Using this method it is not possible to find out that how much the machine is slow or fast.
- 2. This method is not applicable for high voltage alternators, because lamp ratings are normally low. For such situations we need an extra transformer to step down the voltage.

# (b) SYNCHRONIZING BY SYNCHROSCOPE:

Synchroscope is a device that shows the correct instant of closing the synchronizing switch with the help of a pointer which will rotate on the dial. The rotation of pointer also indicates whether the incoming machine is running too slow or too fast. If incoming machine is slow then pointer rotates in anticlockwise direction and if machine is fast then pointer rotates in clockwise direction.



Fig. 3 Synchronizing by Synchroscope

### **CIRCUIT DIAGRAM:**



#### PROCEDURE:-

- 1. Make the connections.
- 2. Run one of the alternators and adjust its voltage at rated value and close the switch to connect with the bus bar.
- 3. Start the second set (incoming machine 2), bring it upto proper speed equal to that of the running machine (bus bar voltage).
- 4. Synchronize the incoming machine by any one synchronization method.

#### **OBSERVATION:-**

- 1. Measure and adjust voltage of incoming machine (Vg) and bus bar (Vs) till Vg=Vs.
- 2. Measure and adjust the speed of incoming machine, till synchroscope needle creeps.
- 3. Close synchronizing switch

INPUTS
Terminal Voltage = 230V + Variation 25 (-50 to 50V)
Field Resistance $R_f = 160\Omega + Variation (\Delta R_f)$ 15 (0-20 $\Omega$ )
Armature Resistance $R_a = 1\Omega + Variation (\Delta R_a) 0.9$ (0-1 $\Omega$ )
OUTPUTS
Speed w(rpm): 1536.01
Current I <sub>a</sub> (A): 1.65

INPUTS
Speed w = 1500rpm + Change in Speed ( $\Delta w$ ) 100 (-150 to 150rpm)
$R_{fg} = 160\Omega + Variation (\Delta R_{fg}) 8$ (-10 to 10 $\Omega$ )
OUTPUTS
Frequency(Hz): 53.33
Terminal Voltage(V): 423.21

**<u>RESULT:</u>** Hence The alternator was successfully synchronized with the infinite bus bar at

53.33Hz frequency and 25v voltage

**<u>OUTCOME:</u>** By doing this Experiment CO5 and PO1,PO2,PO3,PO5,PO8,PO9,

PO10,PO11,PO12.PSO1,PSO2 are Attained