

UNIT-I

1. Identify the parameters Required to calculate the current in a silicon PN Junction diode for a forward-bias voltage of 0.6V at 25°C, Given a Reverse saturation current of 10μA?

Sol:- Given data,

$$\text{Voltage (V)} = 0.6 \text{ V}$$

$$\text{Temperature (T)} = 25^\circ\text{C} = 25 + 273 = 298 \text{ K}$$

$$\text{Reverse saturation current (I}_0\text{)} = 10 \times 10^{-6} \text{ A}$$

$$\text{for silicon diode, } \eta = 2$$

$$\text{known data, } k = 1.38 \times 10^{-23} \text{ J/K}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} \times 298}{1.6 \times 10^{-19}} = 25.7 \text{ mV}$$

Formulas :-

$$I = I_0 \left[e^{\frac{V}{\eta V_T}} - 1 \right]$$

calculation,

$$I = 10 \times 10^{-6} \left[e^{\frac{0.6}{2 \times 25.7 \times 10^{-3}}} - 1 \right]$$

$$I = 10 \times 10^{-6} \left[e^{11.67} - 1 \right]$$

$$\therefore I = 1.17 \text{ mA}$$

2. Identify the factors involved in calculating the DC and AC Resistance of a Germanium junction diode at 25°C with $I_0 = 30\mu\text{A}$ and an applied voltage of 0.2V ?

sol:- Given data, $T = 25^\circ\text{C} = 25 + 273 = 298\text{K}$

$$I_0 = 30 \times 10^{-6} \text{ A}$$

$$V_D = 0.2 \text{ V}$$

$$\eta = 1 \text{ (for Germanium)}$$

Formula :-

$$\text{DC Resistance } (R_{DC}) = \frac{V}{I}$$

$$\text{AC Resistance } (R_{AC}) = \frac{\eta V_T}{I}$$

$$I = I_0 \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$$

$$V_T = \frac{KT}{Q}$$

$$K = 1.38 \times 10^{-23} \text{ J/K}$$

$$Q = 1.6 \times 10^{-19} \text{ C}$$

$$V_T = \frac{1.38 \times 10^{-23} \times 298}{1.6 \times 10^{-19}} = 25.7 \text{ mV}$$

$$I = 30 \times 10^{-6} \left[e^{\frac{0.2}{1 \times 0.0257}} - 1 \right] = 30 \times 10^{-6} [e^{7.8125} - 1]$$
$$= 0.0741 \text{ A}$$

$$\therefore I = 74 \text{ mA}$$

$$\therefore R_{DC} = \frac{0.2}{0.074} = 2.6 \Omega$$

$$\therefore R_{AC} = \frac{1 \times 0.0257}{0.074} = 0.33 \Omega$$

3. Identify the parameters needed to determine the diffusion capacitance due to holes in a Ge diode with a forward-biased current of 26 mA and hole mean life time of 20 μ sec (τ) - at 300K temperature?

Sol:- Given data,

$$T = 27^\circ\text{C} = 27 + 273 = 300\text{K}$$
$$\tau = 20 \times 10^{-6} \text{ sec}$$
$$I = 26 \times 10^{-3} \text{ A}$$
$$\eta = 1$$

Formulas:- $V_T = \frac{kT}{q}$

$$\text{diffusion capacitance } (C_D) = \frac{\tau I}{\eta V_T}$$

$$\therefore V_T = \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} = 0.026 \text{ (or) } 26 \text{ mV}$$

$$\therefore C_D = \frac{20 \times 10^{-6} \times 26 \times 10^{-3}}{1 \times 26 \times 10^{-3}}$$
$$= 20 \times 10^{-6} \text{ F (or) } 20 \mu\text{F}$$

4. Identify the factors needed to calculate the capacitance for a capacitor filter in a full-wave rectifier operating at 400 Hz, given a ripple factor of 10% and a 500 Ω load.

Sol:- Given data,

$$\text{frequency} = 400 \text{ Hz}$$
$$\text{Resistance } (R_L) = 500 \Omega$$

Ripple factor is 10% that is 0.01

Formula :- $\text{Ripple factor} = \frac{1}{4\sqrt{3} f C R_L}$

$$0.01 = \frac{1}{4\sqrt{3} \times 400 \times C \times 500}$$

$$0.01 = \frac{0.722 \times 10^{-6}}{C}$$

$$\therefore \text{Capacitance } (C) = \frac{0.722 \times 10^{-6}}{0.01} = 72.2 \times 10^{-6} \text{ F} \\ = 72.2 \mu\text{F}$$

5. Identify the steps to determine i) peak, average, and RMS values of current, ii) DC power output, iii) AC input power, and iv) Efficiency for a half-wave Rectifier with a 1000Ω Resistance load, Rectifying an AC voltage with a 325 V peak value and a diode forward Resistance of 100Ω ?

Sol:- Given data,

$$V_m = 325 \text{ V}$$

$$R_L = 1000 \Omega$$

$$R_D = 100 \Omega$$

$$\text{Formulas:- peak value of current } (I_m) = \frac{V_m}{R_L + R_D} = \frac{325}{1000 + 100} = 295.5 \text{ mA}$$

$$\text{Average} = I_{\text{avg}} = \frac{I_m}{\pi} = \frac{295.5 \times 10^{-3}}{\pi} = 94.04 \text{ mA}$$

$$I_{\text{rms}} = \frac{I_m}{2} = \frac{295.5 \times 10^{-3}}{2} = 147.7 \text{ mA}$$

$$\text{DC power, } P_{\text{dc}} = I_{\text{avg}}^2 \times R_L = (94.04 \times 10^{-3})^2 \times 1000 = 8.645 \text{ W}$$

$$\text{AC power, } P_{\text{ac}} = I_{\text{rms}}^2 \times (R_L + R_D) = (147.7 \times 10^{-3})^2 \times (1000 + 100)$$

$$= (0.1477)^2 \times (1100)$$

$$= 24 \text{ W}$$

$$\text{Efficiency of half-wave Rectifier } (\eta) = \frac{P_{\text{dc}}}{P_{\text{ac}}}$$

$$= \frac{8.645}{24}$$

$$= 36.8 \%$$

6. Outline the approach to determine a) DC voltage across the load, b) DC current through the load, c) DC power delivered to the load, d) PIV e) Ripple voltage and frequency, f) Rectification Efficiency for a full-wave Rectifier with a 5:1 step down center-tap transformer and a 900 Ω load. Assume a 230V, 60Hz AC input, with a load total resistance of 100 Ω from the diodes and secondary coil.

Sol:- Given data,

$$\text{Input voltage} = 230 \text{ V AC}$$

$$\text{frequency} = 60 \text{ Hz}$$

$$\text{Resistance } (R_D) = 100 \Omega$$

$$\text{Load } R_L = 900 \Omega$$

$$\text{Formulas:- a) DC voltage, } (V_{\text{out}}) = \frac{230}{5} = 46 \text{ V},$$

$$\text{b) } V_{\text{rms}} = \frac{V_{\text{out}}}{2} = \frac{46}{2} = 23 \text{ V}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}, \therefore V_m = V_{\text{rms}} \sqrt{2} = 23 \times \sqrt{2} = 32.5 \text{ V}$$

$$\text{a) DC voltage, } V_{\text{DC}} = \frac{2V_m}{\pi} = \frac{2 \times 32.5}{\pi} = 20.7 \text{ V}$$

$$\text{b) DC current, } I_{\text{DC}} = \frac{V_{\text{DC}}}{R_L + R_D} = \frac{20.7}{100 + 900} = 20.7 \text{ mA}$$

$$\text{c) DC power, } P_{\text{DC}} = (I_{\text{DC}})^2 \times R_L = (20.7 \times 10^{-3})^2 \times 900 = 0.386 \text{ W}$$

$$\text{d) PIV} = 2V_m = 2 \times 32.5 = 65 \text{ V}$$


$$\text{e) Ripple voltage, } V_r, V_{\text{rms}} = \sqrt{(V_{\text{rms}})^2 - (V_{\text{DC}})^2} = \sqrt{(23)^2 - (20.7)^2} = 10.05 \text{ V}$$

$$\text{frequency} = 2f = 2 \times 60 = 120 \text{ Hz}$$

$$\text{f) Efficiency } (\eta) = \frac{P_{\text{DC}}}{P_{\text{AC}}} = \frac{(V_{\text{DC}})^2 / R_L}{(V_{\text{rms}})^2 / R_L} = \frac{(20.7)^2}{(23)^2} = 0.81$$

$$\text{percentage of Rectification Efficiency} = 81\%$$

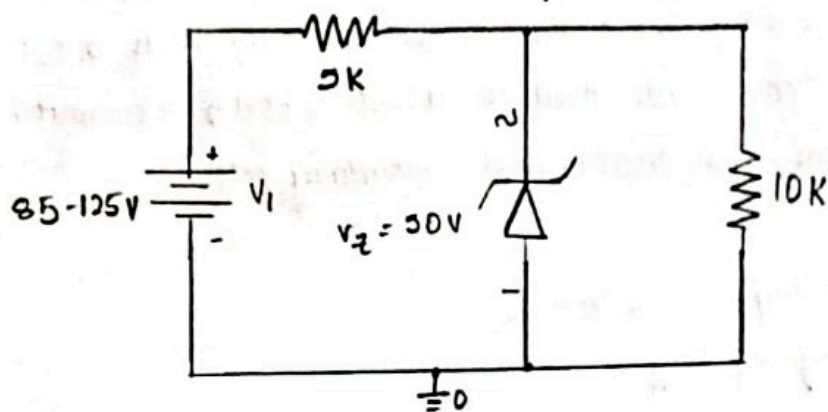7. Identify, conditions for Maximum and minimum current through a Zener diode in a Regulator circuit, considering supply voltage and load Resistance.




Sol:- Given data, $R_s = 5\text{ K}\Omega$
 $R_L = 10\text{ K}\Omega$

Input voltage = 85 to 125 V

Z voltage = 50 V

Re-drawing circuit:-

i) For Minimum:-

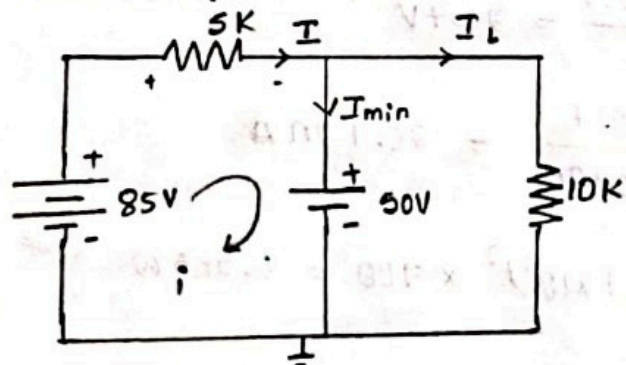

Apply KVL,

$$85 - i(5 \times 10^3) - 50 = 0$$


$$35 = i(5 \times 10^3)$$

$$i = \frac{35}{5 \times 10^3} = 7\text{ mA}$$

We know that, $V = IR$

$$I_L = \frac{V}{R_L} = \frac{50}{10 \times 10^3} = 5\text{ mA}$$

ii) For Maximum:-

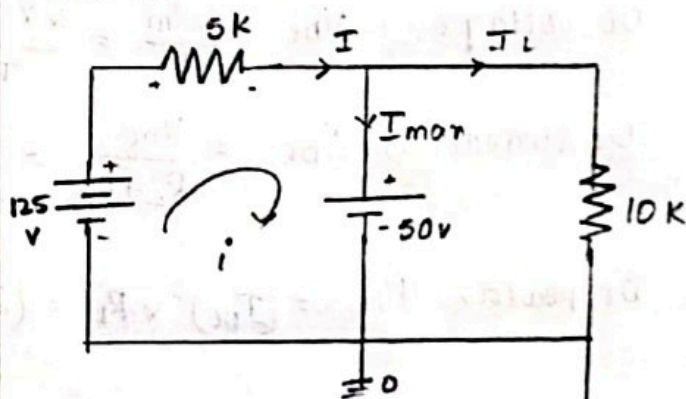

Apply KVL,

$$125 - i(5 \times 10^3) - 50 = 0$$

$$75 = i(5 \times 10^3)$$

$$i = \frac{75}{5 \times 10^3} = 15\text{ mA}$$

We know that, $V = IR_L$

$$I_L = \frac{V}{R_L} = \frac{50}{10 \times 10^3} = 5\text{ mA}$$

From the circuit,

$$I = I_{\min} + I_L$$

$$\therefore I_{\min} = I - I_L = 7 \text{ mA} - 5 \text{ mA}$$

$$\therefore I_{\min} = 2 \text{ mA}$$

From the circuit

$$I = I_{\max} + I_L$$

$$I_{\max} = I - I_L = (7 \text{ mA} - 5 \text{ mA})$$

$$\therefore I_{\max} = 10 \text{ mA}$$

8. Identify the steps needed to determine i) DC output voltage and ii) PIV for a half-wave Rectifier circuit with a 220V AC supply and transformer turn ratio 10:1, assuming an ideal diode.

Sol:- Given data, Input voltage = 230 V AC

Transformer turn Ratio = 10:1

Formula: $V_{\text{out}} = \frac{220}{10} = 22 \text{ V}$

$$V_{\text{RMS}} = \frac{220}{10} = 22 \text{ V}$$

$$\therefore V_{\text{RMS}} = \frac{V_m}{\sqrt{2}} \Rightarrow V_m = \sqrt{2} V_{\text{RMS}} = \sqrt{2} \times 22 = 31.11 \text{ V}$$

i) DC output voltage $V_{\text{DC}} = \frac{V_m}{\pi} = \frac{31.11}{\pi} = 9.902 \text{ V}$

ii) PIV = $V_m = 31.11 \text{ V}$

9. Determine the process to find the average and RMS load current in a full-wave Rectifier circuit, Given an RMS Secondary voltage of 50 V (from center tap to each end), a load Resistance of 900Ω , and a combined diode and transformer resistance of 100Ω .

Sol:- Given data, $R_D = 100 \Omega$
 $R_L = 900 \Omega$

$$\text{RMS secondary voltage} = 50 \text{ V} = V_{\text{RMS}}$$

Formulas:-

$$\text{Load current } I_m = \frac{V_m}{R_0 + R_L} = \frac{V_{rms} \times \sqrt{2}}{R_0 + R_L} = \frac{50 \times \sqrt{2}}{900 + 100} = \frac{70.7}{1000} = 70.7 \text{ mA}$$

$$\text{Average load current, } I_{DC} = \frac{2I_m}{\pi} = \frac{2 \times 70.7 \times 10^{-3}}{\pi} = 45 \text{ mA}$$

$$\text{Rms value of load current, } I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{70.7 \times 10^{-3}}{\sqrt{2}} = 50 \text{ mA.}$$

10. Identify the parameters a LED driver circuit with a 5V supply, 2V LED forward voltage, and 20mA current requirement. Calculate the needed series resistor value.

Sol:- Given data,

$$\text{Supply voltage} = 5V$$

$$V_{LED} = 2V$$

$$I = 20 \times 10^{-3} \text{ A}$$

Formulas:-

$$R = \frac{V}{I} = \frac{V_{\text{supply}} - V_{LED}}{I}$$

$$\therefore V_R = V_{\text{supply}} - V_{LED} = 5V - 2V = 3V.$$

$$\text{Resistor value } (R) = \frac{3V}{20 \times 10^{-3}} = 150 \Omega.$$

- 1) calculate the values of the I_B and current amplification factor α in a common base transistor circuit, the emitter current I_E is 10mA and the collector current I_C is 9.8mA.

Sol:-

Given that:-

$$I_E = 10 \text{ mA}$$

$$I_C = 9.8 \text{ mA}$$

$$\rightarrow I_E = I_B + I_C$$

$$10 \times 10^{-3} = I_B + 9.8 \times 10^{-3}$$

$$I_B = 9.8 \times 10^{-3} - 10 \times 10^{-3}$$

$$I_B = 0.2 \text{ mA}$$

$$\rightarrow \alpha = \frac{I_C}{I_E}$$

$$= \frac{9.8 \times 10^{-3}}{10 \times 10^{-3}}$$

$$= 0.98$$

- 2) calculate α , I_C and I_E for Ge Transistor, $\beta = 50$, $I_{CBO} = 5 \mu\text{A}$ and $I_B = 100 \mu\text{A}$.

Given that:-

$$\beta = 50$$

$$I_{CBO} = 5 \mu\text{A}$$

$$I_B = 100 \mu\text{A}$$

$$\rightarrow I_C = \beta I_B + (1 + \beta) I_{CBO}$$

$$I_C = 50 \times 100 \times 10^{-6} + (1 + 50) 5 \times 10^{-6}$$

$$I_C = 5 \times 10^{-3} + 51 \times 5 \times 10^{-6}$$

$$I_C = 5.255 \text{ mA}$$

$$\rightarrow I_E = I_C + I_B$$

$$I_E = 5.255 \text{ mA} + 0.1 \text{ mA}$$

$$I_E = 5.355 \text{ mA}$$

$$\rightarrow \alpha = \frac{\beta}{1+\beta}$$

$$\alpha = \frac{50}{51} = 0.9804$$

3) Determine the common base dc current gain and base current, in a common base connection, the emitter current is I_E is 6.28 mA and the collector current I_C is 6.20 mA.

Sol:- Given that :-

$$I_E = 6.28 \text{ mA}$$

$$I_C = 6.20 \text{ mA}$$

$$\Rightarrow \alpha = \frac{I_C}{I_E} = \frac{6.20 \times 10^{-3}}{6.28 \times 10^{-3}} = 0.987$$

$$\Rightarrow I_E = I_B + I_C$$

$$I_B = I_E - I_C$$

$$I_B = 6.28 \times 10^{-3} - 6.20 \times 10^{-3}$$

$$I_B = 0.08 \text{ mA}$$

4) Calculate the values of I_C and I_E for a transistor with $\alpha_{dc} = 0.99$ and $I_{CB0} = 5 \mu\text{A}$, I_B is measured as $20 \mu\text{A}$.

Sol:- Given that :-

$$\alpha_{dc} = 0.99$$

$$I_{CB0} = 5 \mu\text{A}$$

$$I_B = 20 \mu\text{A}$$

$$\Rightarrow I_C = \frac{\alpha_{dc} I_B}{1 - \alpha_{dc}} + \frac{I_{CBO}}{1 - \alpha_{dc}}$$

$$= \frac{0.99 \times 20 \times 10^{-6}}{1 - 0.99} + \frac{5 \times 10^{-6}}{1 - 0.99}$$


$$= 2.48 \text{ mA}$$

$$\Rightarrow I_E = I_B + I_C$$

$$I_E = 20 \times 10^{-6} + 2.48 \times 10^{-3}$$

$$I_E = 2.5 \text{ mA}$$

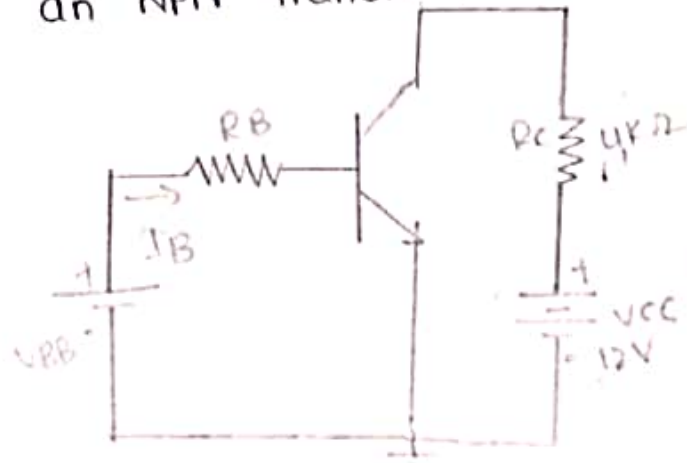5) Determine the base current required in order for the transistor to enter into saturation region of given an NPN transistor switch is 0.98.



Sol:- given that :- $\alpha = 0.98$, $I_{C0} = 2 \mu\text{A}$; $I_{CE0} = 1.6 \mu\text{A}$, $V_{CC} = 12\text{V}$

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{12}{4 \times 10^3} = 3 \text{ mA} \quad \text{and } R_C = 4 \text{ k}\Omega$$


$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

$$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{\beta}$$

$$= \frac{3 \times 10^{-3}}{49}$$

$$= 61.224 \times 10^{-6}$$

$$= 61.224 \mu\text{A}$$

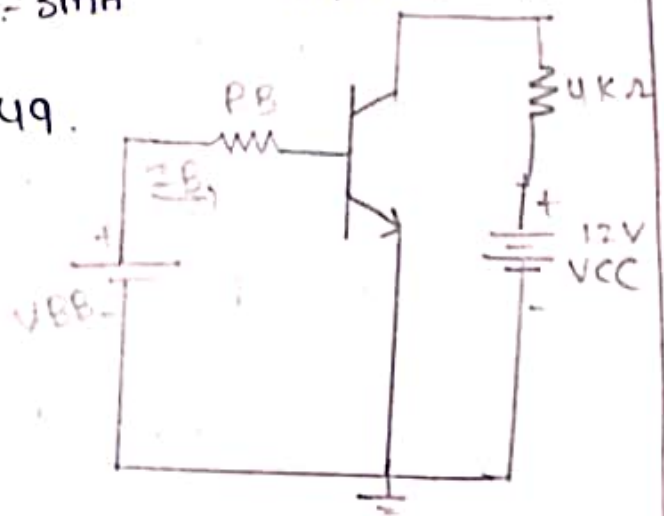

6) calculate the emitter current with $\alpha_{dc} = 0.99$
and $I_{CBO} = 50 \mu A$, I_B is measured as $1 mA$.

Sol: Given that $\alpha_{dc} = 0.99$
 $I_{CBO} = 50 \mu A$
 $I_B = 1 mA$

$$\begin{aligned} I_C &= \frac{\alpha_{dc} I_B}{1 - \alpha_{dc}} + \frac{I_{CBO}}{1 - \alpha_{dc}} \\ &= \frac{0.99 (1 \times 10^{-3})}{1 - 0.99} + \frac{50 \times 10^{-6}}{1 - 0.99} \\ &= \frac{0.99 \times 10^{-3}}{0.01} + \frac{50 \times 10^{-6}}{0.01} \\ &= 99 mA + 5 mA \end{aligned}$$

$$I_C = 104 mA$$

$$\begin{aligned} I_E &= I_B + I_C \\ &= 1 mA + 104 mA \end{aligned}$$

$$I_E = 105 mA$$

7) Determine I_C , I_E and for a transistor circuit having
 $I_B = 15 \mu A$ and $\beta = 150$

Sol: Given that:-

$$I_B = 15 \mu A$$

$$\beta = 150$$


$$\begin{aligned} \Rightarrow I_C &= \beta I_B \\ &= 150 (15 \times 10^{-6}) \\ &= 2.25 mA \end{aligned}$$

$$\begin{aligned} \Rightarrow I_E &= I_C + I_B \\ I_E &= 2.25 \times 10^{-3} + 15 \times 10^{-6} \\ I_E &= 2.265 mA \end{aligned}$$

$$\Rightarrow \alpha = \frac{\beta}{1+\beta}$$

$$= \frac{150}{151} = 0.9934.$$

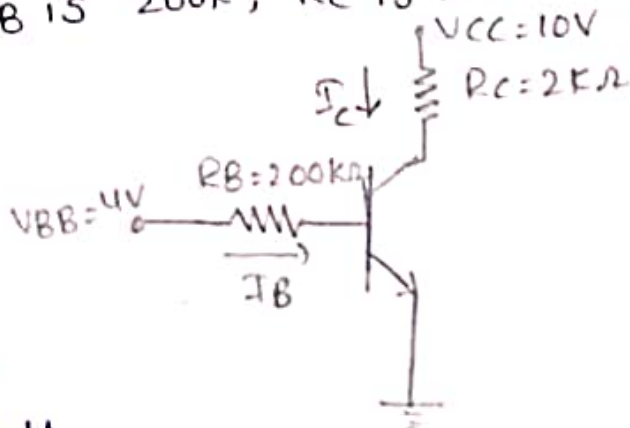B) Determine the base, collector and emitter currents and V_{CE} for the CE circuit V_{CC} is 10V, V_{BB} is 4V, R_B is 200k, R_C is 2k, V_{BE} is 0.7V and β is 200.



Sol:-

Given that :-

$$V_{CC} = 10V$$

$$V_{BB} = 4V$$

$$R_B = 200k\Omega$$

$$R_C = 2k\Omega$$

$$V_{BE} = 0.7V$$

$$\beta = 200.$$

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{4 - 0.7}{200 \times 10^3} = 16.5 \mu A.$$

$$\Rightarrow I_C = \beta I_B = 200(16.5 \times 10^{-6}) = 3.3mA$$

$$\Rightarrow I_E = I_B + I_C = 16.5 \times 10^{-6} + 3.3 \times 10^{-3} = 3.3165mA$$

$$\begin{aligned} \Rightarrow V_{CE} &= V_{CC} - I_C R_C \\ &= 10 - 3.3 \times 10^{-3} \times 2 \times 10^3 \\ &= 3.4V. \end{aligned}$$

9) calculate the value of base current, the common base dc current gain of a transistor is 0.967. if the emitter current is 10 mA.

Sol: Given that :-

$$\alpha = 0.967$$

$$I_E = 10 \times 10^{-3}$$

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E$$

$$I_C = 0.967 (10 \times 10^{-3})$$

$$I_C = 9.67 \text{ mA}$$

$$I_E = I_B + I_C$$

$$I_B = I_E - I_C$$

$$I_B = 10 \times 10^{-3} - 9.67 \times 10^{-3}$$

$$I_B = 0.33 \text{ mA}$$

10) Determine the i) β of the transistor ii) α of the transistor
iii) current I_E of transistor has $I_B = 100 \mu\text{A}$ and $I_C = 2 \text{ mA}$

Sol: Given that :-

$$I_B = 100 \mu\text{A}$$

$$I_C = 2 \text{ mA}$$

$$i) \beta = \frac{I_C}{I_B}$$

$$\beta = \frac{2 \times 10^{-3}}{100 \times 10^{-6}} = \frac{2 \times 10^{-3}}{1 \times 10^{-4}} = 20$$

$$ii) \alpha = \frac{\beta}{1 + \beta}$$

$$= \frac{20}{21} = 0.952$$

$$iii) I_E = I_B + I_C$$

$$= 100 \times 10^{-6} + 2 \times 10^{-3}$$

$$= 2.1 \times 10^{-3} \text{ A}$$

$$= 2.1 \text{ mA}$$

1) Determine the drain current I_{DS} , g_m and g_{m0} of an N-channel JFET has I_{DSS} is 10 mA and V_p is -5V for V_{GS} is -2V in the pinch-off region

Sol: Given data

$$I_{DSS} = 10 \text{ mA}$$

$$V_p = -5 \text{ V}$$

$$V_{GS} = -2 \text{ V}$$

$$\begin{aligned} I_{DS} &= I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2 \\ &= 10 \times 10^{-3} \left[1 - \left(\frac{-2}{-5} \right) \right]^2 \\ &= 10 \times 10^{-3} \left[1 - \frac{2}{5} \right]^2 \\ &= 10 \times 10^{-3} \left[\frac{3}{5} \right]^2 \\ &= 3.6 \times 10^{-3} \end{aligned}$$

$$\boxed{I_{DS} = 3.6 \text{ mAmps}}$$

$$\begin{aligned} g_{m0} &= \frac{-2 I_{DSS}}{V_p} \\ &= \frac{(-2) \times 10 \times 10^{-3}}{(-5)} \\ &= 2 \times 2 \times 10^{-3} \end{aligned}$$

$$\therefore \boxed{g_{m0} = 4 \times 10^{-3} \text{ S}}$$

$$\begin{aligned} g_m &= g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] \\ &= 4 \times 10^{-3} \left[1 - \left(\frac{-2}{-5} \right) \right] \\ &= 4 \times 10^{-3} \left[\frac{3}{5} \right] \end{aligned}$$

$$\boxed{g_m = 2.4 \times 10^{-3} \text{ S}}$$

2) Determine the drain current I_{DS} , g_m and g_{m0} when a JFET has $V_p = -5V$, $I_{DSS} = 8mA$ and $V_{GS} = -2.5V$

Sol: Given data:

$$I_{DSS} = 8mA$$

$$V_p = -5V$$

$$V_{GS} = -2.5V$$

$$\begin{aligned} I_{DS} &= I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2 \\ &= 8 \times 10^{-3} \left[1 - \left(\frac{-2.5}{-5} \right) \right]^2 \\ &= 8 \times 10^{-3} \left[1 - \frac{1}{2} \right]^2 \\ &= 8 \times 10^{-3} \left(\frac{1}{2} \right) \\ &= 2 \times 10^{-3} \end{aligned}$$

$$\boxed{I_{DS} = 2mA}$$

$$\begin{aligned} g_{m0} &= \frac{-2I_{DSS}}{V_p} \\ &= \frac{(-2)(8 \times 10^{-3})}{(-5V)} \end{aligned}$$

$$\boxed{g_{m0} = 3.2 \times 10^{-3} \text{ } \Omega^{-1}}$$

$$\begin{aligned} g_m &= g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] \\ &= 3.2 \times 10^{-3} \left[1 - \left(\frac{-2.5}{-5} \right) \right] \\ &= 3.2 \times 10^{-3} \left(1 - \frac{1}{2} \right) \end{aligned}$$

$$g_m = 3.2 \times 10^{-3} \left(\frac{1}{2} \right)$$

$$\boxed{g_m = 1.6 \times 10^{-3} \text{ } \Omega^{-1}}$$

3) Calculate the values of V_{GS} and V_P when a FET has drain current of 4 mA . If I_{DSS} is 8 mA and $V_{GS(off)}$ is -6 V

Sol Given data $I_D = 4\text{ mA}$

$$I_{DSS} = 8\text{ mA}$$

$$V_{GS(off)} = -6\text{ V}$$

$$\sqrt{\frac{I_D}{I_{DSS}}} = 1 - \frac{V_{GS}}{V_{GS(off)}}$$

$$V_{GS} = \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) V_{GS(off)}$$

$$= \left(1 - \sqrt{\frac{4 \times 10^{-3}}{8 \times 10^{-3}}}\right) (-6\text{ V})$$

$$\boxed{V_{GS} = -1.75\text{ V}}$$

$$V_P = V_{GS(off)}$$

$$\boxed{V_P = -6\text{ V}}$$

4) Determine the pinch-off voltage for an N-channel silicon FET with a channel width of $5.6 \times 10^{-4}\text{ cm}$ and a donor concentration of $10^{15}/\text{cm}^3$. Given the dielectric constant of Si is 12.

Sol Given data: $V_P = \frac{q N_D \alpha^2}{2\epsilon} = \text{Formula}$

$$\underline{\text{Given data:}} \quad N_D = 10^{15}/\text{cm}^3$$

$$\alpha = 5.6 \times 10^{-4}\text{ cm}$$

$$\epsilon_r = 12$$

$$\text{let } q = 1.6 \times 10^{-19}\text{ C}$$

$$\epsilon = \epsilon_r \cdot \epsilon_0$$

$$\therefore \epsilon_0 = 8.85 \times 10^{-14}\text{ F/cm}$$

$$\epsilon = 12 \times 8.85 \times 10^{-14}$$

$$\epsilon = 1.062 \times 10^{-12}\text{ F/cm}$$

$$V_p = \frac{(1.6 \times 10^{-19})(10^{15})(5.6 \times 10^{-4})}{(2)(1.062 \times 10^{-12})}$$

$$= \frac{5.0176 \times 10^{-11}}{2.124 \times 10^{-12}}$$

$$V_p = 23.63 \text{ V}$$

- 5) Determine drain current when V_{GS} is -1.5 V in N channel JFET I_{DSS} is 10 mA and V_p is -33 V .

Sol

Given data

$$V_{GS} = -1.5 \text{ V}$$

$$I_{DSS} = 10 \text{ mA}$$

$$V_p = -33$$

$$I_{DS} = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$$

$$= 10 \times 10^{-3} \left[1 - \left(\frac{-1.5}{-33} \right) \right]^2$$

$$= 10 \times 10^{-3} [1 - 0.045]^2$$

$$= 10 \times 10^{-3} (0.955)^2$$

$$= 10 \times 10^{-3} (0.912)$$

$$= 9.12 \times 10^{-3}$$

$$I_{DS} = 9.12 \text{ mA.}$$

- 6) Determine the value of transconductance at V_{GS} is -4 V of the N-channel JFET has I_{DSS} is 20 mA , V_p is -8 V and g_{m0} is $5000 \mu\text{S}$.

Sol: Given data: $V_{GS} = -4 \text{ V}$

$$I_{DSS} = 20 \text{ mA}$$

$$V_p = -8 \text{ V}$$

$$g_{m0} = 5000 \mu S$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$

where g_{m0} = maximum transconductance

$$g_m = 5000 \times \left(1 - \left(\frac{-4}{-8} \right) \right)$$

$$= 5000 \times \left(1 - \frac{1}{2} \right)$$

$$= 5000 \left(\frac{1}{2} \right)$$

$$\boxed{g_m = 2500 \mu S}$$

∴ transconductance $g_m = 2500 \mu S$

7) Determine the trans conductance of a JFET its amplification factor is 94 and drain resistance is $30 k\Omega$

Sol Given data

$$\mu = 94$$

$$R_D = 30 k\Omega = 30 \times 1000 \Omega$$

$$\text{transconductance } g_m = \frac{\mu}{R_D}$$

$$= \frac{94}{30000}$$

$$\boxed{g_m = 3.13 k\Omega}$$

8) Determine the output voltage of a NMOS transistor in a circuit has a supply voltage of 5V and a drain resistance of $1 k\Omega$, If the drain current is 2mA.

Sol: Given data

$$\text{supply voltage } V_{DD} = 5V$$

$$\text{Drain resistance } R_D = 1 k\Omega$$

$$\text{Drain current } (I_D) = 2 \text{ mA}$$

By ohm law

$$V_{out} = V_{DD} - (I_D \times R_D)$$

$$= 5 \text{ V} - (2 \text{ mA} \times 1 \text{ k}\Omega)$$

$$V_{out} = 5 \text{ V} - 2 \text{ V}$$

$$V_{out} = 3 \text{ V}$$

9) Build an appropriate biasing circuit using with V_{DD} is 30V of JFET is to be operated at a quiescent point defined by I_D is 4mA. V_{DS} is 8V and V_{GS} is -2V.

Given data $V_{DD} = 30 \text{ V}$

$$I_D = 4 \text{ mA}$$

$$V_{DS} = 8 \text{ V}$$

$$V_{GS} = -2 \text{ V}$$

Loop eqn

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DD} = I_D R_D + V_{DS} + I_D R_S$$


$$V_{DD} = (R_D + R_S) I_D + V_{DS}$$

$$R_D = \frac{V_{DD} - V_{DS} - I_D R_S}{I_D} \quad \text{--- (1)}$$

But $R_S = \frac{V_S}{I_D}$

$$= \frac{-V_{GS}}{I_D}$$
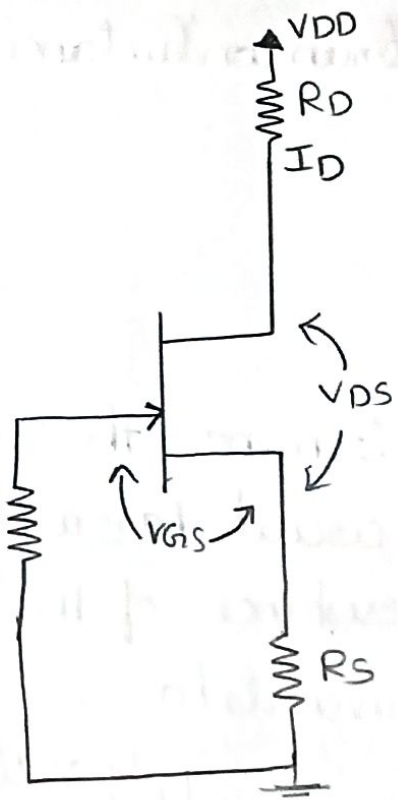
$$R_S = \frac{2}{4 \times 10^{-3}} = 500 \Omega$$



From eq ① $R_D = \frac{30 - 8 - (4 \times 10^{-3} \times 500)}{4 \times 10^{-3}}$

$$R_D = 5000 \Omega$$


$$R_D = 5k\Omega$$

R_G is very large. then

$$R_G = 1M\Omega$$

To build an appropriate biasing circuit of JFET we need $V_{DD} = 30V$, $I_D = 4mA$, $V_{DS} = 8V$, $V_{GS} = -2V$
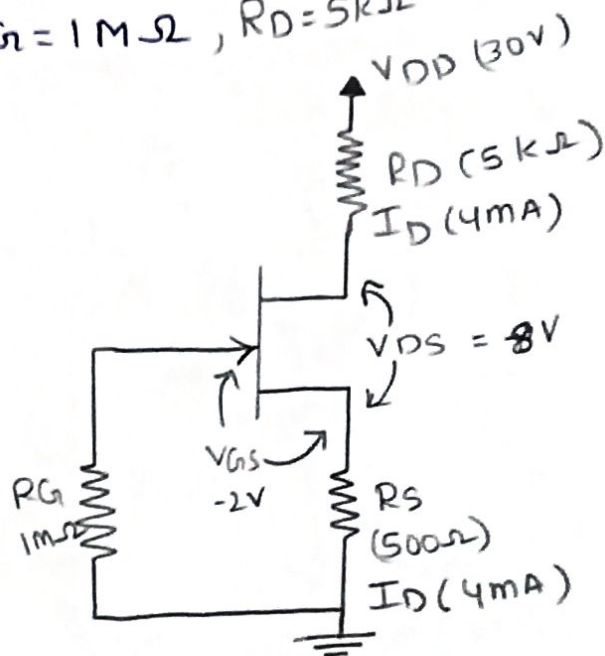
$$R_S = 500\Omega, R_G = 1M\Omega, R_D = 5k\Omega$$



- 10) Calculate the energy consumed per switching cycle of BI MOS gate drives a load capacitance of $20pF$ with a supply voltage $5V$

Given data

$$C_L = 20pF$$

$$V_{DD} = 5V$$

$$\text{Energy } E = \frac{1}{2} C_L V_{DD}^2$$

$$E = \frac{1}{2} \times 20 \times 10^{-12} \times (5)^2$$

$$= 10 \times 10^{-12} \times 25$$

$$E = 250 \times 10^{-12}$$

$$E = 250 \text{ pJ}$$

Unit-4

- 1 Calculate the collector current and collector to Emitter voltages values in the fixed-bias compensation method of transistor with $\beta = 100$ are used V_{CC} is 9V R_C is $3k\Omega$, R_B is $530k$ and $V_{BE} = 0.7V$.

Sol:


Given $\beta = 100$

$$R_C = 3k\Omega$$

$$R_B = 530k$$

$$V_{CC} = 9V$$

$$V_{BE} = 0.7V$$

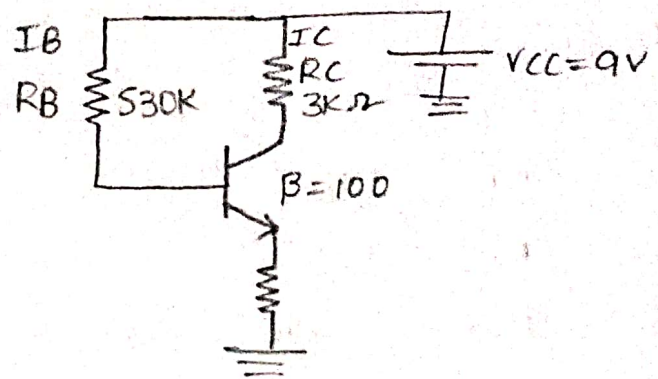

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B R_B = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{9 - 0.7}{530} = \frac{8.3}{530} = 0.015 = 15.66 \mu A$$

$$I_{CQ} = \beta I_B$$

$$= 100 (15.66 \times 10^{-6})$$

$$= 1.566 mA$$

Note: R_B is $530k$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 9 - (1.566 \times 10^{-3}) (300 \times 10^3)$$

$$= 9 - 469.8$$

$$= -460.8$$

2. Determine the h parameters for CC configuration with the help of h parameters for CE configuration are h_{ie} is 2600Ω , h_{fe} is 100, h_{re} is 0.02×10^{-2} and h_{oe} is $5 \times 10^{-6} \text{ A/V}$.

Sol: Given

$$h_{ie} = 2600\Omega$$

$$h_{fe} = 100$$

$$h_{re} = 0.02 \times 10^{-2} = 0.0002$$

$$h_{oe} = 5 \times 10^{-6} \text{ A/V}$$

1. Input impedance (h_{ic})

$$h_{ic} = h_{ie} + \frac{1 + h_{fe}}{h_{oe}}$$

$$= 2600 + \frac{1 + 100}{5 \times 10^{-6}} = 2600 + \frac{101}{5 \times 10^{-6}}$$

$$= 20.2 \text{ M}\Omega$$

2. Forward current gain (h_{fc})

$$h_{fc} = \frac{h_{fe}}{1 + h_{fe}} = \frac{100}{1 + 100} = \frac{100}{101} = 0.9901$$

3. Reverse voltage gain (h_{rc})

$$h_{rc} = \frac{h_{re}}{1 + h_{fe}} = \frac{0.0002}{101} = 1.98 \times 10^{-6}$$

4. Output impedance (h_{oc})

$$h_{oc} = h_{oe}$$

$$= 5 \times 10^{-6} \text{ A/V}$$

3. Determine the quiescent point in an NPN transistor, if β is 50 used in common emitter circuit with V_{CC} is 10V and R_C is $2k\Omega$. The bias is obtained by connecting $100k\Omega$ resistor from collector to base.


Sol:

Given $\beta = 50$

$$V_{CC} = 10V$$

$$R_C = 2k\Omega$$

$$R_B = 100k\Omega$$

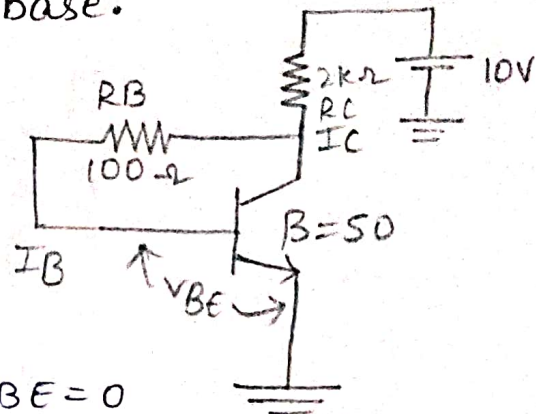

$$V_{CC} - R_C(I_C + I_B) - R_B I_B - V_{BE} = 0$$

$$V_{CC} - R_C[\beta I_B + I_B] - R_B I_B - V_{BE} = 0$$

$$V_{CC} - R_C I_B [1 + \beta] - R_B I_B - V_{BE} = 0$$

$$V_{CC} - V_{BE} = I_B [R_C (1 + \beta) + R_B]$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_C (1 + \beta) + R_B} = \frac{10 - 0.7}{2 \times 10^3 (51) + 100 \times 10^3}$$

$$= \frac{9.3}{202000} = 0.046 \times 10^{-3}$$

$$I_C = \beta I_B$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_{CQ} = \beta I_B = 50 \times 0.046 \times 10^{-3} = 2.3 \times 10^{-3} = 2.3mA$$

$$V_{CC} - R_C(I_C + I_B) - V_{CE} = 0$$

$$V_{CC} - R_C[\beta I_B + I_B] - V_{CE} = 0$$


$$V_{CEQ} = V_{CC} - R_C[\beta I_B + I_B]$$

$$= V_{CC} - R_C I_B (1 + \beta)$$

$$= 10 - (2 \times 10^3)(0.046 \times 10^{-3})(51)$$

$$= 10 - 4.692$$

$$= 5.3V$$

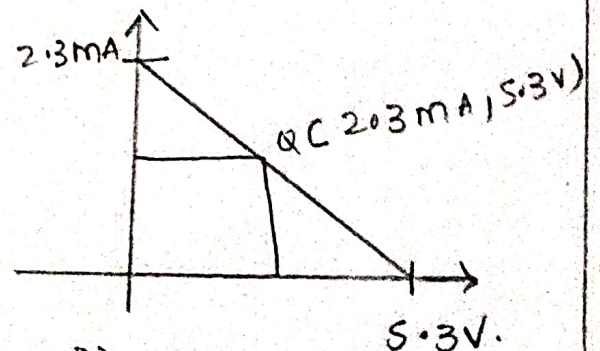

4. Examine the operating point in a silicon transistor with a fixed bias, $V_{CC} = 9V$, $R_C = 3k\Omega$, $R_B = 1M\Omega$, $\beta = 200$, $V_{BE} = 0.7V$

Sol: Given

$$V_{CC} = 9V$$


$$R_B = 1M\Omega$$

$$R_C = 3k\Omega$$

$$V_{BE} = 0.7V$$

$$\beta = 200$$

circuit diagram

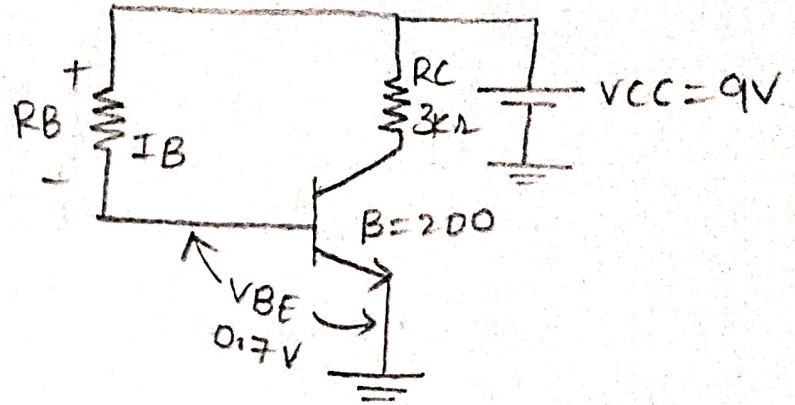

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$V_{CC} - V_{BE} = I_B R_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{9 - 0.7}{1 \times 10^6} = 8.3 \times 10^{-6} \text{ Amp}$$

$$I_B = 8.3 \mu\text{Amp}$$

$$I_C = \beta I_B = 200 \times (8.3 \times 10^{-6}) = 1.6 \times 10^{-3} \text{ Amp}$$


$$I_{CQ} = 1.6 \times 10^{-3} \text{ Amps}$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 9 - (1.6 \times 10^{-3})(3 \times 10^3)$$

$$V_{CE} = 4.2V$$

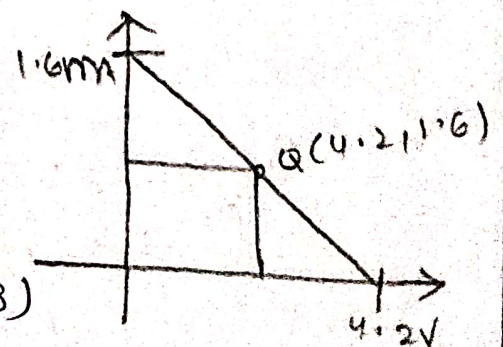

$$S = 1 + \beta$$

$$= 1 + 200 = 201$$

5. Determine the R_E value of a silicon transistor with β is 100 is to be used in self bias circuit such that Q point corresponds to V_{CE} is 12V, I_C is 2mA, V_{CC} is 24V and R_C is $5k\Omega$

Sol: Given

$$V_{CE} = 12V$$

$$I_C = 2mA$$


$$V_{CC} = 24V$$

$$R_C = 5k\Omega$$

$$\beta = 100$$

$$I_B = \frac{I_C}{\beta} = 0.02mA$$

$$I_E = I_B + I_C = 0.02 + 2 = 2.02mA$$

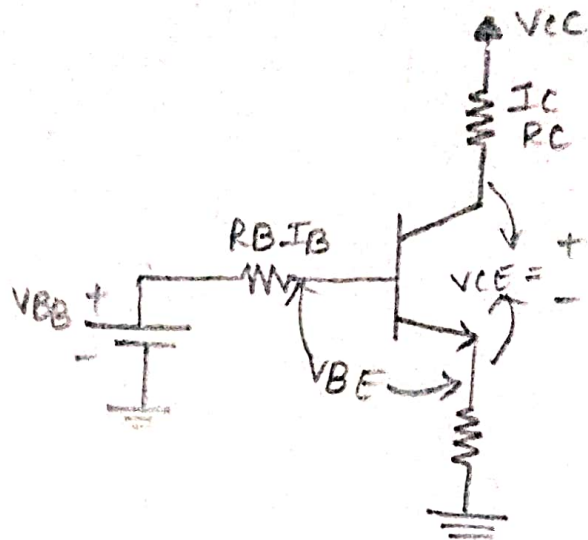

WKT

$$V_{CEQ} = V_{CC} - I_C R_C - I_E R_E$$

$$R_E = \frac{V_{CC} - I_C R_C - V_{CEQ}}{I_E}$$

$$R_E = \frac{24 - 2 \times 10^{-3} \times 5 \times 10^3 - 12}{2.02 \times 10^{-3}}$$



$$= \frac{24 - 10 - 12}{2.02 \times 10^{-3}}$$

$$= \frac{2}{2.02 \times 10^{-3}}$$

$$= 990.09\Omega$$

$$= 0.99k\Omega$$

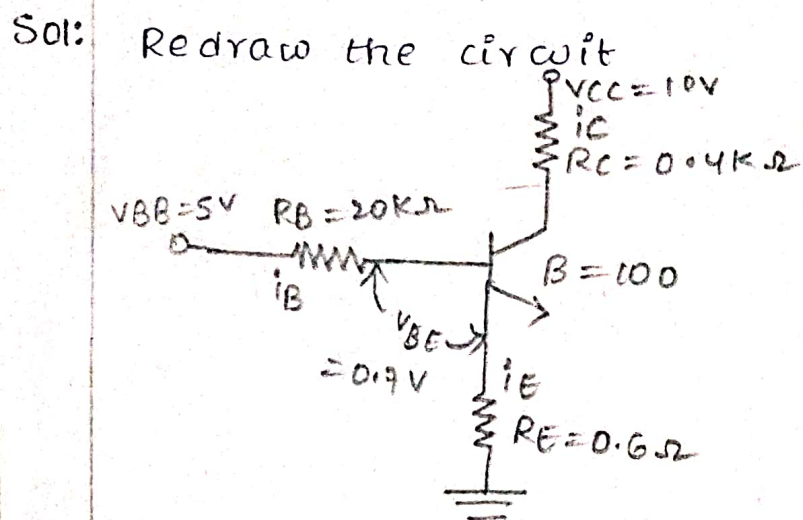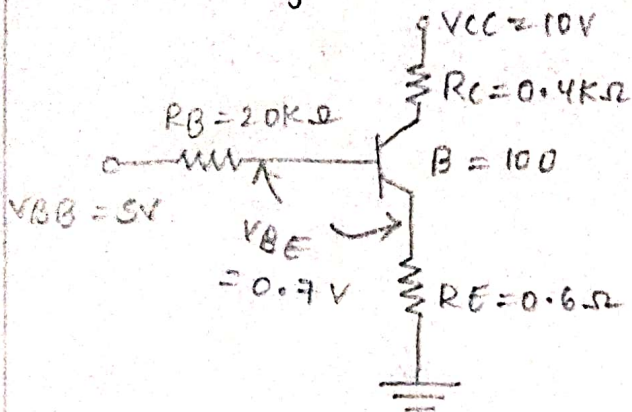6. Determine the Q-point values of as shown in following circuit diagram assume that $\beta = 100$ and V_{BE} is $0.7V$.



Given

$$V_{BB} = 5V, R_B = 20k\Omega, R_C = 0.4k\Omega$$

$$\beta = 100, R_E = 0.6\Omega, V_{BE} = 0.7V$$

By applying KVL

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

$$I_E = I_B + I_C = I_B + \beta I_B$$

$$= (1 + \beta) I_B$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$= \frac{5 - 0.7}{20 \times 10^3 + 101(600)} = \frac{4.3}{80600}$$

$$= 53.34 \mu A$$

$$I_C = \beta I_B = 100 (53.34 \times 10^{-6}) = 5.334 \text{ mA}$$


$$I_E = I_C + I_B = 5.334 \times 10^{-3} + 53.34 \times 10^{-6} = 5.3874$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 10 - 5.334 \times 10^{-3} \times 400 - 5.38734 \times 10^{-3} \times 600$$

$$= 4.634 V$$

The Q point is at $V_{CEQ} = 4.634V$ and $I_{CQ} = 5.334 \text{ mA}$.

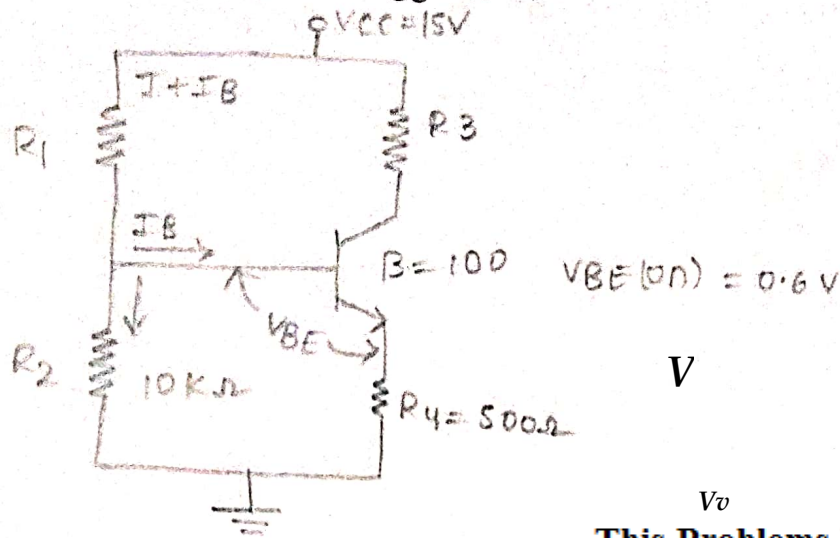7. Calculate R_1 and R_3 as shown in the following circuit, I_B I_C is 2mA and V_{CE} is 3V.



This Problems Discussed in the Notes

Sol:

Given

$$V_{CC} = 15V$$

$$\beta = 100$$

$$V_{BE(on)} = 0.6V$$

$$R_4 = 500\Omega$$

$$R_2 = 10k\Omega$$

$$I_C = 2mA$$

$$V_{CE} = 3V$$


I_B is negligible
assumption $I_B = I_C$

$$R_1 = \frac{V_{CC} - V_{BE}}{I_B}$$

$$= \frac{15 - 0.6}{2 \times 10^{-3}} = \frac{14.4}{2 \times 10^{-3}} = 7200$$

$$R_3 = \frac{V_{CE}}{I_C} = \frac{3V}{2mA} = \frac{3}{2 \times 10^{-3}} = 1500$$

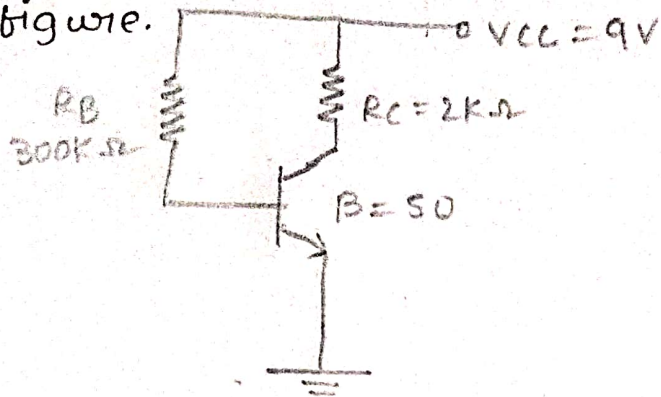8. Calculate the collector current and collector to emitter voltage for the given circuit as shown in following figure.



Sol: Given $V_{CC} = 9V$
 $R_C = 2k\Omega$
 $\beta = 50$
 $R_B = 300k\Omega$

$$I_C = \beta I_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$
$$= \frac{9 - 0.7}{300 \times 10^3} = \frac{8.3}{300 \times 10^3} = 0.0277 \text{ mA}$$

$$I_C = 50 \times 0.0277 \times 10^{-3} = 1.385 \times 10^{-3}$$
$$= 1.385 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C \times R_C$$
$$= 9 - (1.385 \times 10^{-3}) (1 \times 10^3)$$
$$= 7.615 \text{ V}$$

∴ Collector current = 1.385 mA

collector to emitter voltage = 7.615 V

9. Determine current gain, input impedance and voltage gain of CE transistor amplifier is characterized by h_{ie} is $2k$, h_{re} is 2×10^{-4} , h_{fe} is 50 and h_{oe} is $2 \times 10^{-6} A/V$ if load resistance is $4k$ and the source resistance is 200Ω

Sol: Given $h_{ie} = 2k\Omega$
 $h_{re} = 2 \times 10^{-4}$
 $h_{fe} = 50$
 $h_{oe} = 20 \times 10^{-6} A/V$
 $R_L = 4k\Omega$
 $R_S = 200\Omega$

$$\text{current gain } (A_i) = \frac{-h_{fe}}{1 + h_{oe}R_L} = \frac{-50}{1 + (20 \times 10^{-6})(4 \times 10^3)}$$

$$= \frac{-50}{1.08} = -46.29$$

$$\text{Input impedance } (Z_i) = \frac{h_{ie} - h_{re}h_{fe}R_L}{1 + h_{oe}R_L}$$

$$= \frac{2 \times 10^3 - (2 \times 10^{-4})(50)(4 \times 10^3)}{1 + (20 \times 10^{-6})(4 \times 10^3)}$$

$$= 2 \times 10^3 - 37.03$$

$$= 1962.97\Omega$$

$$\text{Voltage gain } (A_v) = \frac{-h_{fe}R_L}{h_{ie} + R_L \Delta h}$$

$$\Delta h = h_{oe}h_{ie} - h_{re}h_{fe} = (20 \times 10^{-6})(2 \times 10^3) - (2 \times 10^{-4})(50)$$


$$= 0.03$$

$$A_v = \frac{-(50)(4 \times 10^3)}{(2 \times 10^3) + (4 \times 10^3)(0.03)} = \frac{200000}{2120} = 94.33$$

10. Draw the DC load line and locate the operating point for fixed biasing transistor values $R_B = 820\text{k}\Omega$ $R_C = 4.7\text{k}\Omega$ $V_{CC} = 15\text{V}$ and $\beta = 120$

Sol: Given $R_B = 820\text{k}\Omega$
 $R_C = 4.7\text{k}\Omega$
 $V_{CC} = 15\text{V}$
 $\beta = 120$

Circuit diagram:

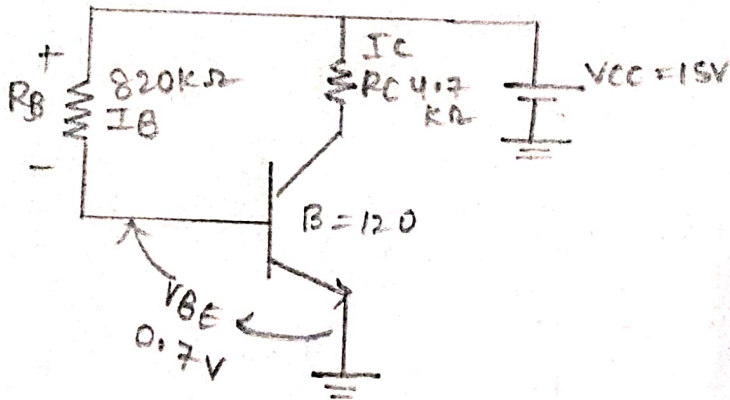

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{15 - 0.7}{820 \times 10^3} = \frac{14.3}{820 \times 10^3} = 17.44 \times 10^{-6}$$


$$I_C = \beta I_B = 120 \times (17.44 \times 10^{-6}) = 2.09 \times 10^{-3} = 2.09\text{mA}$$

$$I_{CQ} = 2.09\text{mA}$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 15 - (2.09 \times 10^{-3}) (4.7 \times 10^3) \\ &= 15 - 9.8 \end{aligned}$$

$$V_{CEQ} = 5.6\text{V}$$

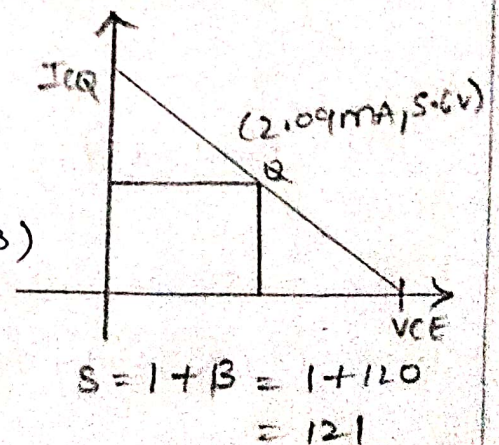

1B)

Calculate the input impedance, circuit input impedance and output impedance of a small signal amplifier with unbypassed emitter resistor of h_{fe} is 100, h_{ie} is 560 and R_C is 2k and R_B is 600k

Sol:- Given data:-


$$h_{fe} = 100$$

$$h_{ie} = 560$$

$$R_C = 2\text{K}\Omega$$

$$R_B = 600\text{K}\Omega$$

Circuit diagram:-

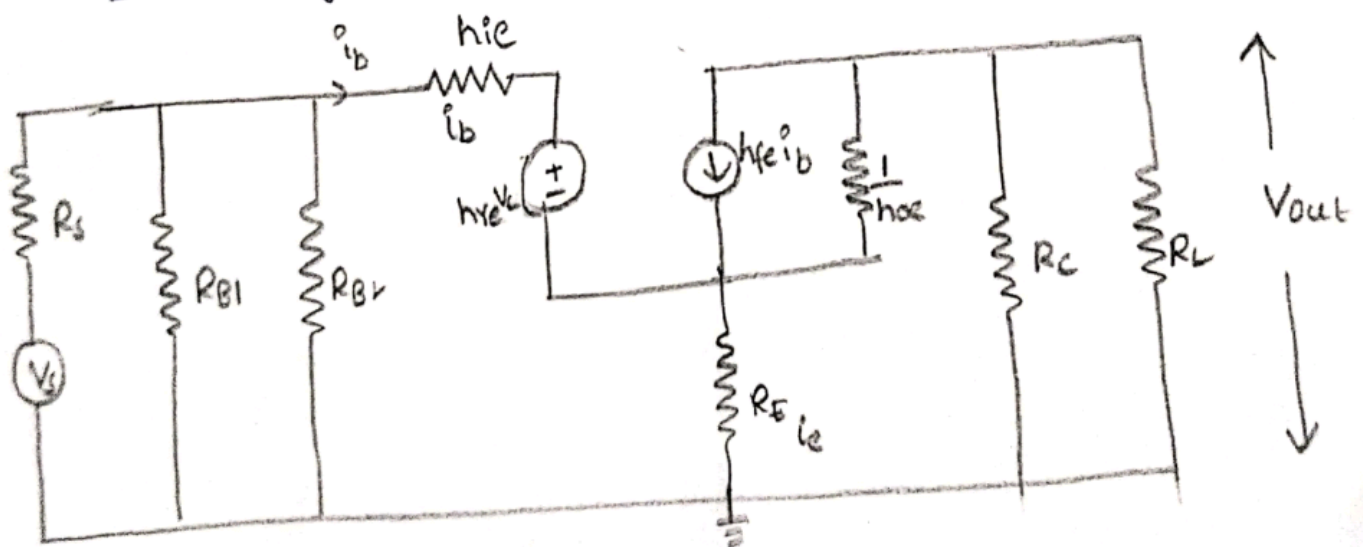

1) input impedance (R_{in}):-

$$R_{in} = h_{ie} + R_E (1 + \beta) \quad [\because R_E = 0]$$

$$R_{in} = h_{ie}$$

$$R_{in} = 560\Omega$$

2) circuit Input Impedance:-

$$Z_{in} = R_B \parallel R_{in}$$

$$= \frac{R_B R_{in}}{R_B + R_{in}}$$

$$= \frac{(600 \times 10^3)(560)}{(600 \times 10^3) + 560}$$

$$Z_{in} = 554.5 \Omega$$

3) output impedance :-

$$Z_{out} = R_c$$

$$Z_{out} = 2 k\Omega$$

3b) Determine the input resistance, current gain and voltage gain of a CE transistor amplifier has the following characteristics h_{ie} is 1000, h_{fe} is 50, h_{re} is 2.5×10^{-4} and h_{oe} is $25 \times 10^{-6} \text{ A/V}$ if the load resistance is R_L is 10K and source resistance R_s is 100.

Sol:-

Given data:-

$$h_{ie} = 1000 \Omega$$

$$h_{fe} = 50$$


$$h_{re} = 2.5 \times 10^{-4}$$

$$h_{oe} = 25 \times 10^{-6} \text{ A/V}$$

$$R_L = 10 \text{ K}$$

$$R_s = 100 \Omega$$

Circuit diagram:-

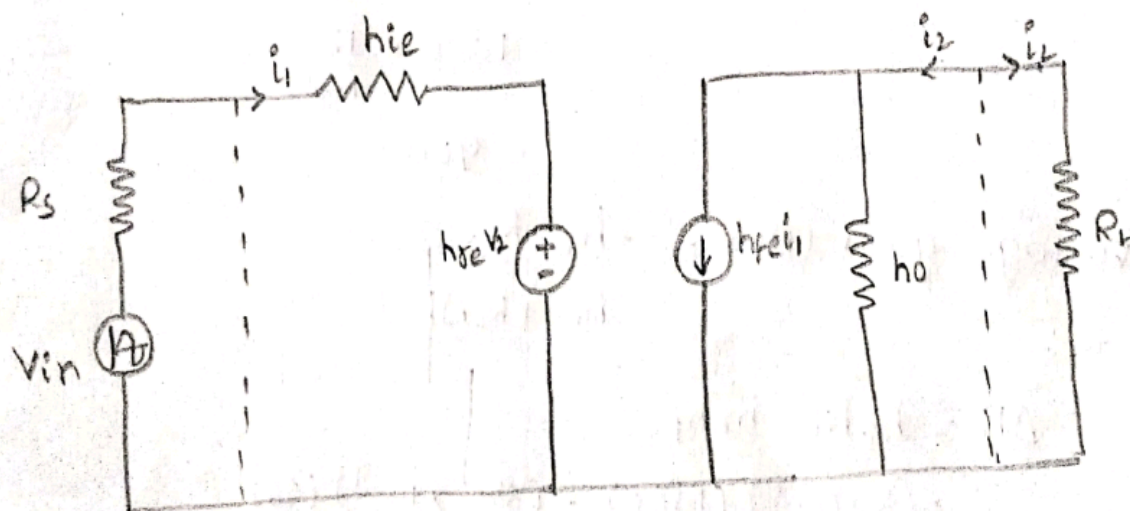

Formulas:-

$$\text{Current gain } (A_i) = \frac{-h_{fe}}{1 + h_{oe}R_L}$$

$$\text{input resistance } (Z_i) = h_{ie} - \frac{h_r h_f R_L}{1 + h_o R_L}$$

output

$$\text{voltage gain } (A_v) = \frac{-h_{fe} R_L}{h_{ie} + R_L \Delta h}$$

$$\begin{aligned} 1) \text{ current gain } (A_i) &= \frac{-h_{fe}}{1 + h_{oe} R_L} \\ &= \frac{-50}{1 + (25 \times 10^{-6})(10 \times 10^3)} \\ &= -40 \end{aligned}$$


$$\begin{aligned} 2) \text{ Input impedance } (Z_i) &= h_{ie} - \frac{h_r h_f R_L}{1 + h_o R_L} \\ &= 1000 - \frac{(2.5 \times 10^{-4})(50)(10 \times 10^3)}{1 + (25 \times 10^{-6})(10 \times 10^3)} \\ &= 1000 - \frac{125}{1 + (250 \times 10^{-3})} \\ &= 1000 - \frac{125}{1.25} \\ &= 900 \end{aligned}$$

$$3) \text{ voltage gain } (A_v) = \frac{-h_{fe} R_L}{h_{ie} + R_L \Delta h}$$

$$\begin{aligned} \Delta h &= h_o h_i - h_r h_f \\ &= (25 \times 10^{-6})(1000) - (2.5 \times 10^{-4})(50) \\ &= 0.025 - 0.0125 \\ &= 0.0125 \end{aligned}$$

$$\begin{aligned} A_v &= \frac{-(50)(10 \times 10^3)}{1000 + (10 \times 10^3)(0.0125)} \\ &= -444.4 \end{aligned}$$

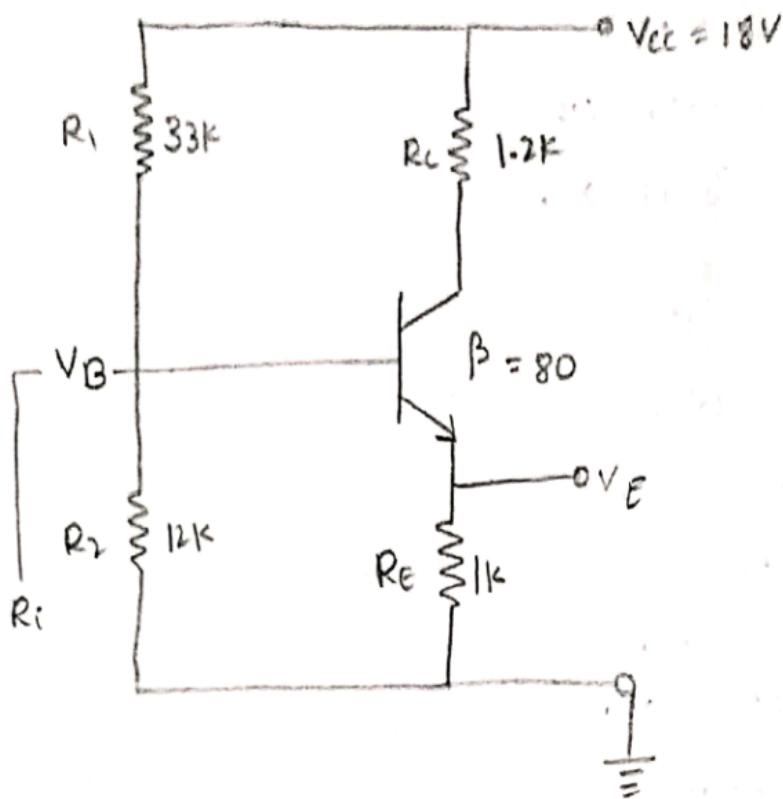4a) Calculate the I_C , V_E , V_B , V_{CE} , R_{in} for the voltage divider bias circuit as shown in below.



Sol:- Given Data:-

$$R_1 = 33k$$

$$R_2 = 12k$$

$$R_C = 1.2k$$


$$R_E = 1k$$

$$V_{CC} = 18V$$

$$\beta = 80$$

$$V_{BE} = 0.7$$

Circuit diagram:-

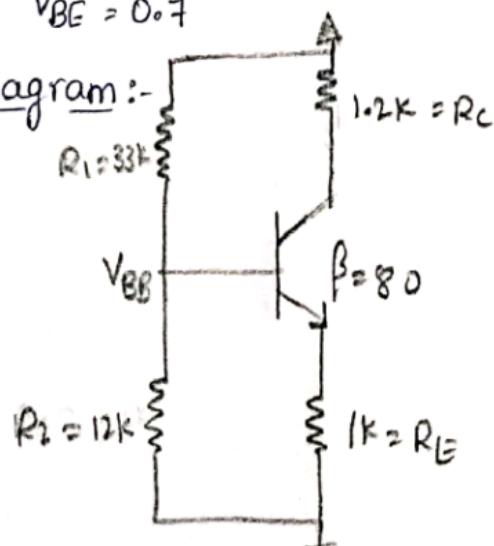

Formula

$$\begin{aligned} 1) \quad V_{BB} &= \frac{R_2 V_{CC}}{R_1 + R_2} \\ &= \frac{(12 \times 10^3)(18)}{(33 + 12) \times 10^3} \\ &= \frac{216}{45} \\ &= 4.8 \text{ V} \end{aligned}$$

$$\begin{aligned} R_B &= \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{12 \times 33 \times 10^6}{(12 + 33) \times 10^3} \\ R_B &= 8.8 \text{ K}\Omega \end{aligned}$$


loop Equation,

$$V_{BB} - V_{BE} - i_e R_E = 0$$

$$\begin{aligned} i_e &= \frac{V_{BB} - V_{BE}}{R_E} \\ &= \frac{4.8 - 0.7}{1 \times 10^3} \\ &= 4.1 \text{ mAmp} \end{aligned}$$

We know that
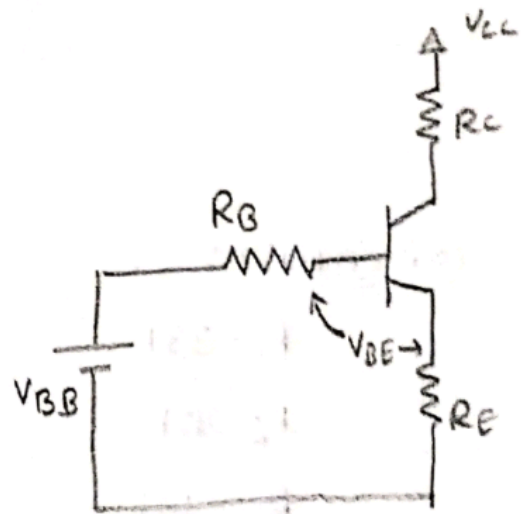
$$\begin{aligned} \alpha &= \frac{\beta}{1 + \beta} \\ &= \frac{80}{1 + 80} \\ \alpha &= 0.98 \\ \alpha &= \frac{i_c}{i_e} \\ i_c &= \alpha i_e \end{aligned}$$



$$(2) \quad i_c = (0.98) \times (4.1)$$

$$\boxed{i_c = 4.01 \text{ mAmp}}$$

3) We know that

$$V_E = i_e R_E$$

$$= 4.1 \times 10^{-3} \times 1 \times 10^3$$

$$\boxed{V_E = 4.1 \text{ V}}$$

$$4) \quad V_{CE} =$$

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CC} - I_C R_C - I_E R_E = V_{CE}$$

$$V_{CE} = 18 - (4.01 \times 10^{-3})(1.2 \times 10^3) - (4.1 \times 10^{-3})(1 \times 10^3)$$

$$= 18 - (4.81) - 4.1$$

$$V_{CE} = 9.088 \text{ V}$$


5)

$$R_{in} = \beta R_E$$

$$= 80 \times 1 \times 10^3$$

$$R_{in} = 80 \text{ k}\Omega$$

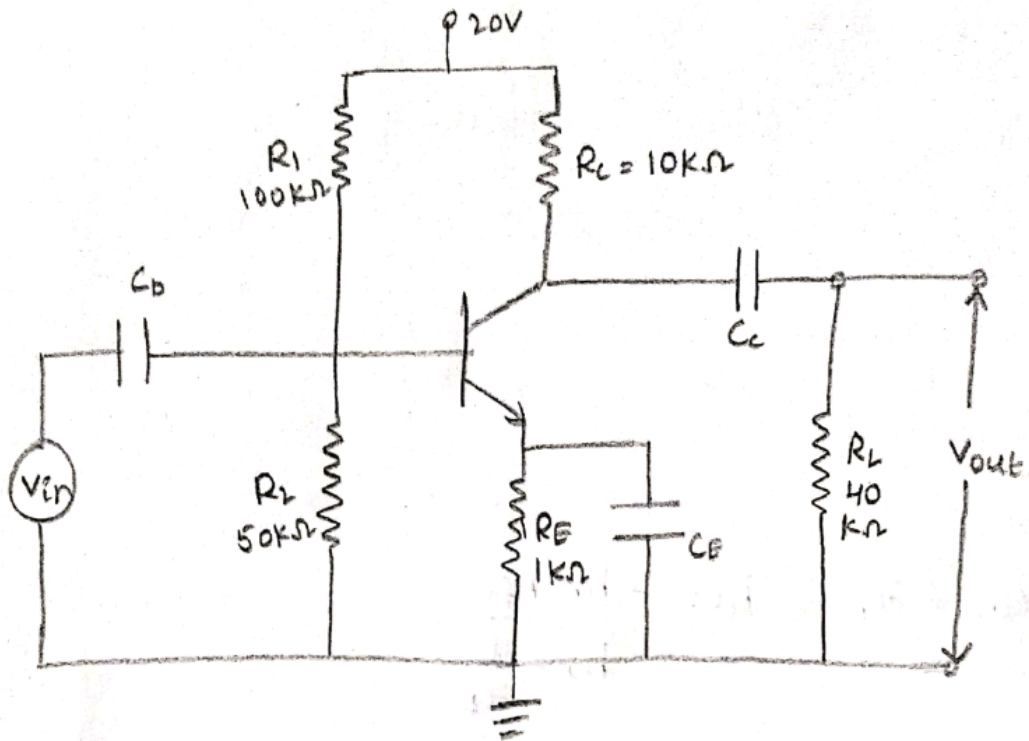4b) calculate Z_{in} , Z_{in} with biasing network and voltage gain of a BJT is given in following figure. The parameters are h_{ie} is 1500, h_{re} is 4×10^{-4} and h_{fe} is 100 and h_{oe} is $4 \times 10^{-4} S$



Sol:- Given Data:-

$$R_1 = 100 k\Omega$$

$$R_2 = 50 k\Omega$$

$$R_E = 1 k\Omega$$

$$R_L = 40 k\Omega$$

$$R_C = 10 k\Omega$$

$$h_{ie} = 1500$$


$$h_{re} = 4 \times 10^{-4}$$

$$h_{fe} = 100$$

$$h_{oe} = 4 \times 10^{-4} S$$

Circuit diagram

Equivalent circuit:-

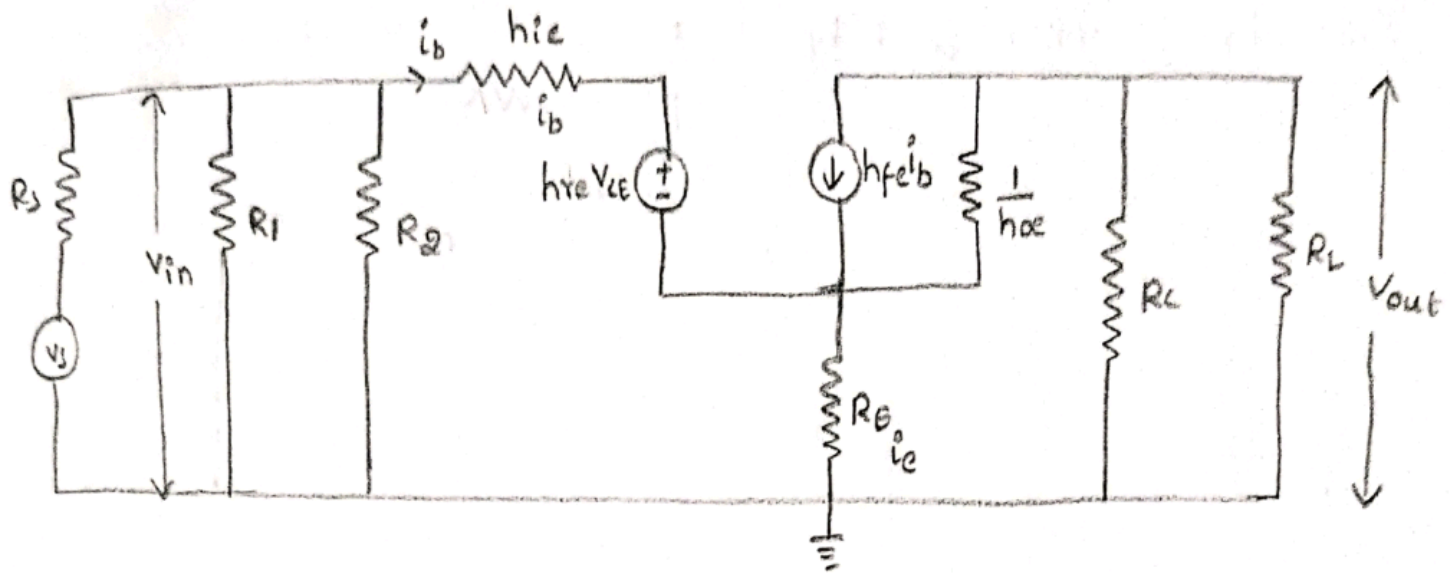

Formulas:-

$$Z_{in} = Z_b = h_{ie} - \frac{h_{re} h_{fe}}{h_{oe} + \frac{1}{Z_L}}$$

$$Z_{feedback} = Z_b \parallel R_1 \parallel R_2$$

$$\text{voltage gain } (A_v) = -\frac{h_{fe}}{h_{ie}} (R_C \parallel R_L)$$

1) input impedance

$$Z_{in} = h_{ie} - \frac{h_{re} h_{fe}}{h_{oe} + \frac{1}{Z_L}}$$

$$= 1500 - \frac{4 \times 10^{-4} \times 100}{4 \times 10^{-4} + \frac{1}{40 \times 10^3}}$$

$$= 1500 - \frac{4 \times 10^{-4} \times 100}{4 \times 10^{-4} + 0.25 \times 10^{-4}}$$

$$= 1500 - \frac{400}{4.25}$$

$$Z_{in} = 1.405 \text{ k}\Omega$$

$$2) \quad Z_{\text{feedback}} = Z_b \parallel R_1 \parallel R_2$$

$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{100 \times 50 \times 10^6}{(100 + 50) \times 10^3}$$

$$= 33.33 \text{ k}\Omega$$

$$Z_{\text{feedback}} = \frac{33.33 \times 10^3 \times 1.405 \times 10^3}{(33.33 + 1.405) \times 10^3}$$

$$= 1.348 \text{ k}\Omega$$

$$3) \quad \text{Voltage gain } (A_v):$$

$$A_v = \frac{-h_{fe}}{h_{ie}} (R_c \parallel R_L)$$

$$= -\frac{100}{1500} \left[\frac{10 \times 40 \times 10^3 \times 10^3}{(10 + 40) \times 10^3} \right]$$

$$= -\frac{1}{15} \left[\frac{10 \times 40 \times 10^3}{50} \right]$$

$$= -533.3$$

$$A_v = -533.3$$

5b) Determine the input impedance, output impedance and voltage gain for the common base circuit values and parameters are $R_1 = 20k$, $R_2 = 5k$, $R_C = 8k$, $R_E = 4k$, $R_L = 6k$, $h_{ib} = 25$, $h_{ob} = 0.5 \times 10^{-6} A/V$ and $h_{fb} = -9.8$

Sol:- Given data:-

$$R_1 = 20k$$

$$R_2 = 5k$$

$$R_C = 8k$$

$$R_E = 4k$$


$$R_L = 6k$$

$$h_{ib} = 25$$

$$h_{ob} = 0.5 \times 10^{-6} A/V$$

$$h_{fb} = -9.8$$

Circuit diagram:-

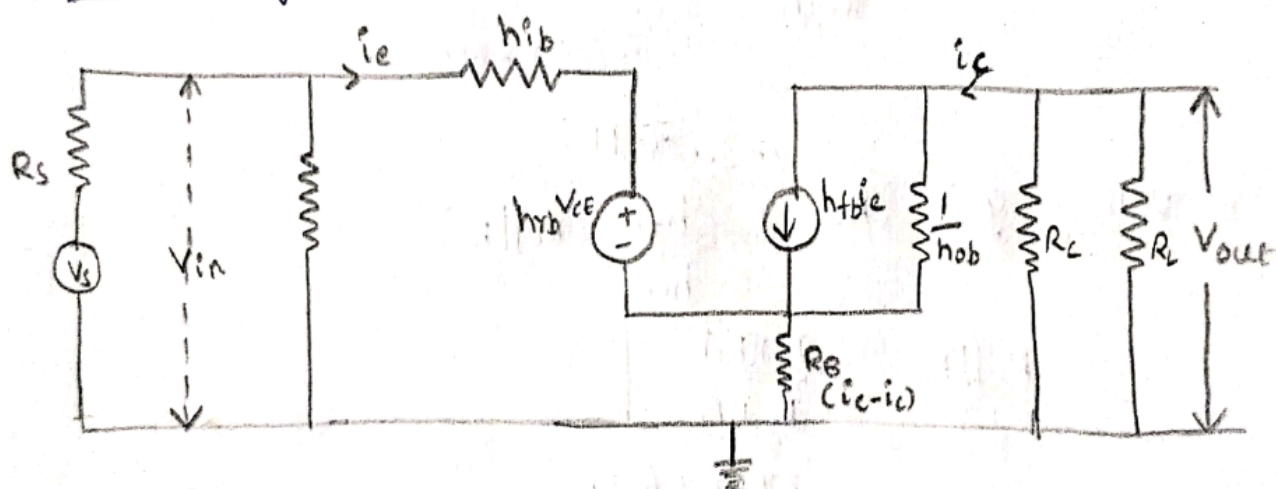

Formulas:-

$$\text{input impedance } (Z_{in}) = Z_E \parallel R_E$$

$$\text{output impedance } (Z_{out}) = \frac{1}{h_{ob}} \parallel R_C$$

$$\text{voltage gain } (A_v) = \frac{-h_{fb}}{h_{ib}} (R_C \parallel R_L)$$

1) input impedance (Z_{in}) = $Z_E \parallel R_E$

$$Z_{in} = \frac{Z_E R_E}{Z_E + R_E} \quad [\because Z_E = h_{ib}]$$

$$Z_{in} = \frac{25 \times 4 \times 10^3}{25 + (4 \times 10^3)}$$

$$= 24.8$$

2) Output impedance (Z_{out}) = $\frac{1}{h_{ob}} \parallel R_L$

$$\frac{1}{h_{ob}} = \frac{1}{0.5 \times 10^{-6}}$$

$$\frac{1}{h_{ob}} = 2 \times 10^6$$

$$Z_{out} = \frac{2 \times 10^6 \times 8 \times 10^3}{2 \times 10^6 + 8 \times 10^3}$$

$$= 7.9 \text{ k}\Omega$$

3) Voltage gain (A_v) = $\frac{-h_{fb}}{h_{ib}} (R_C \parallel R_L)$

$$R_C \parallel R_L = \frac{(R_C)(R_L)}{R_C + R_L}$$

$$= \frac{8 \times 10^3 \times 6 \times 10^3}{14 \times 10^3}$$

$$= 3.428 \text{ k}\Omega$$

$$A_v = \frac{-(-9.8)}{25} (3.428 \text{ k}\Omega)$$

$$= (0.392)(3.428 \times 10^3)$$

$$= 1343$$

6b) compute the Q-point (I_{DQ} and V_{DSQ}) and draw the DC load line of N-channel JFET has R_D is $2K$ I_{DSS} is $10mA$ and V_p is $-4V$ when V_{GS} is $-1.5V$

Sol:- Given;


$$R_D = 2K$$

$$I_{DSS} = 10mA$$

$$V_p = -4V$$

$$V_{GS} = -1.5V$$

Circuit diagram:-

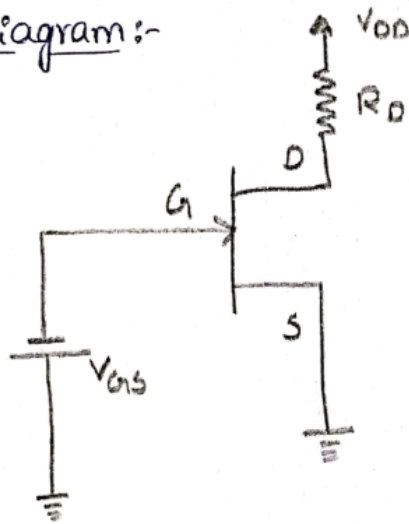


Formula:-

$$\begin{aligned} I_{DQ} &= I_{DSSQ} \left[1 - \frac{V_{GS}}{V_p} \right]^2 \\ &= (10 \times 10^{-3}) \left[1 - \frac{(-1.5)}{(-4)} \right]^2 \\ &= (10 \times 10^{-3}) [1 - 0.375]^2 \\ &= (10 \times 10^{-3}) [0.625]^2 \\ &= (10 \times 10^{-3}) (0.3906) \\ &= 3.906 \times 10^{-3} \end{aligned}$$

$$\boxed{I_{DQ} = 3.906mA}$$

$$\begin{aligned}V_{DSQ} &= V_{DD} - I_{DQ} R_D \\&= 16 - (3.90 \times 10^{-3} \times 2 \times 10^3) \\&= 16 - (3.90 \times 2)\end{aligned}$$

$$V_{DSQ} = 8.2V$$

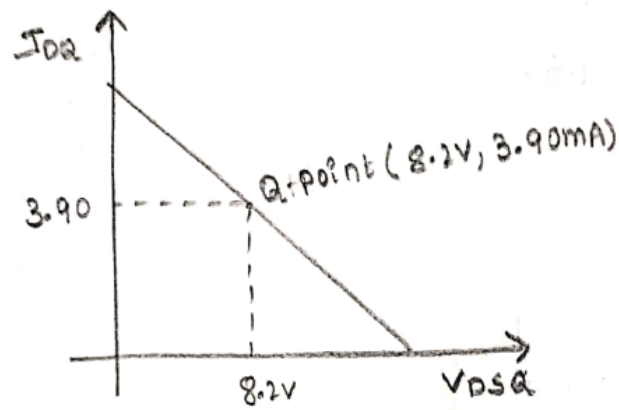

7b) calculate the values of R_D and R_S of JFET amplifier circuit

R_{G1} is $500k$, V_{G1S} is $-1V$, V_{DS} is $4.0V$ and I_{DSS} is $1mA$, V_{DD} is $10V$

Sol:- Given Data:-

$$V_{DD} = 10V$$


$$V_{G1S} = -1V$$

$$V_{DS} = 4V$$

$$I_{DS} = 1mA$$

$$R_{G1} = 500k\Omega$$

Circuit diagram:-

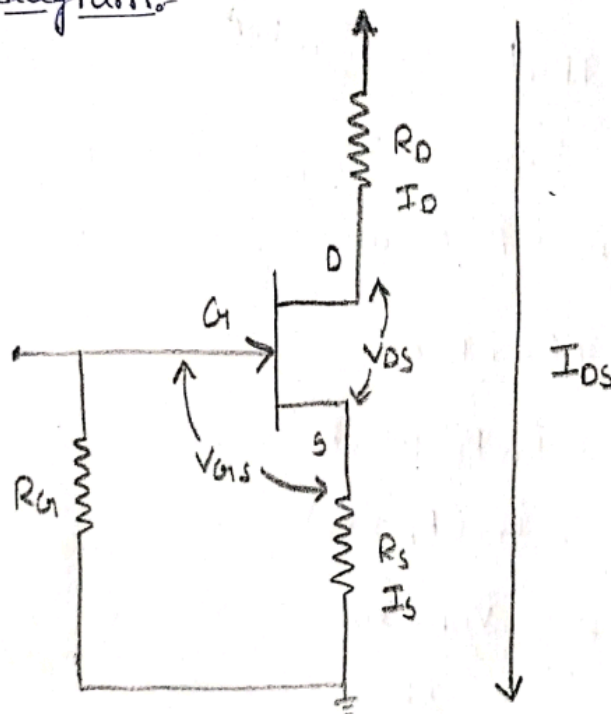

Now,

$$V_{G1S} = -1V$$

$$V_{G1} - V_S = -1V$$

We know that,

$$\begin{aligned} V_{G1} &= i_{G1} R_{G1} \\ &= i_{G1} \times 500 \times 10^3 \\ &= 0 \times 500 \times 10^3 \end{aligned}$$

$$[\because i_{G1} = 0]$$

$$V_{G1} = 0$$

Now

$$V_{G1} - V_S = -1V$$

$$\boxed{V_S = 1V}$$

from ohm's law

$$V_S = i_S R_S$$

$$V_S = i_{ds} R_S$$

$$R_S = \frac{V_S}{i_{ds}}$$

$$= \frac{1}{1 \times 10^{-3}}$$

$$R_S = 1 \times 10^3$$

$$\boxed{R_S = 1k\Omega}$$

from loop equation

$$V_{DD} - i_D R_D - V_{DS} - R_S i_S = 0$$

$$V_{DD} - V_{DS} = i_D R_D + R_S i_S$$

$$V_{DD} - V_{DS} = i_{ds} R_D + i_{ds} R_S$$

$$V_{DD} - V_{DS} = i_{ds} (R_D + R_S)$$

$$R_D + R_S = \frac{V_{DD} - V_{DS}}{i_{ds}}$$

$$R_D = \frac{V_{DD} - V_{DS}}{i_{ds}} - R_S$$

$$= \frac{10 - 4}{1 \times 10^{-3}} - (1 \times 10^3)$$

$$= \frac{6}{1 \times 10^{-3}} - (1 \times 10^3)$$

$$= (6 \times 10^3) - (1 \times 10^3)$$

$$= 5 \times 10^3$$

$$\boxed{R_D = 5k\Omega}$$

8b) calculate voltage gain A_v and output resistance R_o of the common source amplifier, drain resistance (R_D) is 5K , amplification factor (μ) is 50 and r_d is 35K


Sol:- Given data,

$$R_D = 5\text{K}$$

$$r_d = 35\text{K}$$

$$\mu = 50$$

Circuit diagram:-

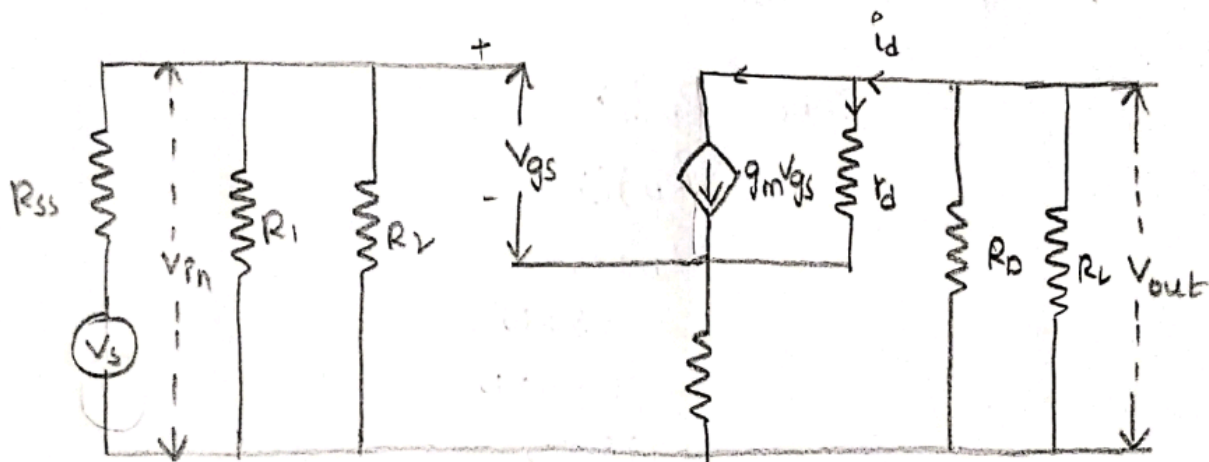

Formulas:-

$$A_v = -g_m (r_d \parallel R_D)$$

$$\text{Output impedance } (R_o) = R_D \parallel r_d$$

1) Voltage gain (A_v):

$$A_v = -g_m (r_d \parallel R_D)$$

$$= \frac{-g_m r_d R_D}{r_d + R_D}$$

$$= \frac{-\frac{\partial I_D}{\partial V_{GS}} \cdot \frac{\partial V_{DS}}{\partial I_D} R_D}{R_D + r_d}$$

$$= -\frac{\mu R_D}{R_D + r_d}$$

$$= -\frac{50 \times (5 \times 10^3)}{(5 + 35) \times 10^3}$$

$$= -\frac{250}{40}$$

$$\boxed{A_v = -6.25}$$

2) Output Resistance (R_o) :-

$$R_o = R_D \parallel r_d$$

$$= \frac{(R_D \cdot r_d)}{R_D + r_d}$$

$$= \frac{35 \times 5 \times 10^6}{(35 + 5) \times 10^3}$$

$$= \frac{175 \times 10^3}{40}$$

$$\boxed{R_o = 4.37 \text{ k}\Omega}$$

9b) Determine the voltage gain of the amplifier of a JFET, The transconductance is $2500 \mu S$ and load resistance is $12k$. Assume r_d and $R_D \ll R_L$

Sol:- Given data:-

$$g_m = 2500 \mu S$$

$$R_L = 12k\Omega$$

Formula:-

$$\text{Voltage gain}(A_v) = -g_m (r_d \parallel R_D \parallel R_L)$$

$$= -g_m R_L \quad [\because R_L \gg R_D]$$

$$= -(2500 \times 10^{-6})(12 \times 10^3)$$

$$= -(2500) \times 10^{-3} \times 12$$

$$A_v = -30$$

10b) Calculate the input impedance, output impedance and voltage gain of the common drain amplifier R_1 is $4M$, R_2 is $2M$, $R_S = 2.5k$ and R_L is $25k$ and g_m is $2500 \mu S$.

Sol:- Given Data:-

$$R_1 = 4M\Omega$$


$$R_2 = 2M\Omega$$

$$R_S = 2.5k\Omega$$

$$R_L = 25k\Omega$$

$$g_m = 2500 \mu S$$

Circuit diagram:-

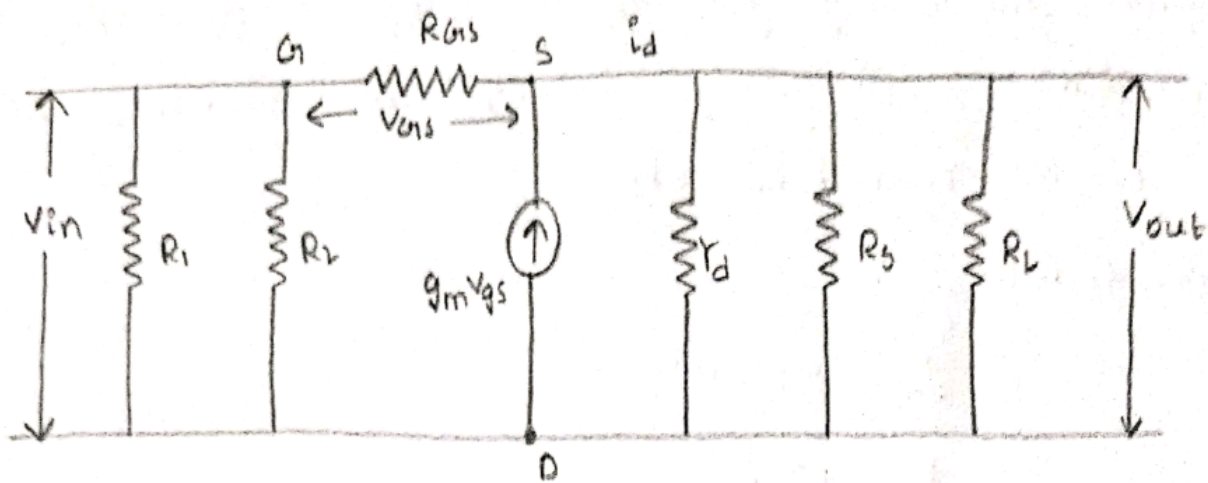

Formulas:-

input impedance :-

$$R_{G1} = \frac{R_1 R_2}{R_1 + R_2}$$

output impedance :-

$$R_{out} = R_S \parallel \frac{1}{g_m}$$

$$\text{voltage gain } (A_v) : \frac{g_m (R_S \parallel R_L)}{1 + g_m (R_S \parallel R_L)}$$

1) Input impedance

$$\begin{aligned} R_{G1} &= \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{4 \times 10^6 \times 2 \times 10^6}{(4 + 2) \times 10^6} \\ &= \frac{8 \times 10^6}{6} \end{aligned}$$

$$R_{G1} = 1.33 \text{ M}\Omega$$

2) output impedance :-

$$R_{out} = R_S \parallel \frac{1}{g_m}$$

$$\begin{aligned} \frac{1}{g_m} &= \frac{1}{2500 \times 10^{-6}} \\ &= 400 \Omega \end{aligned}$$

$$\frac{1}{g_m} = 0.4 \text{ K}\Omega$$

$$\begin{aligned} R_{out} &= \frac{2.5 \times 10^3 \times 0.4 \times 10^3}{(2.5 + 0.4) \times 10^3} \\ &= \frac{2.5 \times 0.4 \times 10^3}{2.9} \end{aligned}$$

$$R_{out} = 0.34 \text{ K}\Omega$$