

GATE 2026 TEST SERIES

Electric Circuits

Test 1

1. The resistance R of a filament lamp is related to the current by the following equation:

$R = 50 + 1200I$ ohm, where I is the current (A).

What is the value of the resistance(in Ω) ,when a voltage of 240V is applied to the lamp?

Correct Answer: **563**

Answer Range: **(560 , 565)**

Not Attempted : 

Marks : 2 / 0 (-Ve)


$$V = IR = I(50 + 1200I), \therefore 240 = 50I + 1200I^2$$

$$\text{or } I = \frac{-5 \pm \sqrt{25 + 11,520}}{240} = \frac{-5 \pm 107.45}{240}$$

$$\text{Taking the positive root, } I = \frac{102.45}{240} = 0.427\text{A},$$

$$R = \frac{240}{0.427} = 563\Omega$$

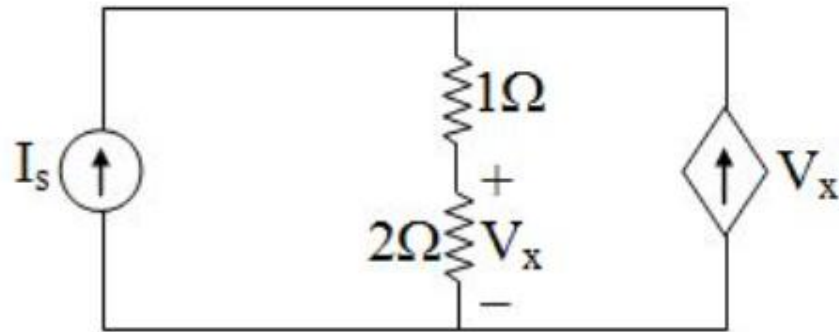2. The equivalent resistance R_{eq} (in Ω) seen by the current source I_s is ____.




Correct Answer: -3

Answer Range: (-3 , -3)

Not Attempted : !

Marks : 2 / 0 (-Ve)

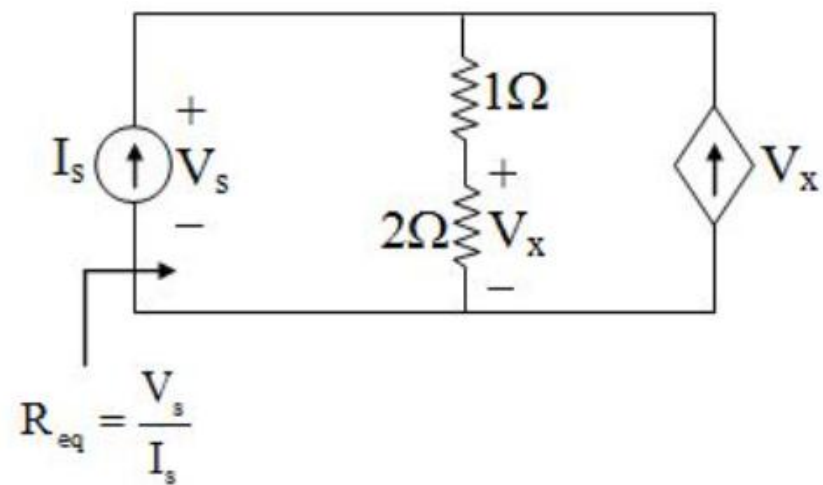

Hence

$$V_s = V_x + \frac{V_x}{2} = \frac{3}{2} V_x$$

$$2[I_s + V_x] = V_x$$

$$2I_s + 2V_x = V_x$$

$$2I_s = -V_x$$

$$V_x = -2I_s$$

$$\text{So, } V_s = \frac{3}{2} [-2I_s] \Rightarrow R_{eq} = \frac{V_s}{I_s} = -3\Omega$$

$$\text{So, } R_{eq} = -3\Omega$$

3. A steady voltage of 100V is applied to a 2-H inductor. What is the value of energy stored after 10sec, given that the current at $t = 0$ was zero?

- A) 5kJ
- B) 2.5kJ
- C) 0.25MJ
- D) 1MJ

Correct Answer: C

Not Attempted : !


Marks : 1 / 0.33 (-Ve)

$$i(10) = \frac{1}{L} \int_0^{10} v(t) dt + i(0)$$
$$= \frac{1}{2} \int_0^{10} 100 dt, \text{ since } i(0)=0$$

$$= \frac{1}{2} [100t]_0^{10} = 500A.$$

$$W = \frac{1}{2} LI^2$$
$$= \frac{1}{2} \times 2 \times 500^2 = 0.25MJ.$$

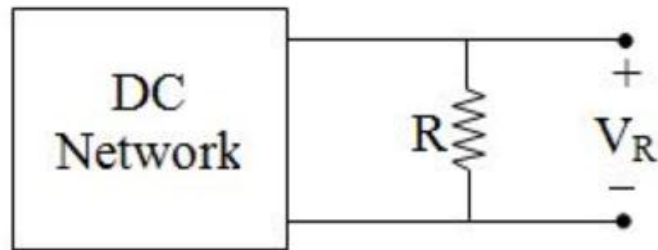4. For circuit shown in figure $V_R = 20V$ when $R = 10\Omega$ and $V_R = 30V$, when $R = 20\Omega$. For $R = 80\Omega$, V_R is _____.




- A) 48V
- B) 60V
- C) 120V
- D) 160V

Correct Answer: **A**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

Use thevenin's equivalent

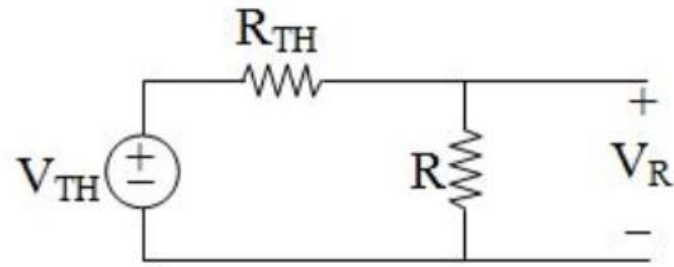

Step - 1

$$-V_{TH} + 2R_{TH} + 20 = 0$$


Step - 2

$$-V_{TH} + \frac{3}{2}R_{TH} + 30 = 0$$

$$\text{So, } \frac{R_{TH}}{2} = 10 \rightarrow R_{TH} = 20\Omega$$


$$\text{So, } V_{TH} = 60V$$

$$\text{So, if } R = 80\Omega$$

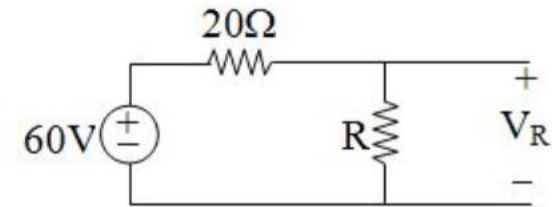

$$V_R = 60 \left[\frac{80}{20 + 80} \right] = 48 \text{ Voltage}$$

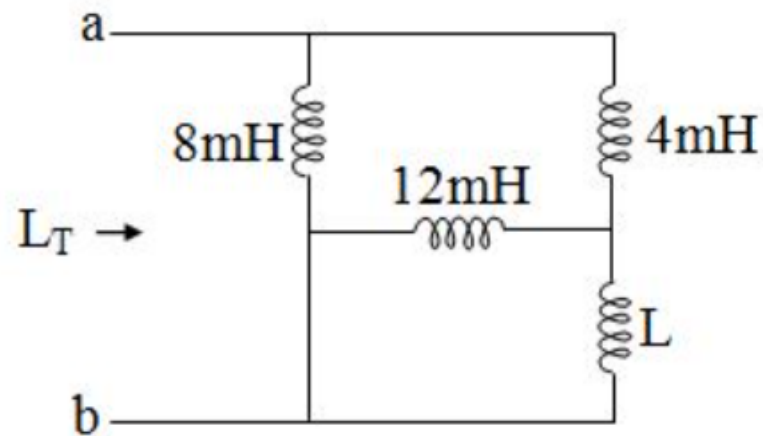5. If total inductance seen from terminal a-b in the network is equal to 4mH , then what will be the value of L (in mH)?




Correct Answer: **6**

Answer Range: **(6 , 6)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

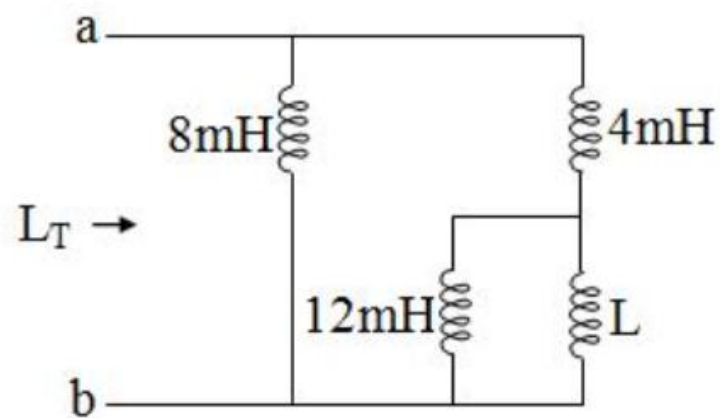

$$L_T = [8 // [4 + 12 // L]] \text{mH}$$

$$L_T = \left[8 // \left[4 + \frac{12L}{12+L} \right] \right] \text{mH}$$

$$L_T = \left[8 // \left[\frac{48+16L}{12+L} \right] \right] \text{mH}$$

$$L_T = \left[\frac{8 \left[\frac{48+16L}{12+L} \right]}{\frac{96+8L+48+16L}{12+L}} \right] \text{mH}$$


$$4\text{mH} = \left[\frac{8[48+16L]}{8[18+3L]} \right] \text{mH}$$

$$72 + 12L = 48 + 16L$$

$$4L = 24$$

$$L = 6\text{mH}$$

6. Value of current I_1 in circuit is

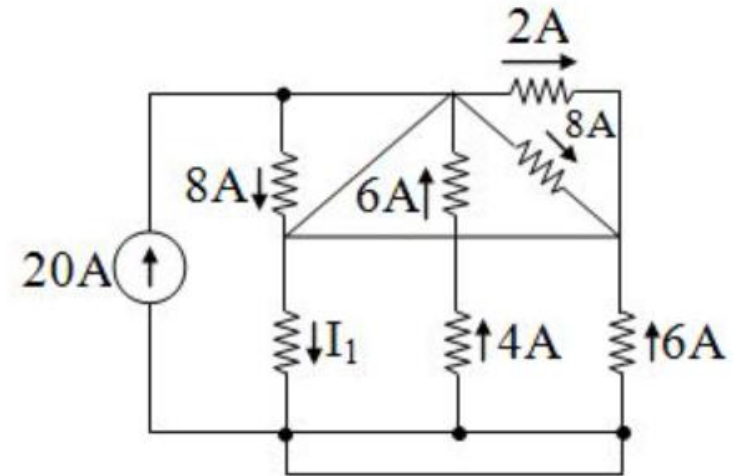


- A) 10A
- B) 30A
- C) 2A
- D) 18A

Correct Answer: **B**

Not Attempted : 

Marks : 1 / 0.33 (-Ve)


Apply KCL at Gaussian surface.

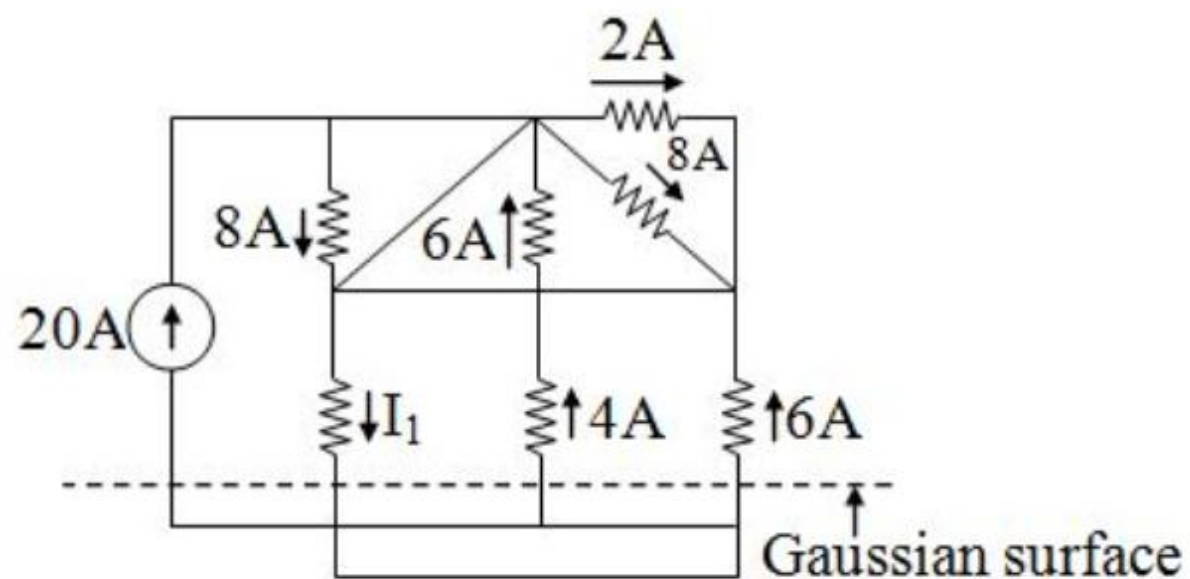


$$I_1 = 20 + 4 + 6$$

$$I_1 = 30\text{A}$$

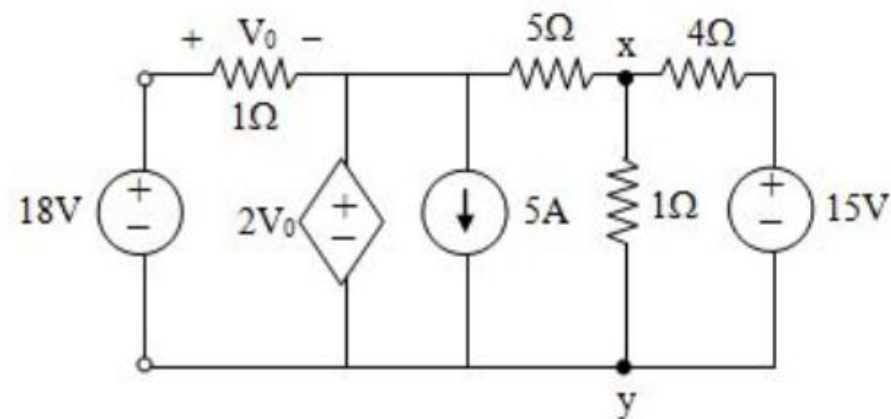7. What is the value of current (in Amperes) through 1Ω resistor across x-y in the circuit shown in figure?
(rounded off to two decimal places)



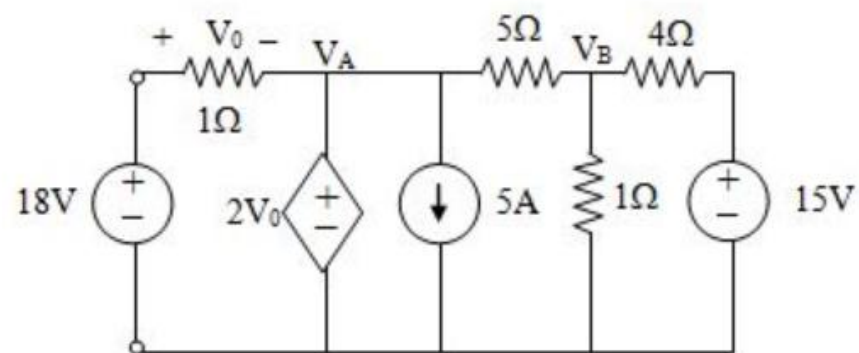

$$V_A = 18 - V_0 \text{ (but } V_A = 2V_0\text{)}$$

$$2V_0 = 18 - V_0$$

$$V_0 = \frac{18}{3} = 6V$$

By applying KCL at node b than

$$\frac{V_B}{1} + \frac{V_B - 15}{4} + \frac{V_B - V_A}{5} = 0$$

$$V_B \left(1 + \frac{1}{4} + \frac{1}{5} \right) = \frac{V_A}{5} + \frac{15}{4} \text{ (but } V_A = 18 - 6 = 12V\text{)}$$


$$V_B \left[\frac{20 + 5 + 4}{20} \right] = \frac{12}{5} + \frac{15}{4}$$

$$V_B \left[\frac{29}{20} \right] = \left[\frac{48 + 75}{20} \right]$$

$$V_B = 4.24V$$

∴ so current through 1Ω resistor is $\frac{V_B}{1\Omega} = 4.24A$

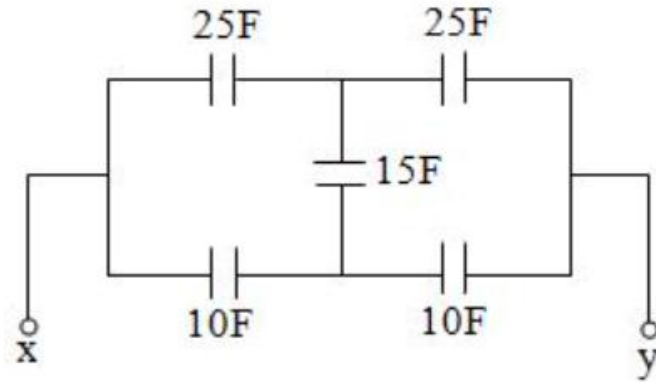8. What is the value of equivalent capacitance between terminals x –y in below figure?




- A) 15.5 F
- B) 17.5 F
- c) 18.5 F
- D) 19.5 F


Correct Answer: **B**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

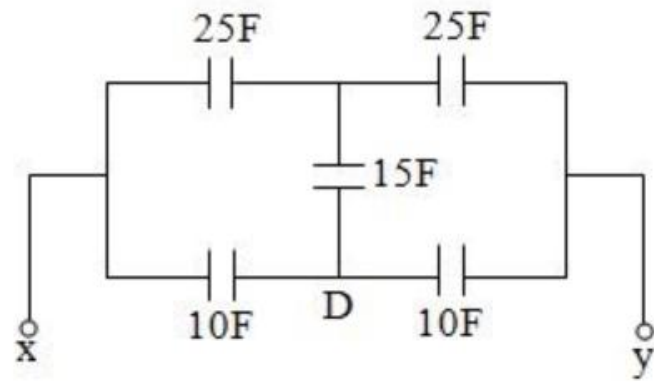

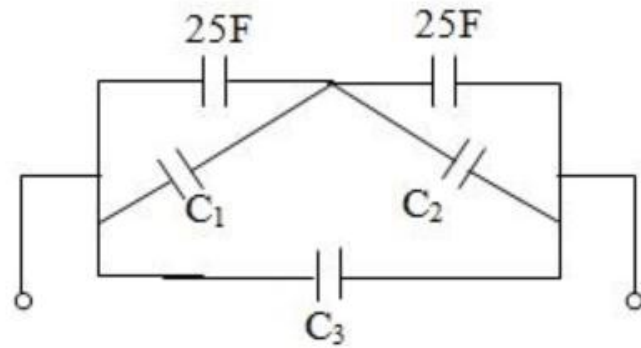
Here star point at “D” has been replaced by equivalent delta having delta branch capacitances C_1 , C_2 and C_3



$$C_1 = \frac{10 \times 15}{35} = 4.28F$$


$$C_2 = \frac{15 \times 10}{35} = 4.28F$$
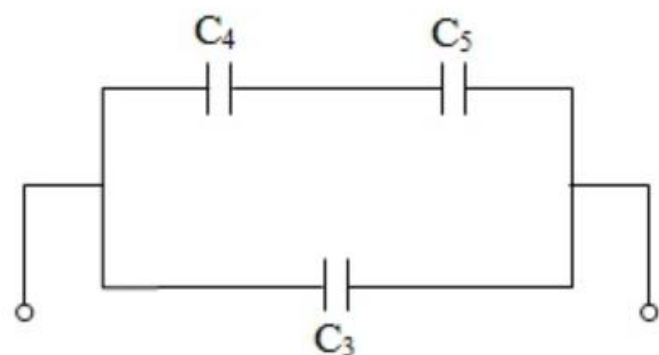
$$C_3 = \frac{10 \times 10}{35} = 2.86F$$



$$C_4 = C_1 + 25 = 29.28F$$

$$C_5 = C_2 + 25 = 29.28F$$

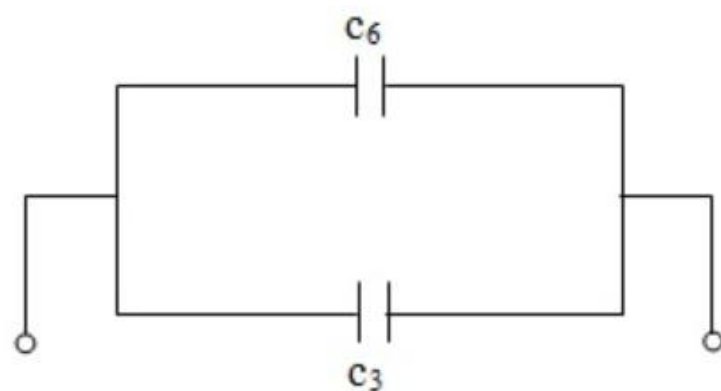




C_6 is formed by series combination of C_4 and C_5

$$C_6 = \frac{(29.28) \times (29.28)}{2 \times (29.28)} = 14.64F$$


$$\begin{aligned} \therefore C_{x-y} &= C_6 + C_3 = 14.64 + 2.86 \\ &= 17.5F \end{aligned}$$

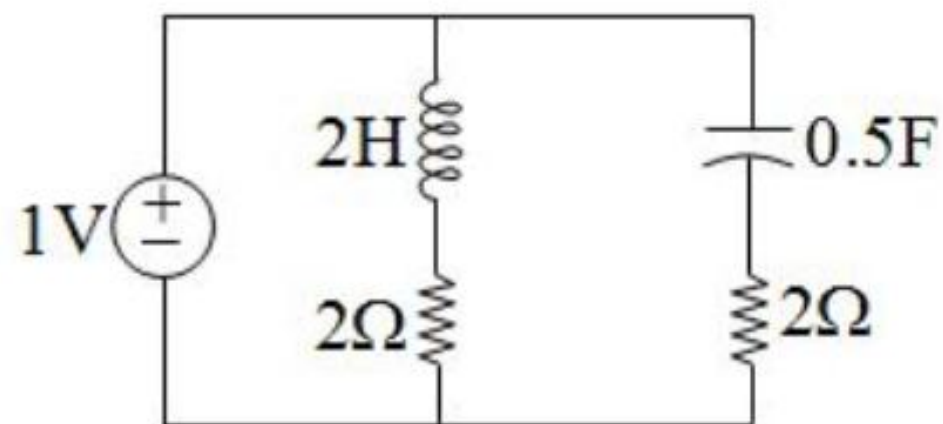9. The dual of following network shown below is_____



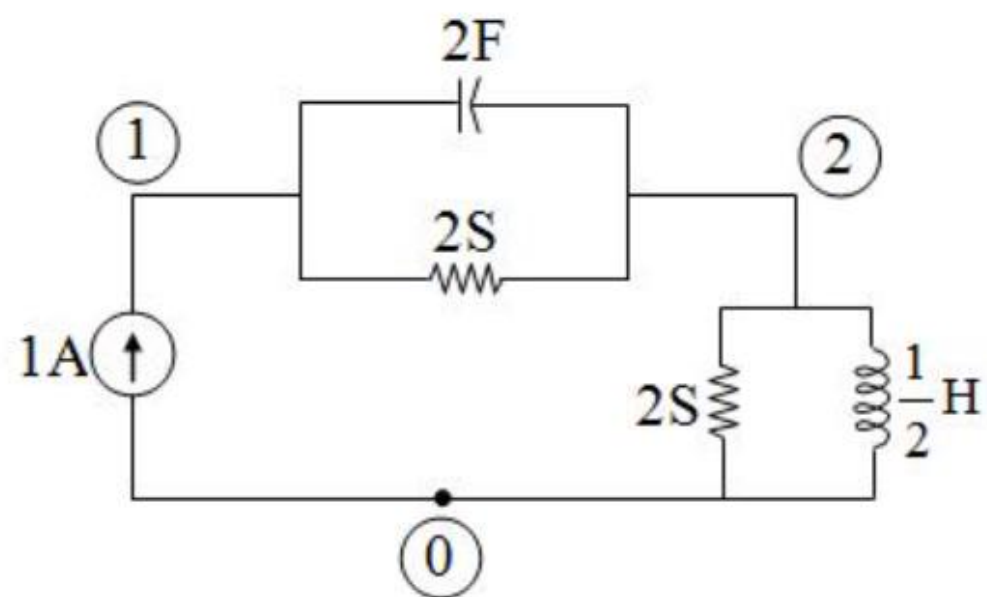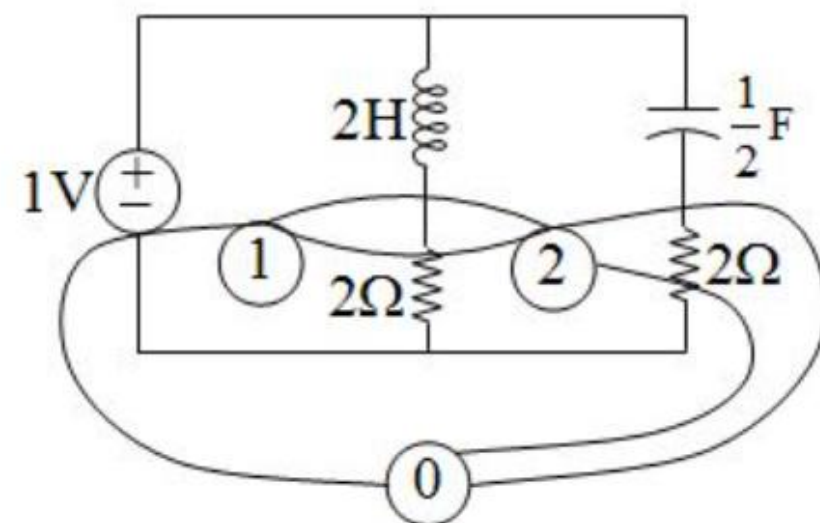

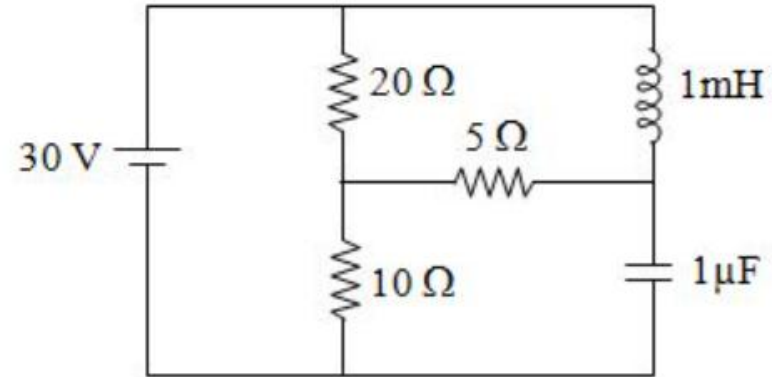10. The total energy stored in a network will be (in mJ) _____.
(rounded off to two decimal places)



Correct Answer: **1.92**


Answer Range: **(1.8 , 2)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

It can be assumed that the circuit is in existence for a long time, and has hence reached a steady state. In the steady state there are only 2 energy storing elements.

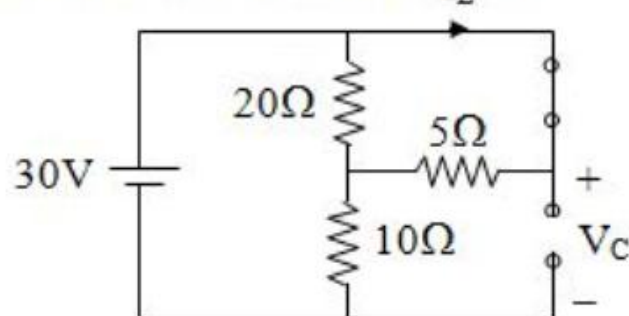For DC source inductor acts as a short circuit and capacitor as an open circuit. Hence the circuit is as show below.



$$\therefore V_C = 30V$$


$$I_L = 1.714A$$

$$\text{Therefore, energy in inductor} = \frac{1}{2} L I_L^2 = 1.47 \text{ mJ}$$

$$\text{Energy stored in capacitor} = \frac{1}{2} C V^2 = 0.45 \text{ mJ}$$

$$\text{Total energy} = 1.92 \text{ mJ}$$

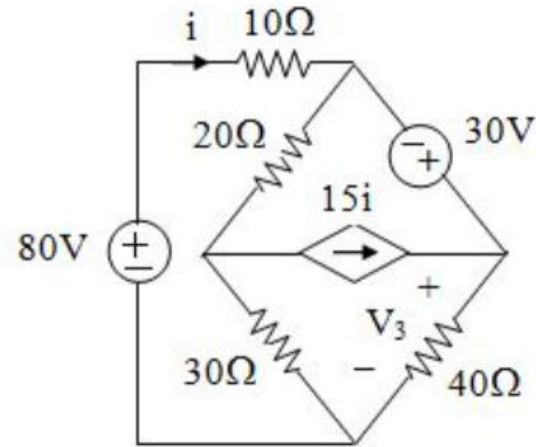11. The approximate value of voltage V_3 in the circuit given below is




- A) 104 V
- B) 100 V
- C) 108 V
- D) 96 V

Correct Answer: **A**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

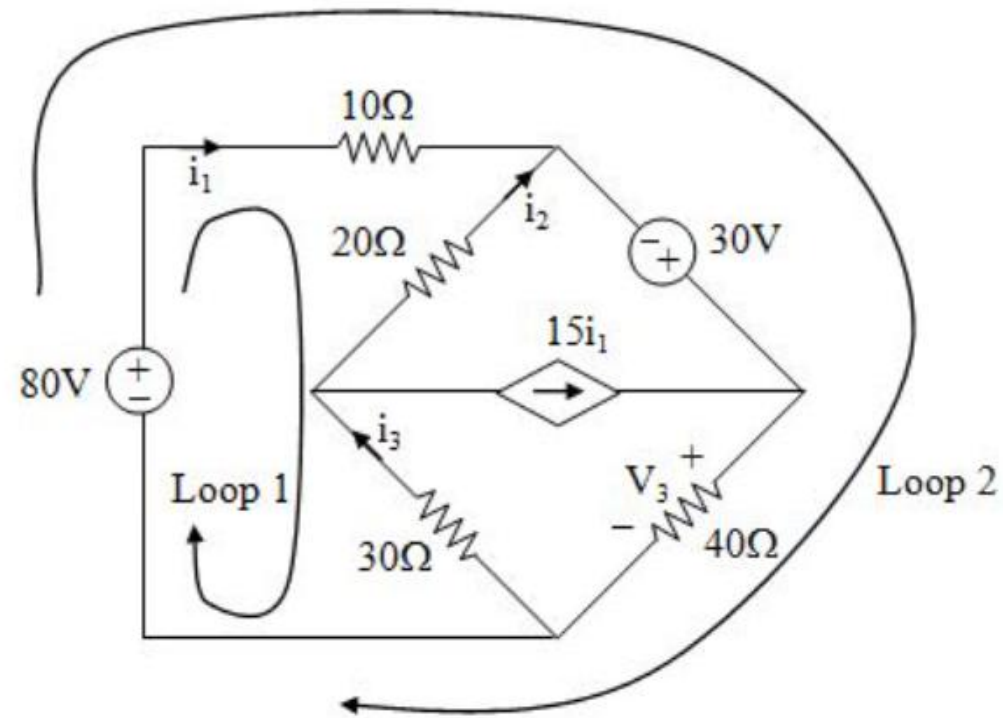

By solving (1), (2) & (3)

$$i_1 = 0.58 \text{ A} \quad i_2 = -6.68 \text{ A} \quad i_3 = 2.02 \text{ A}$$


$$\therefore V_3 = 40(i_1 + i_3) \approx 104\text{V}$$

$$\therefore 80 - 10i_1 + 20i_2 + 30i_3 = 0 \quad \dots\dots (1)$$

$$80 - 10i_1 + 30 - 40(i_1 + i_3) = 0 \quad \dots\dots (2)$$

$$15i_1 = i_3 - i_2 \quad \dots\dots (3)$$

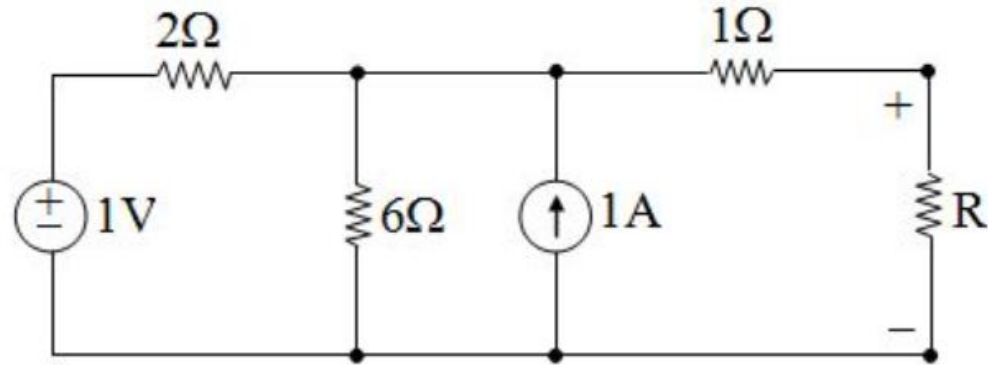12. Find the maximum power delivered to R in the circuit in figure, when R is set for maximum power transfer?




- A) 1W
- B) 0.5W
- C) 2W
- D) 2.25W

Correct Answer: **B**

Not Attempted : 

Marks : 1 / 0.33 (-Ve)

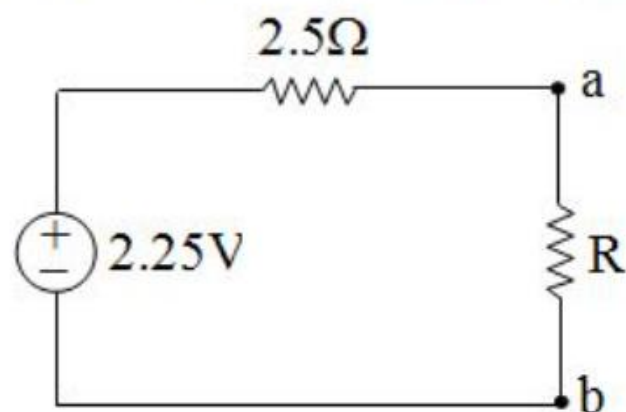Applying Thevenin theorem, the Thevenin equivalent has Thevenin voltage of 2.25V and a Thevenin resistance of 2.5Ω .




According to the maximum power transfer principle, when $R = R_{Th} = 2.5\Omega$, the load R receives the maximum power.

The maximum power received by the load in this case is

$$P_{Load} = \frac{(V_{Th}/2)^2}{R_{Th}} = \frac{((2.25V)/2)^2}{2.5\Omega} = \frac{81}{160} = 0.50625W .$$

13. Consider the following network

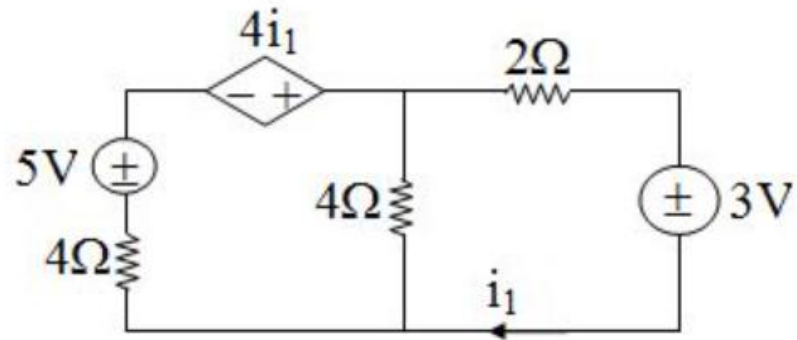

The value of i_1 in amperes is _____
(rounded off to two decimal places)

Correct Answer: **-0.25**

Answer Range: **(-0.25 , -0.25)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

$$\text{Nodal} \Rightarrow \frac{V - 4i - 5}{4} + \frac{V - 0}{4} + \frac{V - 3}{2} = 0$$

$$\Rightarrow 4V - 4i_1 = 11 \dots\dots\dots (1)$$


$$\text{By KVL} \Rightarrow V - 2i_1 - 3 = 0$$

$$\Rightarrow V - 2i_1 = 3 \dots\dots\dots (2)$$

$$\text{Eq. (2) in Eq. (1)} \Rightarrow 4(2i_1 + 3) - 4i_1 = 11$$

$$\Rightarrow i_1 = -\frac{1}{4} \text{ A} = -0.25 \text{ A}$$

14. Consider the following circuit

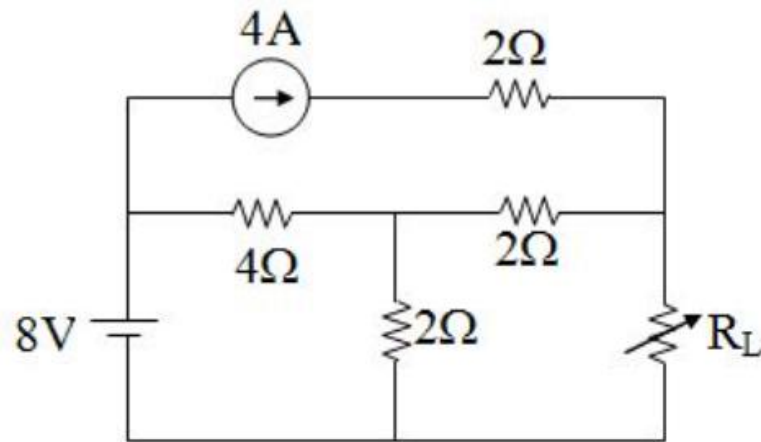


The value of maximum power transfer to load resistor ' R_L ' in watts is (rounded off to one decimal place)

Correct Answer: **19.2**


Answer Range: **(19 , 19.5)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

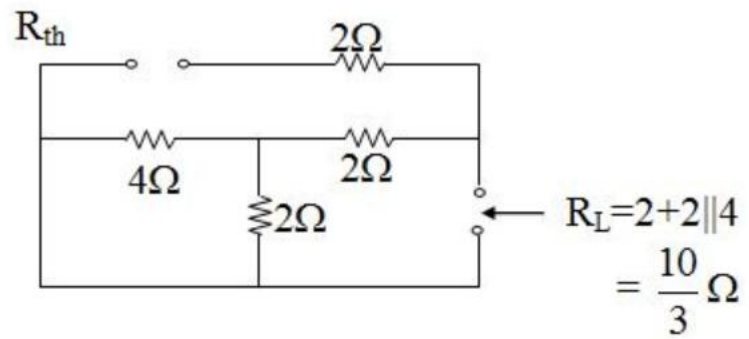

$V_{th}:$

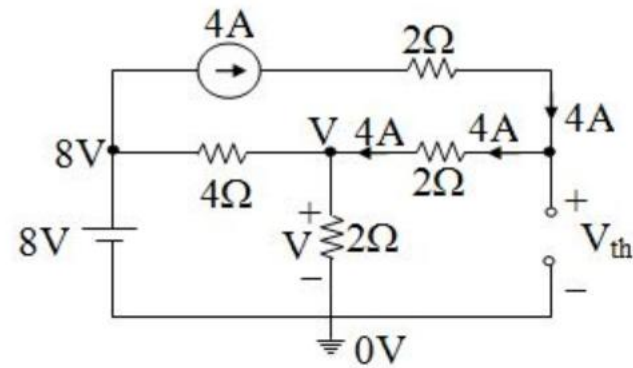


$$\text{Nodal} \Rightarrow \frac{V-8}{4} + \frac{V}{2} - 4 = 0$$

$$\Rightarrow V = 8 \text{ V}$$

$$\text{By KVL} \Rightarrow V + 8 - V_{th} = 0$$

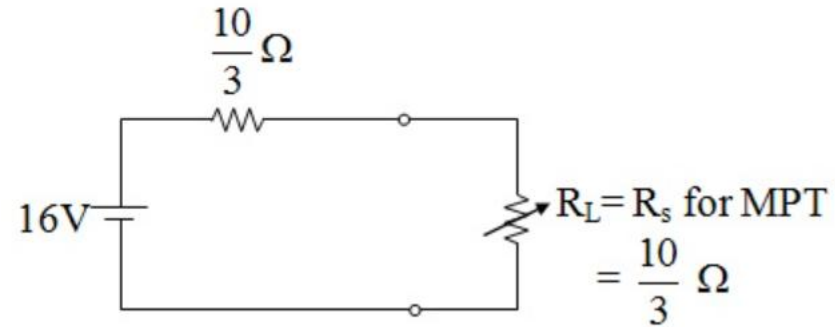
$$\Rightarrow V_{th} = v + 8 = 8 + 8 = 16 \text{ V}$$




$$\Rightarrow P_{\max} = \frac{V_{th}^2}{4R_{th}} (\text{W}) = \frac{16^2}{4 \times \frac{10}{3}} = 19.2 \text{ W}$$

15.

In the circuit shown below, the dependent source delivers the power (in Watts) is _____.

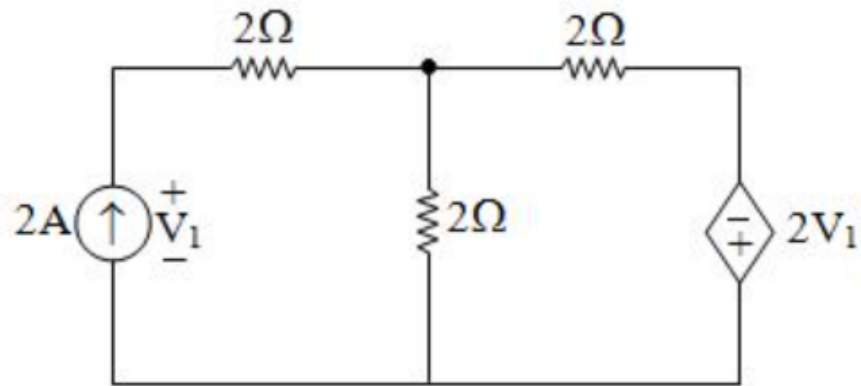Correct Answer: **15**Answer Range: **(15 , 15)**Not Attempted : 

Marks : 1 / 0 (-Ve)

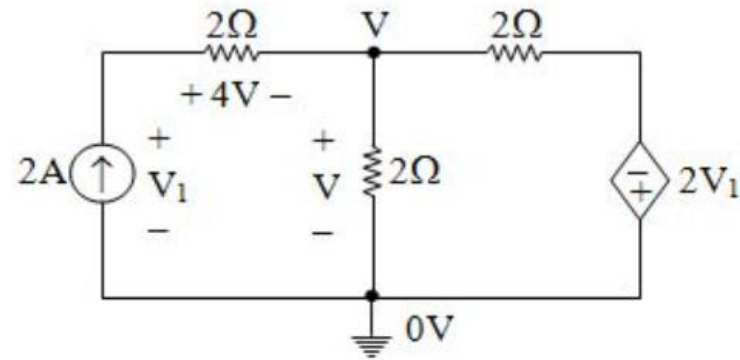

$$\text{Nodal} \Rightarrow -2 + \frac{V}{2} + \frac{V + 2V_1}{2} = 0 \Rightarrow V_1 + V = 2 \rightarrow (1)$$

$$\text{KVL} \Rightarrow V_1 - 4 - V = 0 \Rightarrow V_1 - V = 4 \rightarrow (2)$$

From eqns (1) & (2) $V_1 = 3V$ & $V = -1V$

$$\text{So, } I_{2V_1} = \frac{V + 2V_1}{2} = \frac{-1 + 6}{2} = \frac{5}{2} \text{ A}$$

$$\Rightarrow P_{2V_1} = 2 \times 3 \times 5/2$$

$$= 15 \text{ W (delivered)}$$