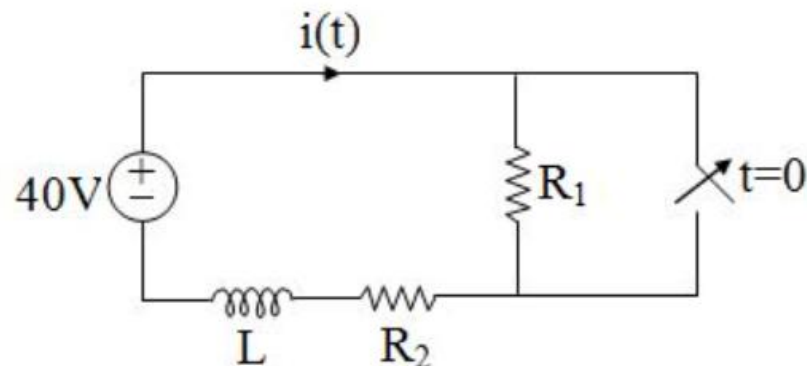


GATE 2026 TEST SERIES

Electric Circuits

Test 2

1. In circuit below, the switch is open at $t = 0$, if $i(t) = 5 + 3e^{-16t}$ A for $t > 0$, then value of R_1 , R_2 and L are respectively



- A) $8\Omega, 3\Omega, 128H$
- B) $5\Omega, 3\Omega, \frac{1}{2}H$
- C) $3\Omega, 8\Omega, 128H$
- D) $3\Omega, 5\Omega, \frac{1}{2}H$

This is step response of first order circuit.


$$i(t) = I(\infty) + [I(0) - I(\infty)]e^{\frac{-t}{\tau}} \text{ comparing } i(t) = 5 + 3e^{-16t}$$

$$\rightarrow I(\infty) = 5$$

$$\rightarrow I(0) - I(\infty) = 3$$


$$\rightarrow \frac{1}{\tau} = 16$$

So, $t > 0$:

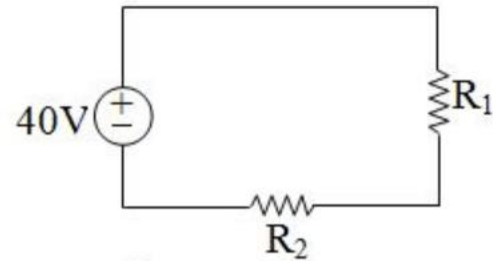

$$I(\infty) = \frac{40}{R_1 + R_2} = 5 \dots\dots\dots(1)$$

$t < 0$:

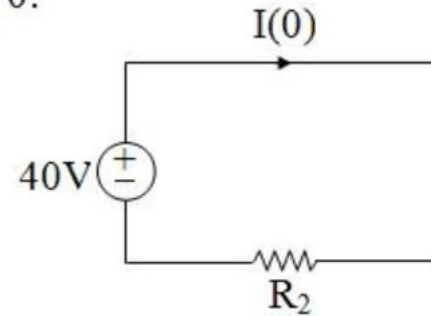

$$\Rightarrow I(0) - 5 = 3$$

$$I(0) = 8A$$

$$I(0) = \frac{40}{R_2} = 8 \rightarrow R_2 = 5\Omega \dots\dots\dots(2)$$

Solve (1) and (2)

$$40 = 5R_1 + 25$$

$$R_1 = 3\Omega$$


$$\tau = \frac{L}{R_{eq}} = \frac{L}{R_1 + R_2} = \frac{1}{16}$$

$$\frac{L}{5 + 3} = \frac{1}{16}$$

$$L = \frac{1}{2}H$$

$$R_1 = 3\Omega, R_2 = 5\Omega, L = \frac{1}{2}H,$$

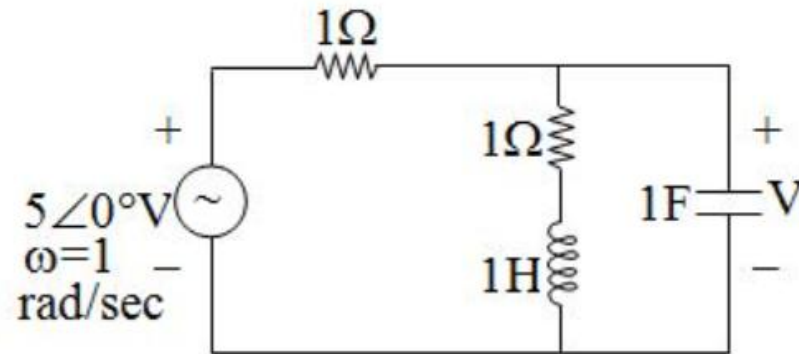2. The voltage $\bar{V}$ in circuit shown is _____.





- A) $5[1 + j]\text{V}$
- B) $1.66[1 + j]\text{V}$
- C) $[3 - j1]\text{V}$
- D) 0V

Correct Answer: **C**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

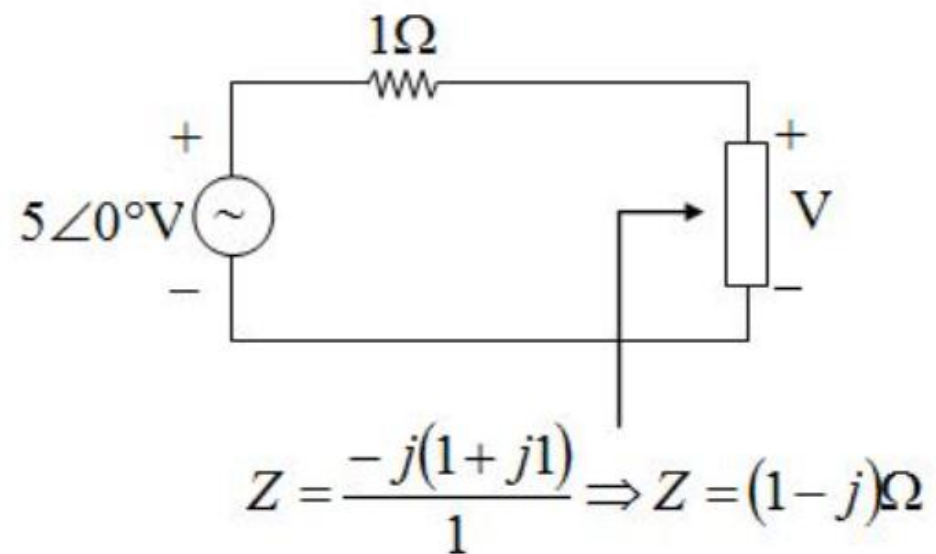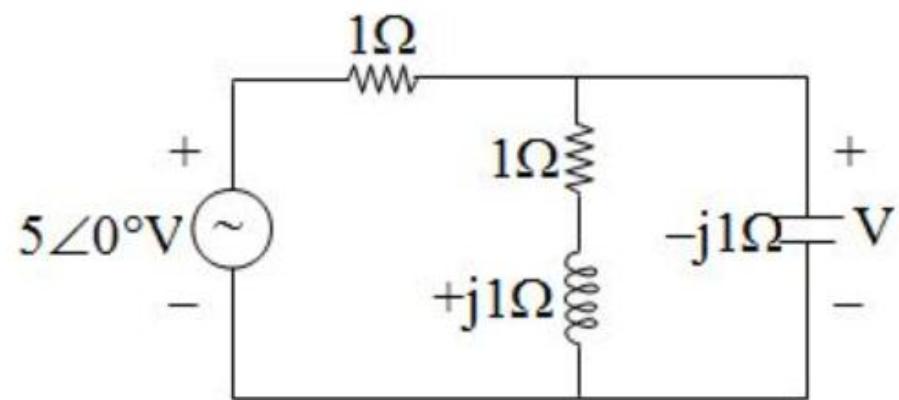


$$\text{So, } V = 5\angle 0 \left[\frac{1-j}{2-j} \right] \frac{(2+j)}{2+j}$$

$$= \frac{5[3-j]}{4+1}$$

$$V = (3-j1)\text{V}$$

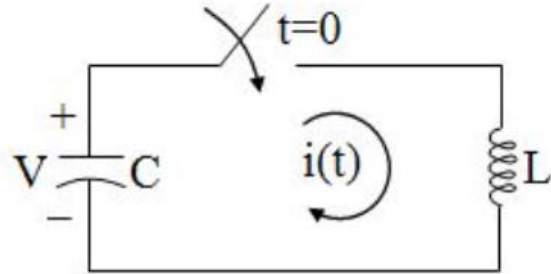3. The nature of current $i(t)$, when switch is instantly closed at $t = 0$ is_____.



- A) Sinusoidal
- B) Impulse
- c) Ramp
- D) DC current


Correct Answer: **A**

Not Attempted : 

Marks : 1 / 0.33 (-Ve)

Pure L-C [Loss less] circuit is undamped as capacitor is charged, so sinusoidal option (a)

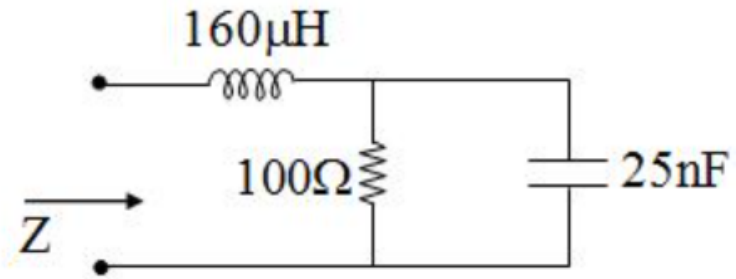4. The value of impedance Z at its natural frequency is_____.



- A) 100Ω
- B) 64Ω
- C) 80Ω
- D) 40Ω

Correct Answer: **B**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

First find natural frequency circuit

$$Z = j\omega L + \left[R // \frac{1}{j\omega C} \right]$$
$$= j\omega L + \frac{R}{1 + j\omega RC} = j\omega L + \frac{R[1 - j\omega RC]}{1 + \omega^2 R^2 C^2}$$

$$Z = \frac{R}{1 + \omega^2 R^2 C^2} + j \left[\omega L - \frac{\omega R^2 C}{1 + \omega^2 R^2 C^2} \right]$$

At natural frequency 'Z' is purely resistive, so,

$$\omega L = \frac{\omega R^2 C}{1 + \omega^2 R^2 C^2}$$

$$L + \omega^2 R^2 C^2 L = CR^2$$


$$\omega^2 = \frac{CR^2 - L}{R^2 C^2 L} \Bigg\} = 9 \times 10^{10}$$

$$\omega = 300 \text{ k rad/sec}$$

Now, impedance at this frequency is purely resistive so, $Z = \frac{R}{1 + \omega^2 R^2 C^2}$

$$Z = \frac{100}{1 + (300 \times 10^3)^2 (100)^2 (25 \times 10^{-9})^2} = 64 \Omega$$

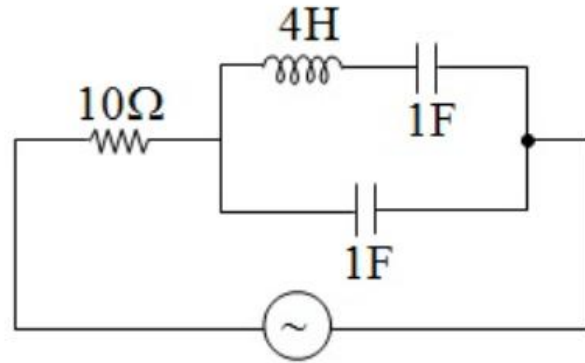5. The following circuit shown, resonates at _____ frequency



- A) All frequencies
- B) $\frac{1}{2}$ rad/sec
- C) 5 rad/sec
- D) 1 rad/sec

Correct Answer: **B**

Not Attempted :

Marks : 2 / 0.66 (-Ve)

$$Z = R + \left[\left[j\omega L + \frac{1}{j\omega C} \right] // \frac{1}{j\omega C} \right]$$


$$= R + \frac{j \left(\omega L - \frac{1}{\omega C} \right) \left(\frac{-j}{\omega C} \right)}{j \left(\omega L - \frac{1}{\omega C} \right) + \frac{-j}{\omega C}}$$

At resonance, $\text{Im}[Z] = 0$

$$\text{So, } \left[\omega L - \frac{1}{\omega C} \right] = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{4(1)}} = \frac{1}{2} = 0.5 \text{ rad/sec}$$

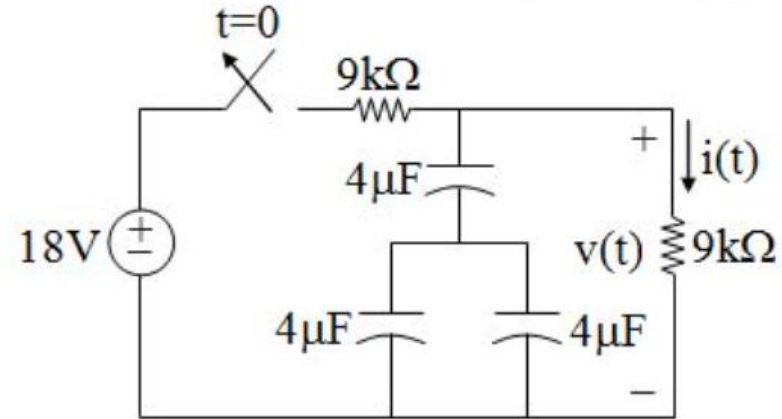6. In the circuit shown below, current $i(t)$ for $t > 0$ is _____



- A) $6e^{-41.67t}\text{mA}$
- B) $9e^{-41.67t}\text{mA}$
- C) $e^{-41.67t}\text{mA}$
- D) $4e^{-20.83t}\text{mA}$


Correct Answer: C

Not Attempted : !


Marks : 1 / 0.33 (-Ve)

This is source free first order circuit, so, $v(t) = v_0 e^{\frac{-t}{\tau}}$

$t = 0^-$;

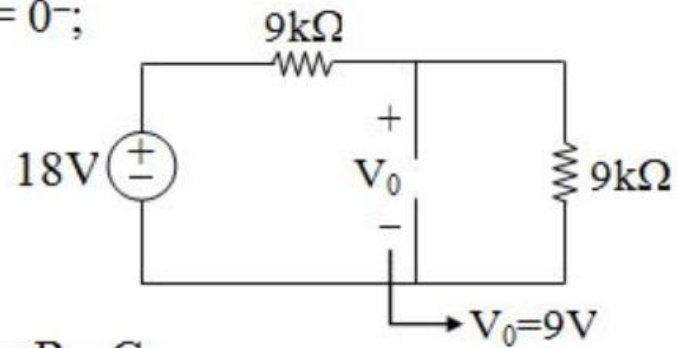

$$\tau = R_{eq} C_{eq}$$

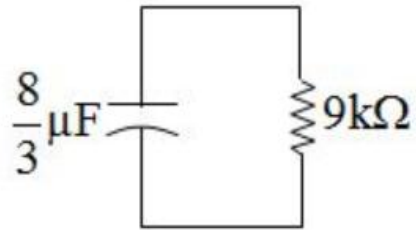


$$\tau = R_{eq} \cdot C_{eq} = 9k \left[\frac{8}{3} \mu F \right] = \frac{72}{3} \text{ m sec}$$

$$\text{So, } v(t) = v_0 e^{\frac{-t}{\tau}} = 9e^{\frac{-3t}{72\text{m}}}$$

$$i(t) = \frac{v(t)}{9k\Omega} = \frac{9e^{\frac{-3000}{72}t}}{9k} = 1e^{-41.67t} \text{ mA}$$

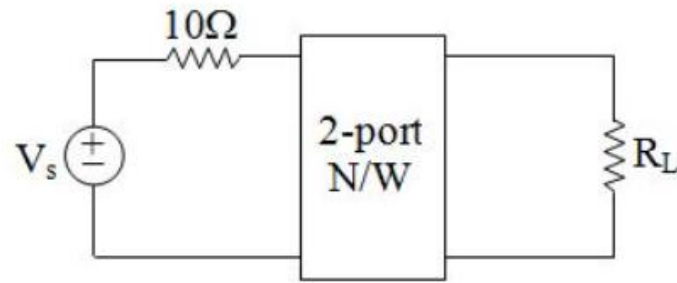7. In circuit shown below ABCD parameters of two port network are $\begin{bmatrix} 4 & 20 \\ 0.1 & 2 \end{bmatrix}$. What should be the value of load R_L to transfer the maximum power?



- A) $\frac{40}{3}\Omega$
- B) 10Ω
- C) 4Ω
- D) 8Ω

Correct Answer: **D**


Not Attempted : 

Marks : 2 / 0.66 (-Ve)

$$V_1 = 4V_2 - 20I_2$$

$$I_1 = 0.1 V_2 - 2I_2$$

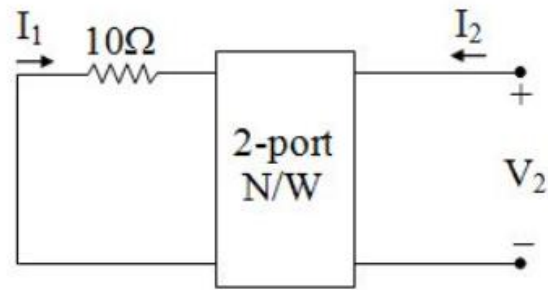To obtain maximum power transfer, we have to calculate Thevenin impedance across load terminal so,



Substitute $V_1 = -10I_1$ in above equations.

$$-10I_1 = 4V_2 - 20I_2$$


$$-10[0.1V_2 - 2I_2] = 4V_2 - 20I_2$$

$$\text{So, } 40I_2 = 5V_2$$

$$Z_{TH} = \frac{V_2}{I_2} = \frac{40}{5} = 8\Omega$$

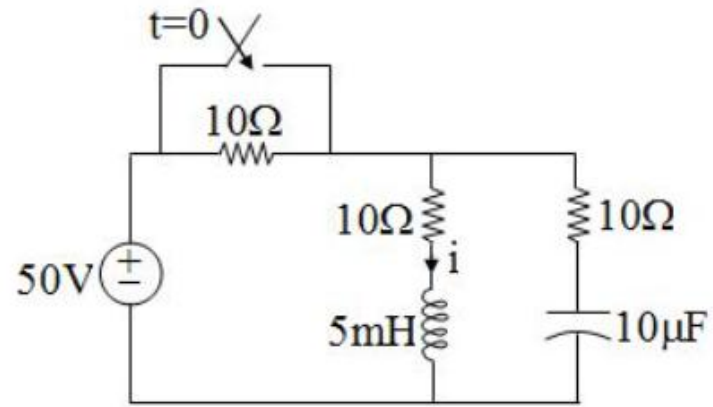8.

What is the value of $\frac{di(0^+)}{dt}$?




- A) 1kA/sec
 B) 5kA/sec
 C) 10kA/sec
 D) 25kA/sec

Correct Answer: **B**


Not Attempted :

Marks : 2 / 0.66 (-Ve)

$t = 0^-$:

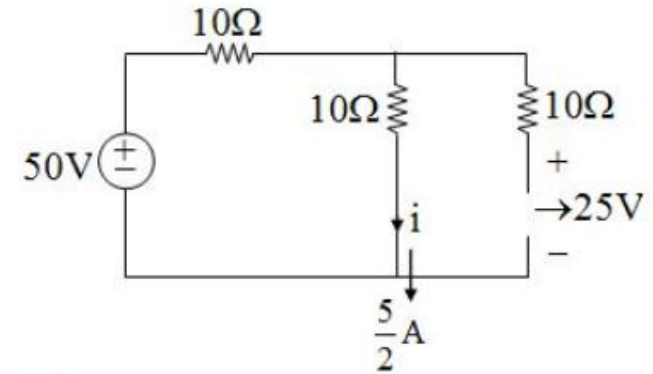

$t = 0^+$:

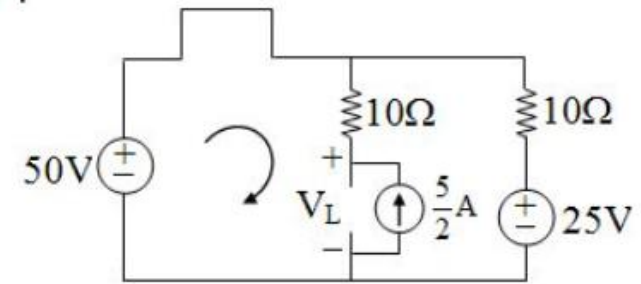

KVL

$$-50 + \frac{5}{2}(10) + V_L(0^+) = 0$$

$$V_L(0^+) = 25$$

$$\frac{di(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{25}{5\text{m}} = 5\text{kA/sec}$$

9. An initially relaxed RC series network with $R = 2 \text{ M}\Omega$ and $C = 1 \text{ }\mu\text{F}$ is switched on to a 10 V step input. The voltage across capacitor after 2 seconds will be

- A) Zero
- B) 3.68 V
- C) 6.32 V
- D) 10 V

Correct Answer: C


Not Attempted : 

Marks : 1 / 0.33 (-Ve)


$$V_c(t) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) e^{\frac{-t}{RC}}$$

$$V_c(t) = 10 + (0 - 10) e^{\frac{-t}{2}} = 10(1 - e^{\frac{-t}{2}})$$

$$V_c(t)|_{t=2} = 10(1 - e^{-1}) = 6.32 \text{ V}$$

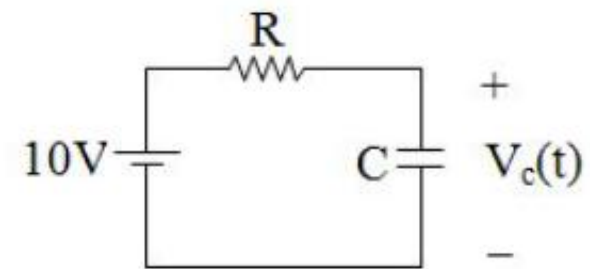

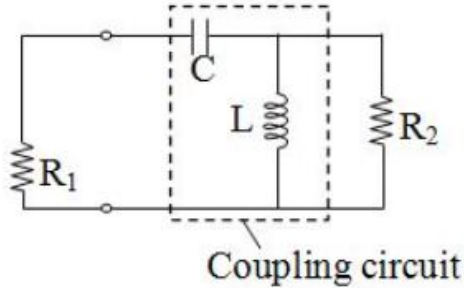10. A source of internal resistance, R_1 is to be matched, at angular frequency ω , to a purely resistive load R_2 (where $R_2 > R_1$) by means of the coupling circuit shown in figure. The expressions for L and C in terms of R_1 , R_2 and ω are



- A) $L = \frac{R_2}{\omega} \sqrt{\frac{R_1}{(R_2 - R_1)}}$, $C = \frac{1}{\omega} \sqrt{\frac{1}{R_1(R_2 - R_1)}}$
- B) $L = \omega R_2 \sqrt{\frac{R_1}{R_2 + R_1}}$, $C = \omega \sqrt{\frac{R_1}{(R_2 - R_1)}}$
- C) $L = \frac{R_1}{\omega R_2} \left(\frac{1}{R_2 + R_1} \right)$, $C = \frac{1}{\omega} \frac{R_1}{(R_2 + R_1)}$
- D) $L = \frac{\omega R_1}{R_1^2 + R_2^2}$, $C = \frac{\omega R_2}{R_1^2 + R_2^2}$

For matching we must have:

$$R_1 = -\frac{j}{\omega C} + \frac{j\omega L R_2}{R_2 + j\omega L}$$

Equating real and imaginary parts,

$$L = C R_1 R_2 \text{ and } R_1 \omega^2 L C = R_2 \omega^2 L C - R_2$$

$$\therefore L = \frac{R_2}{\omega} \sqrt{\frac{R_1}{(R_2 - R_1)}}, C = \frac{1}{\omega} \sqrt{\frac{1}{R_1(R_2 - R_1)}}$$

Correct Answer: A


Not Attempted : 1

Marks : 2 / 0.66 (-Ve)

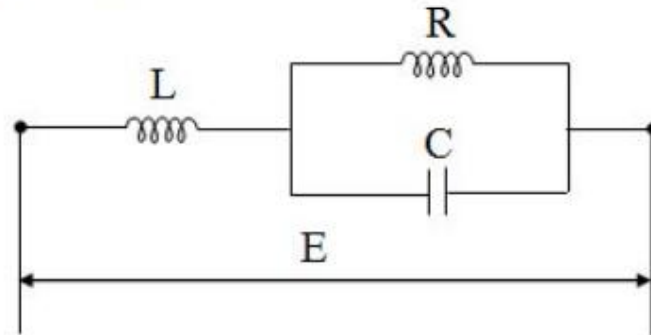11. For the circuit give in figure, the applied e.m.f. is given by:

$$E = 10 + 12\sin 2\pi ft + 9\sin[4\pi ft + (\pi/4)]V$$

and L is a pure inductance whose reactance at frequency f is 2Ω and C is a pure capacitance whose reactance at frequency f is 6Ω . The resistance of R is 5Ω .



The r.m.s. value of the total current(in A) taken from the supply is

Correct Answer: 4.5

Answer Range: (4 , 5)

Not Attempted : !

Marks : 2 / 0 (-Ve)

The reactive components have no effect on the steady component of current due to the steady component of p.d.

$$\therefore I_{DC} = \frac{E_{DC}}{R} = \frac{10}{5} = 2A$$

At frequency f ,

$$\omega L = 2\Omega, \frac{1}{\omega L} = 6\Omega$$

$$\therefore I_{f(peak)} = \frac{12}{j2 - (5 \times j6)/(5 - j6)} = \frac{3(5 - j6)}{3 - j5}$$

$$\therefore I_{f(peak)} = \frac{3\sqrt{(25+36)}}{\sqrt{(9+25)}} = 4.02A$$

$$\therefore I_{f(r.m.s)} = \frac{4.02}{\sqrt{2}} = 2.84A$$

At frequency $2f$,

$$\omega L = 4\Omega, \frac{1}{\omega L} = 3\Omega$$

$$\therefore I_{2f(peak)} = \frac{9}{j4 - (5 \times j3)/(5 - j3)} = \frac{9(5 - j3)}{12 + j5}$$


$$\therefore I_{2f(peak)} = \frac{9\sqrt{(25+9)}}{\sqrt{(144+25)}} = 4.04A$$

$$\therefore I_{2f(r.m.s)} = 2.85A$$

$$\text{Total } I_{(r.m.s)} = \sqrt{(2^2 + 2.84^2 + 2.85^2)} = 4.5A$$

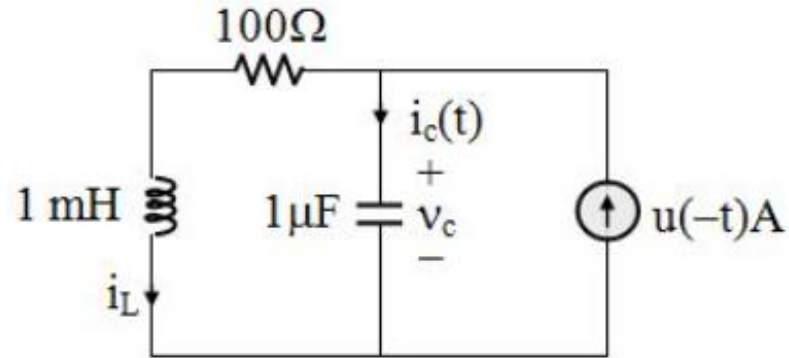12.

For the circuit shown in the given figure, $\frac{dv_c(0^+)}{dt}$ is




- A) 10^6 V/sec
- B) -10^6 V/sec
- C) 10^3 V/sec
- D) -10^3 V/sec

Correct Answer: B

Not Attempted : !


Marks : 1 / 0.33 (-Ve)

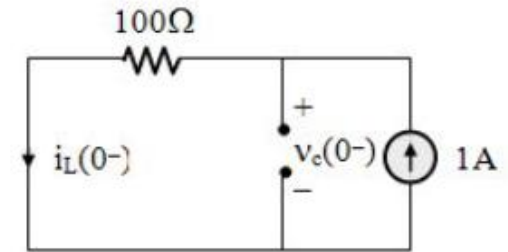

$$v_c(0^-) = 1 \times 100 = 100\text{V} = v_c(0)$$

$$i_L(0^-) = 1\text{A} = i_L(0^+)$$

$$t = 0^+$$

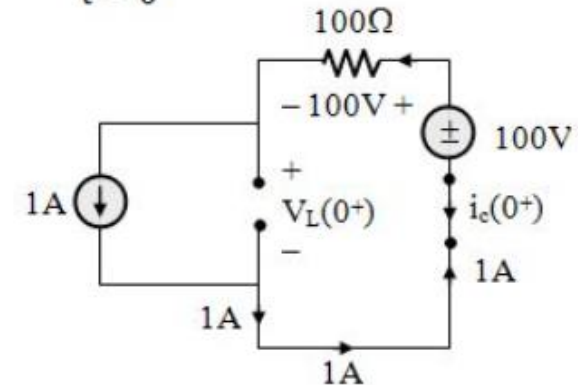


$$i_c(0^+) = -1$$

$$\frac{C dv_c(0^+)}{dt} = -1$$

$$\frac{dv(0^+)}{dt} = \frac{-1}{C} = -10^6 \text{ V/sec}$$

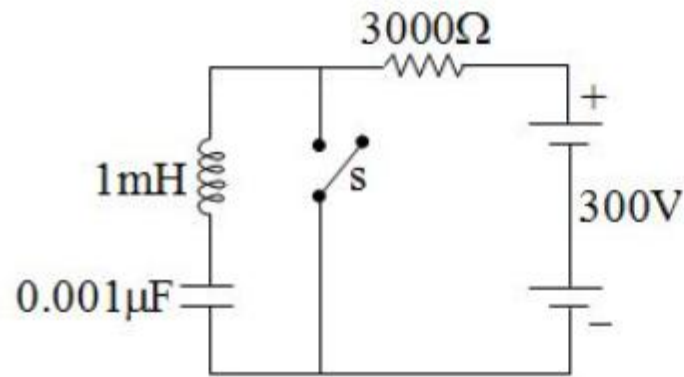13. The circuit below contains a rapid acting switch S. After the circuit has reached a steady state, the switch is closed and automatically re-opens permanently when the current through it becomes zero. Find for how long the Switch remains closed?



- A) 15.5μsec
- B) 15.5 msec
- C) 3.48μsec
- D) 50msec

Correct Answer: C

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

Before closing, the charge q on C is CV and $dq/dt = 0$.

After closing

$$v = L \frac{d}{dt} \left(-V \frac{dv}{dt} \right)$$

$$\therefore \frac{d^2 v}{dt^2} + \frac{v}{LC} = 0$$

$$\therefore v = V \cos \omega t \quad \text{where } \omega = \frac{1}{\sqrt{LC}}$$

$$\begin{aligned} \text{The current through } S &= \frac{V}{R} - C \frac{dv}{dt} \\ &= \frac{V}{R} + \omega CV \sin \omega t \end{aligned}$$

$\therefore$ switch opens when

$$\omega CV \sin \omega t + \frac{V}{R} = 0$$

$$\therefore \sin \omega t = -\frac{1}{\omega CR}$$

$$\text{but } \omega = \frac{1}{\sqrt{LC}}$$


$$\therefore \sin \omega t = -\frac{1}{R} \sqrt{\frac{L}{C}}$$

$$L = 10^{-3} \text{H}, C = 10^{-9} \text{F}, R = 3 \times 10^3 \Omega, \omega = 10^6 \text{rad/sec}$$

$$\therefore \sin \omega t = -1/3$$

$$\begin{aligned} \therefore t &= \left(\pi + \sin^{-1} \frac{1}{3} \right) \mu \text{sec} \\ &= 3.48 \mu \text{sec} \end{aligned}$$

14. Consider the following network

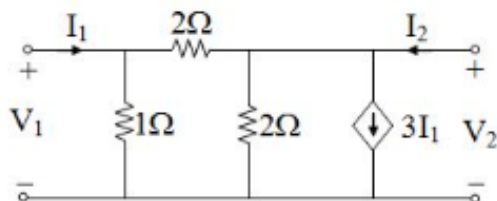

The transmission parameters are

A) $\begin{pmatrix} \frac{-1}{4} & \frac{-1}{8} \\ \frac{-3}{8} & \frac{-5}{16} \end{pmatrix}$

B) $\begin{pmatrix} \frac{-15}{16} & \frac{-3}{8} \\ \frac{-1}{8} & \frac{-1}{4} \end{pmatrix}$

C) $\begin{pmatrix} \frac{+1}{8} & \frac{-1}{4} \\ \frac{-5}{16} & \frac{-3}{8} \end{pmatrix}$

D) $\begin{pmatrix} \frac{-3}{8} & \frac{-5}{16} \\ \frac{-1}{4} & \frac{-1}{8} \end{pmatrix}$

Correct Answer: C

Not Attempted : 1

Marks : 2 / 0.66 (-Ve)

$$\therefore \text{Nodal} \Rightarrow -I_1 + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = 0$$

$$\Rightarrow I_1 = 1.5V_1 - 0.5V_2 \dots\dots\dots (1)$$

$$\text{Nodal} \Rightarrow -I_2 + 3I_1 + \frac{V_2}{2} + \frac{V_2 - V_1}{2} = 0$$

$$\Rightarrow I_2 = 3I_1 + V_2 - 0.5V_1 \dots\dots\dots (2)$$

Substituting eqn. (1) in (2)

$$\Rightarrow I_2 = 4V_1 - 0.5V_2$$

$$\Rightarrow V_1 = \frac{1}{8}V_2 + \frac{1}{4}I_2 \dots\dots\dots (3)$$


Substituting eqn. (3) in (1)

$$\begin{aligned} \Rightarrow I_1 &= 1.5 \left(\frac{1}{8}V_2 + \frac{1}{4}I_2 \right) - 0.5V_2 \\ &= \frac{-5}{16}V_2 + \frac{3}{8}I_2 \dots\dots\dots (4) \end{aligned}$$

From eqns (3) & (4)

$$\Rightarrow (T) = \begin{pmatrix} \frac{1}{8} & \frac{-1}{4} \\ \frac{-5}{16} & \frac{3}{8} \end{pmatrix}$$

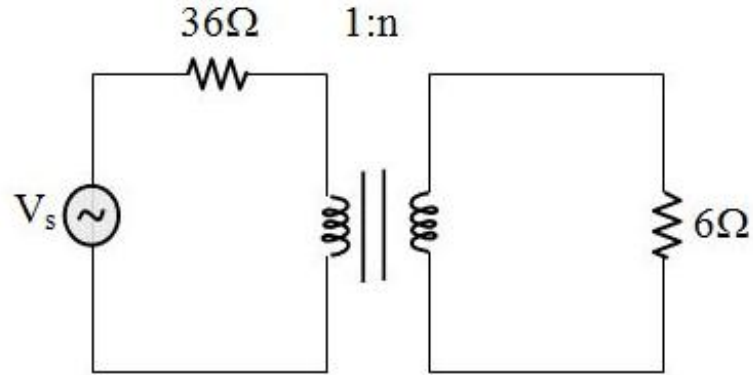15. Consider the following circuit for maximum power transfer to $6\ \Omega$ resistance, determine value of n .




- A) 6
- B) $2\sqrt{6}$
- C) $\sqrt{6}$
- D) $\frac{1}{\sqrt{6}}$

Correct Answer: D

Not Attempted:

Marks : 1 / 0.33 (-Ve)

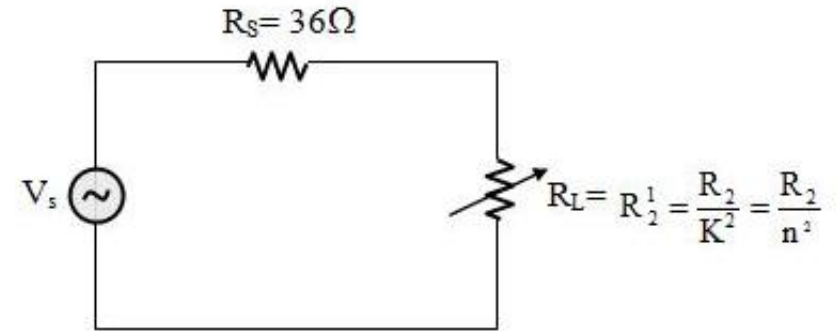

$$\frac{N_2}{N_1} = \frac{n}{1} = K$$

For MPT $\Rightarrow R_L = R_s$

$$\frac{R_2}{n^2} = 36$$

$$\frac{6}{n^2} = 36$$

$$n^2 = \frac{6}{36} = \frac{1}{6}$$

$$n = \frac{1}{\sqrt{6}}$$