

GATE 2026 TEST SERIES

Power Electronics

Test 2

1. A single-phase bridge inverter delivers power to a series connected RLC load with $R=2\Omega$, $\omega L = 8\Omega$. For this inverter-load combination, load commutation is possible in case the magnitude of $1/\omega C$ in ohms is
- A) 10
 - B) 8
 - C) 6
 - D) Can't say

Correct Answer: **A**

Not Attempted : 


Marks : 1 / 0.33 (-Ve)

Load commutation will occur when RLC load is underdamped

i.e., $X_L < X_C$

$\Rightarrow X_C > 8$

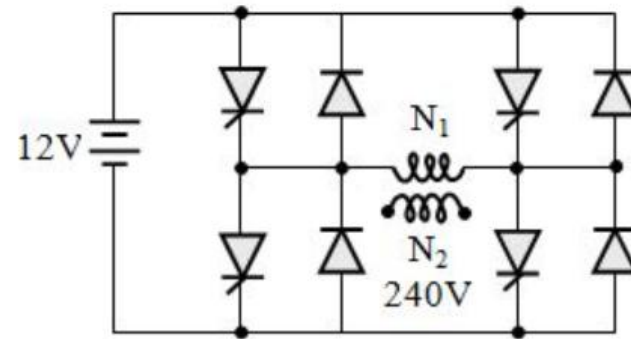2. A single-phase bridge inverter shown in figure, has an ideal transformer with primary turns equal to 10. For obtaining a fundamental frequency output voltage of 240V, the number of secondary turns in transformer should approximately be equal to _____.



Correct Answer: **222**

Answer Range: **(222 , 222)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

$$V_0 = \sum_{n=1,3,\dots}^{\infty} \frac{4V_s}{n\pi} \sin(n\omega_0 t)$$

$$V_{01,p} = \frac{2\sqrt{2}V_s}{\pi}$$

$$V_{01,s} = 240V$$

$$\frac{V_{01,p}}{V_{01,s}} = \frac{N_p}{N_s} = \frac{10}{N_s} \Rightarrow N_s = 10 \times \frac{240}{\left(\frac{2\sqrt{2} \times 12}{\pi}\right)} = \frac{100\pi}{\sqrt{2}} \approx 222$$

3. In single-pulse modulation used in PMW inverters, V_s is the input d.c. For eliminating third harmonic, the rms value of fundamental component of output voltage and pulse width respectively are

A) $\frac{2\sqrt{2}}{\pi} V_s, 120^\circ$

B) $\frac{\sqrt{6}}{\pi} V_s, 60^\circ$

C) $\frac{2\sqrt{2}}{\pi} V_s, 60^\circ$

D) $\frac{\sqrt{6}}{\pi} V_s, 120^\circ$

$$\sin(nd) = 0, n = 3$$

$$\Rightarrow nd = 180^\circ$$

$$\Rightarrow d = 60^\circ$$

$$\text{Pulse width, } W = 2d = 120^\circ$$

$$\text{RMS, } V_{01} = \frac{2\sqrt{2}V_s}{\pi} \sin 60^\circ = \frac{\sqrt{6}}{\pi} V_s$$

Correct Answer: D

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

4. A single-phase half-bridge inverter, connected to 230V dc source, feeds a resistive load of 10Ω . The input power factor is
- A) 0.5
 - B) 0.90
 - C) 0.57
 - D) 0.41

Correct Answer: **A**

Not Attempted : 

Marks : 1 / 0.33 (-Ve)

$$\begin{aligned}\text{input power factor} &= \frac{P_{\text{in}}}{S} = \frac{P_{\text{out}}}{S} \\ &= \frac{V_{0\text{rms}}^2 / R}{V_{s(\text{rms})} I_{s(\text{rms})}} = \frac{V_{0r}^2 / R}{V_{sr} \times I_{0r}} \\ &= \frac{V_{0r}^2 / R}{V_{sr} \times \frac{V_{0r}}{R}} = \frac{V_{0r}}{V_{sr}} = \frac{115}{230} = \frac{1}{2} = 0.5\end{aligned}$$

5. A 3-phase VSI supplies a purely capacitive 3-phase load. Upon Fourier analysis, the output voltage waveform is found to have an n -th order harmonic of magnitude α_n times that of the fundamental component ($\alpha_n < 1$). The load current would then have an n -th order harmonic of magnitude is

- A) Zero
- B) α_n times the fundamental frequency component
- C) $n\alpha_n$ times the fundamental frequency component
- D) α_n/n times the fundamental frequency component

Correct Answer: C

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

$$V_0(t) = \sum_{n=1,3,5,\dots} V_n \sin(n\omega t)$$

$$i_L(t) = C \frac{dV_0(t)}{dt} = \sum_{n=1,3,5} n\omega C V_n \cos(n\omega t)$$

$\Rightarrow$ n -th order current harmonic,

$$i_{Ln} = n\omega C V_n$$

$\Rightarrow$ Fundamental component,

$$i_{L1} = \omega C V_1$$

$$V_n = \alpha_n V_1$$

$$\Rightarrow i_{Ln} = n\alpha_n i_{L1}$$

6. For a dc-dc buck converter with supply voltage V_s , switch chopping frequency f , output voltage V_0 , output power P_0 , the critical inductance L_C for filter circuit is

A) $\frac{V_0(V_s - V_0)}{2fP_0}$

B) $\frac{V_0(V_s - V_0)}{fP_0}$

C) $\frac{V_0^2(V_s - V_0)}{2fV_sP_0}$

D) $\frac{V_0^2(V_s - V_0)}{fV_sP_0}$

Correct Answer: C

Not Attempted : !

Marks : 2 / 0.66 (-Ve)

For critical case, $I_{\min} = 0$

$$I_0 = \frac{I_{\max}}{2}$$


$$T_{\text{on}}: \Delta V_L = V_s - V_0 = \frac{L_C \Delta I_L}{T_{\text{on}}} = L_C \frac{I_{\max}}{DT}$$

$$L_C = \frac{(DT)(V_s - V_0)}{I_{\max}}$$

$$= \frac{D(V_s - V_0)}{2I_0 f} = \frac{DV_s(V_s - V_0)}{\frac{2P_0}{V_0} f V_s}$$

$$L_C = \frac{V_0^2(V_s - V_0)}{2fV_sP_0}$$

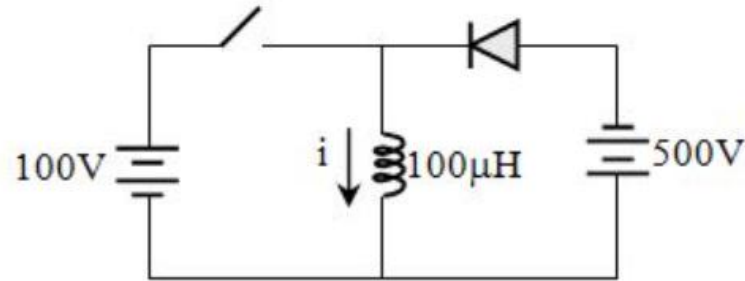7. The given converter circuit is operated at boundary of continuous and discontinuous conduction, the switching frequency is $f = 10 \text{ kHz}$. The value of $T_{\text{on}}/T_{\text{off}}$ is _____.



Correct Answer: **5**

Answer Range: **(5 , 5)**


Not Attempted : 

Marks : 1 / 0 (-Ve)

$$\frac{V_0}{V_s} = \frac{D}{1-D} \Rightarrow \frac{500}{100} = \frac{D}{1-D} \Rightarrow D = \frac{5}{6}$$

$$\frac{T_{\text{on}}}{T_{\text{on}} + T_{\text{off}}} = \frac{5}{6} \Rightarrow \frac{T_{\text{on}}}{T_{\text{off}}} = 5$$

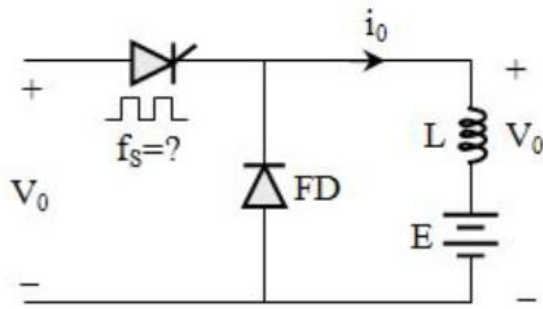8. An RLE load is operating in a chopper circuit from a 60 V supply. For the load $R = 0 \Omega$, $L = 60 \text{ mH}$, $E = 12 \text{ V}$ and duty cycle $D = 0.2$. The chopping frequency to limit amplitude of load current excursion to 1 A is



- A) 400 Hz
- B) 320 Hz
- C) 240 Hz
- D) 160 Hz

Correct Answer: **D**

Not Attempted : 


Marks : 2 / 0.66 (-Ve)

$$I_{\max} - I_{\min} = \frac{V_s - E}{fL} D = \frac{E(1-D)}{fL}$$

$$\Delta I = \frac{V_s - E}{fL} D$$

$$f = \frac{V_s - E}{L \Delta I} D = \frac{60 - 12}{60 \times 10^{-3} \times 1} \times 0.2 = 160 \text{ Hz}$$

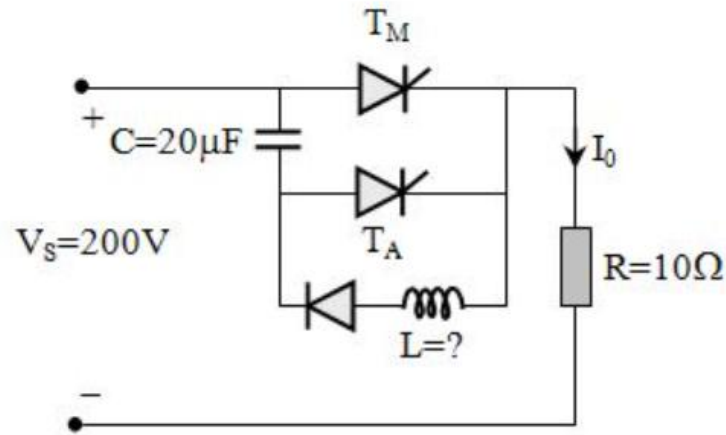9. A voltage commutated chopper is shown. The minimum value of inductor L in case maximum permissible current through the main SCR is 2.5 times load current, is _____ mH.



Correct Answer: **0.89**

Answer Range: **(0.8 , 0.9)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

$$i_{T_M, \text{ peak}} = \frac{V_s}{R} + V_0 \sqrt{\frac{C}{L}} \leq 2.5 \frac{V_s}{R}$$

$$\Rightarrow V_0 \sqrt{\frac{C}{L}} \leq 1.5 \frac{V_s}{R}$$

$$L \geq \frac{R^2 C}{1.5^2} = 888.88 \mu\text{H}$$

$$L_{\min} = 0.89 \text{ mH}$$

10. The main disadvantage of non-circulating current type dual converter is

- A) Power loss is high in comparison to circulating current type.
- B) Reversal of armature current not possible.
- C) Slow speed response due to commutation delay
- D) Only two quadrant operation is possible

Correct Answer: C

Not Attempted : 

Marks : 1 / 0.33 (-Ve)

Power loss is higher in circulating current type converter due to circulating current present.

Reversal of armature current is possible, but it is not smooth.

All four-quadrant operation is possible

11. For a buck-boost regulator, input voltage $V_s = 12V$, duty ratio $D = 0.25$, switching frequency 25 kHz , inductance $150 \mu\text{H}$ and filter capacitance $C = 220 \mu\text{F}$. If the average load current is 1.25A , the peak switch current is

- A) 2.067A
- B) 2.467A
- C) 1.650A
- D) 2.010A

Correct Answer: **A**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

$$I_{\text{sw,peak}} = \frac{I_o}{(1-D)} + \frac{\Delta I}{2}$$

$$\Delta I = \frac{DV_s}{fL} = \frac{0.25 \times 12}{25 \times 10^3 \times 150 \times 10^{-6}} = 0.8\text{A}$$

$$I_{\text{sw,peak}} = \frac{1.25}{(1-0.25)} + \frac{0.8}{2} = 2.067\text{A}$$

12. A dc battery is to be charged from a constant dc source of 220V. The battery is to be charged from its internal emf of 90V to 122V. The battery has internal resistance of 1Ω . If the charging current remains constant at 10A, the range of duty cycle is

- A) $0.41 < D < 0.55$
- B) $0.45 < D < 0.6$
- C) $0.41 < D < 0.6$
- D) $0.45 < D < 0.55$

Correct Answer: **B**

Not Attempted : 

Marks : 2 / 0.66 (-Ve)

$$V_0 = E_b + I_0 R$$

$$DV_s = E_b + I_0 R$$

$$D = \frac{E_b + I_0 R}{V_s}$$

$$D_{\min} = \frac{E_{b,\min} + I_0 R}{V_s} = \frac{90 + 10 \times 1}{220} = 0.4545$$

$$D_{\max} = \frac{E_{b,\max} + I_0 R}{V_s} = \frac{122 + 10 \times 1}{220} = 0.6$$

13. For the circuit realization of DC –DC converters, which of the following rule(s) is/are to be followed?

- A) Current sources should not be open circuited
- B) Voltage sources should not be short circuited.
- C) Inductor currents should not be interrupted
- D) Capacitor voltages should not be shorted.

Correct Answer: **A,B,C,D**

Not Attempted : 

Marks : 1 / 0 (-Ve)

All the given statements are fundamental rules of network theory and applicable to dc-dc converter circuits.

14. A DC chopper is used in regenerative braking mode of a dc series motor. The dc supply is 500 V, the duty cycle is 60%. The average value of armature current is 100 A. It is continuous and ripple free. The value of power feedback to the supply is _____ kW.

Correct Answer: **20**

Answer Range: **(20 , 20)**

Not Attempted : 

Marks : 2 / 0 (-Ve)

Incase of regenerative braking mode

$$V_s = V_0$$

$$V_0 = 500 \text{ V}, I_0 = 100 \text{ A}$$

For regenerative mode chopper is step-up chopper

$$V_0 = \frac{V_s}{1 - D}$$

$$V_s = V_0(1 - D) = 500(1 - 0.6) = 200 \text{ V}$$

$$\text{Power feedback to the supply} = V_s I_s = 200 \times 100 = 20 \text{ kW}$$

15. A single phase capacitor commutated CSI with Resistive load of R is 20 ohm. Commutating capacitor is 1 μ F. Minimum value of operating frequency to obtain sinusoidal current at output is

- A) 2.3 kHz
- B) 3.3 kHz
- C) 4.3 kHz
- D) 5.3 kHz

Correct Answer: D

Not Attempted : !

Marks : 2 / 0.66 (-Ve)

Minimum value of inverter operating frequency for obtaining sinusoidal output current for capacitor commutated CSI is,

$$\omega_{\text{minimum}} = \frac{2}{3RC}$$

Or,
$$f_{\text{minimum}} = \frac{1}{2\pi} \times \frac{2}{3 \times 20 \times 1 \times 10^{-6}}$$

$$F_{\text{minimum}} = 5.3 \text{ kHz}$$